

Digital Logic Design Equipment Training


Fall 2024

Training Objectives

- Breadboards
- Wiring
- Power Supply
- Voltmeter
- Logic Probe
- Logic Chips
- Switch Input
- LED Output
- Experiment – Digital Combination Lock


Breadboards

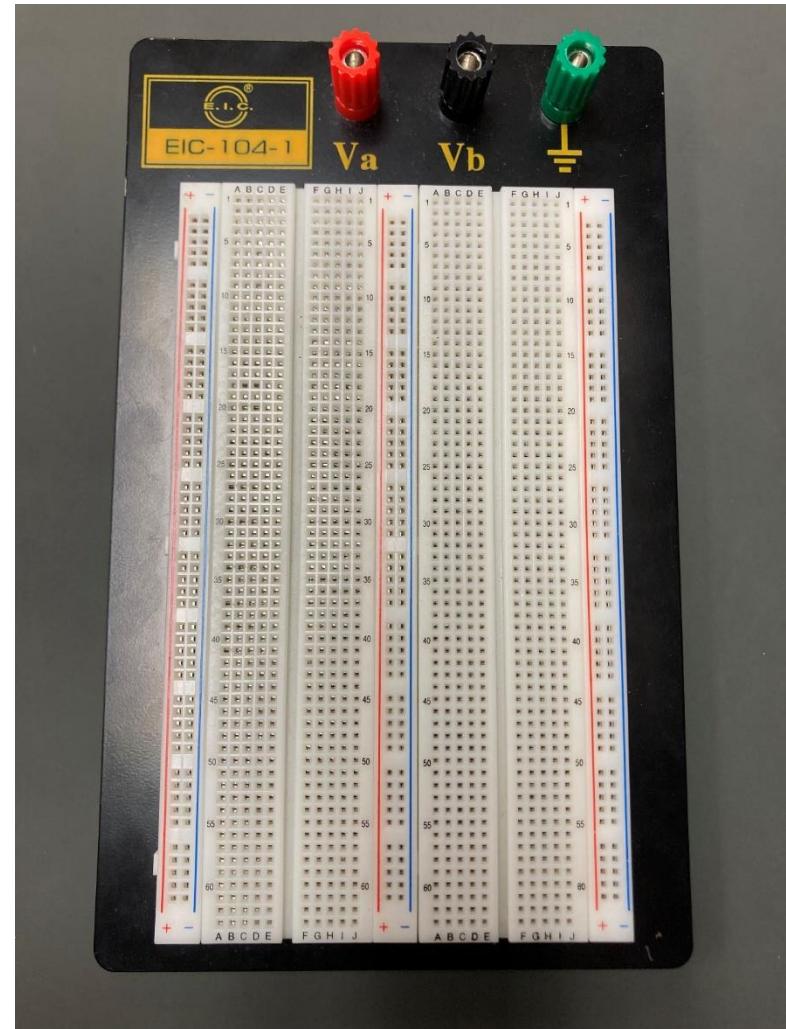- You will create all your circuits on breadboards like this one
- The Breadboard allows you to easily construct a circuit, make changes to it, and disassemble it.




Breadboards

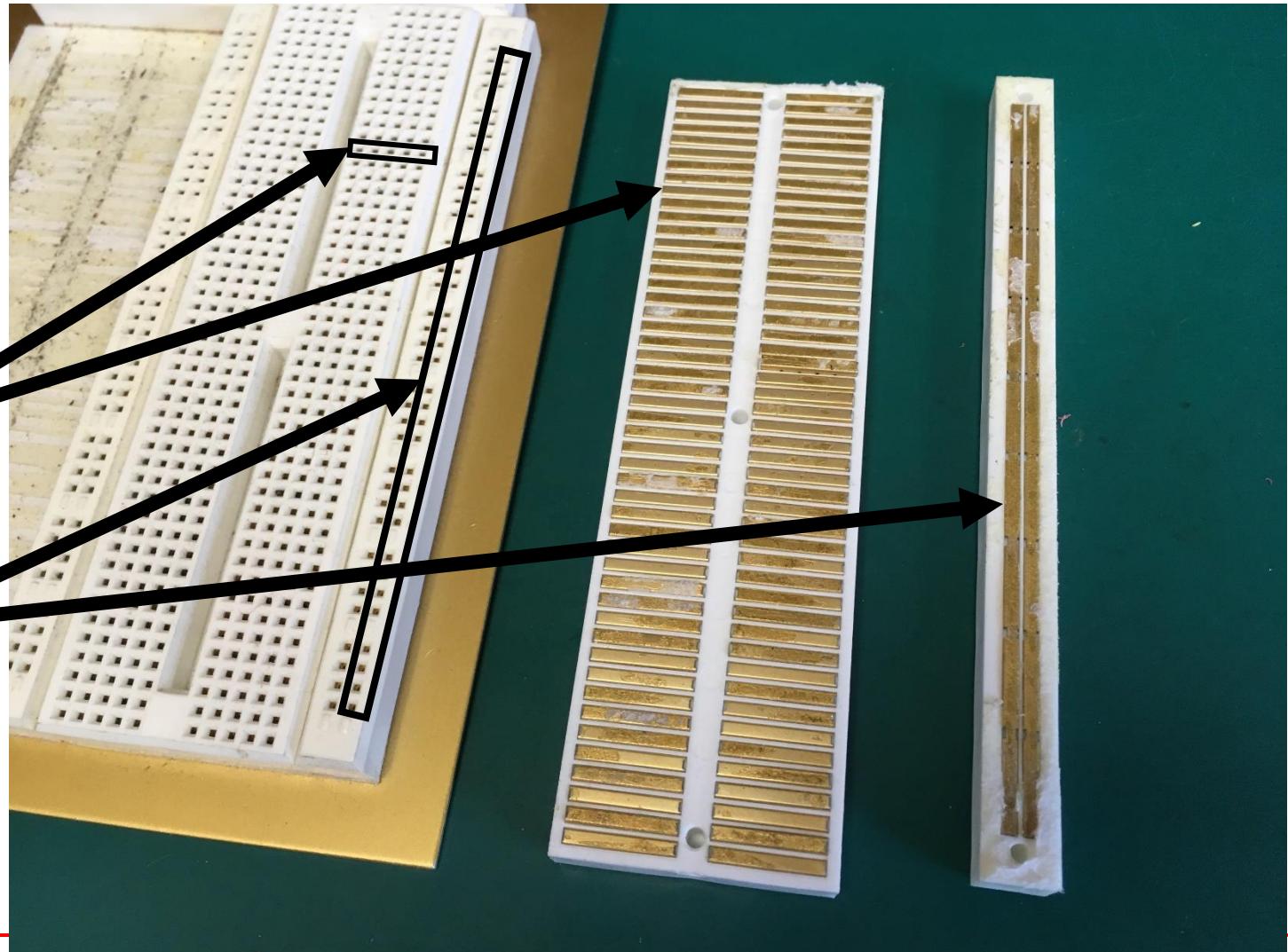- The holes are connected together in the back with metal strips.
- So these five holes are connected electrically.
- And all these holes are connected.




Power Supply

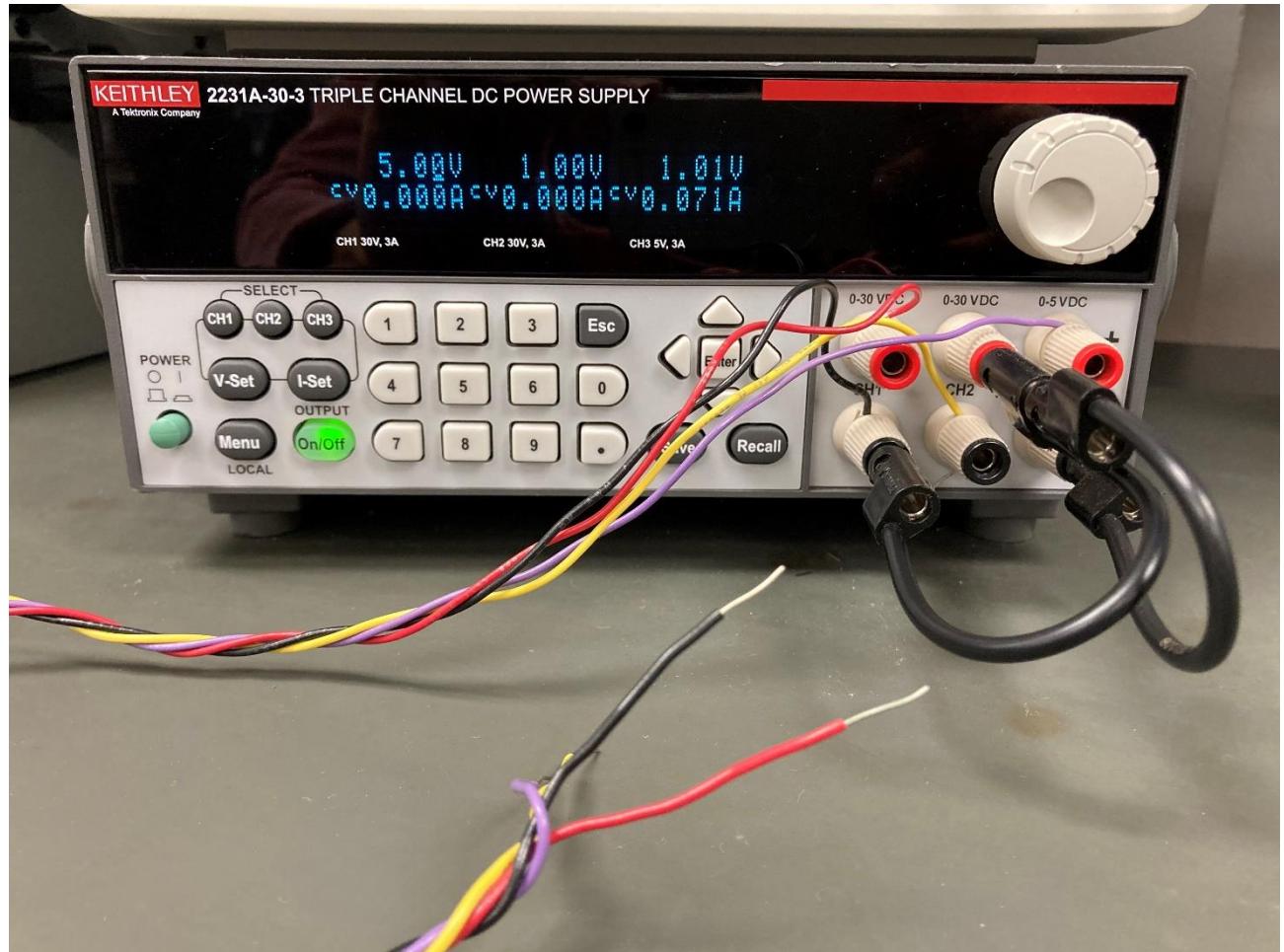- The logic circuits we will be using all require 5 VDC to operate.
- You will get the 5V power from a power supply that probably looks like this.
- The wiring is already connected:
 - **RED** wire is +5V
 - **BLACK** wire is Ground




Power Supply

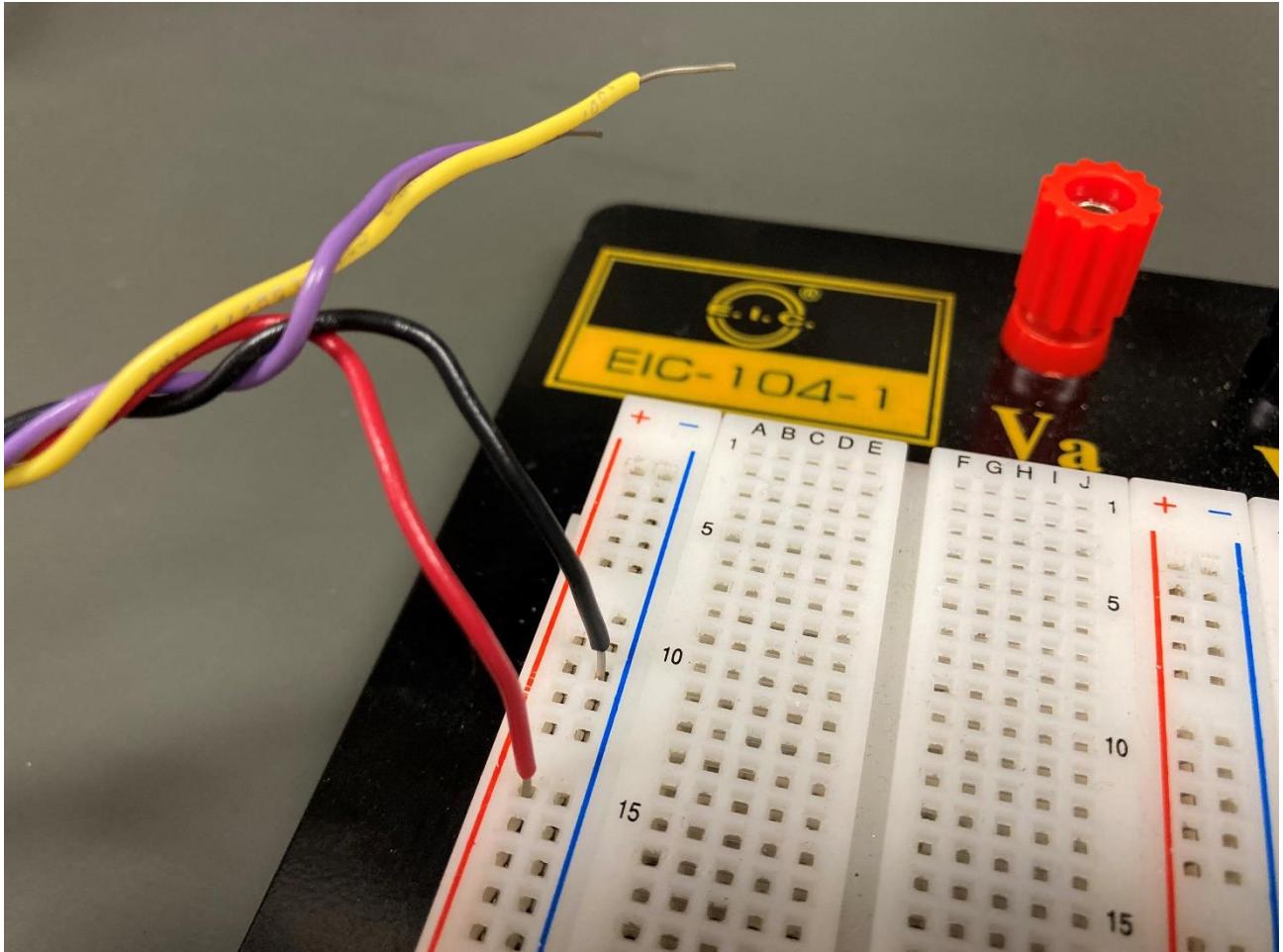- Connect your power supply to your breadboard.
- Connect the RED wire to the RED bus.
- Connect the BLACK wire to the BLUE bus. For whatever reason, they used blue instead of black.




Power Supply

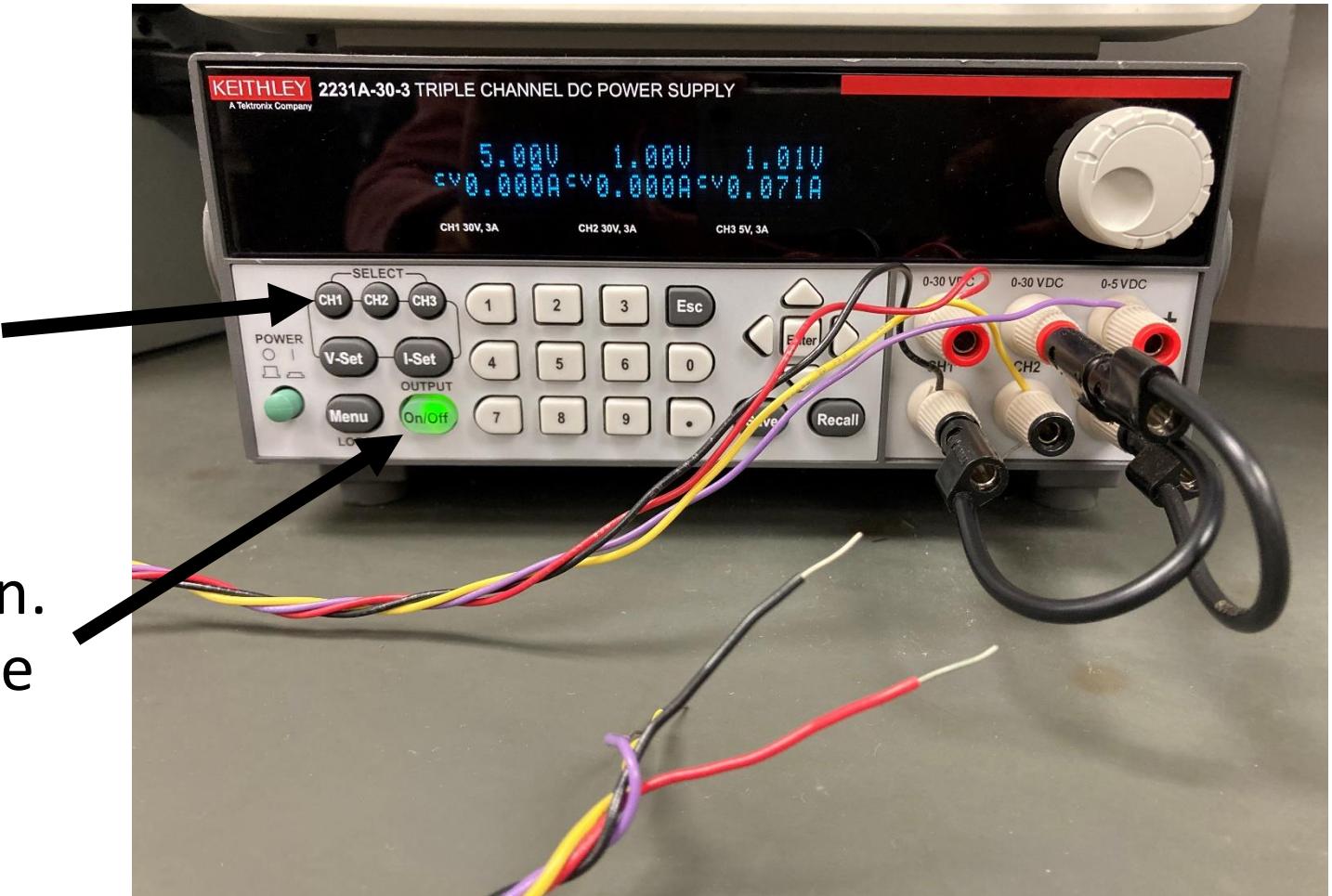- Turn on your power supply.
- Program your power supply channel 1 for 5 Volts. Push the CH1 button, then 5, then Enter.
- Push the On/Off button. This will energize all the outputs.



Voltmeter

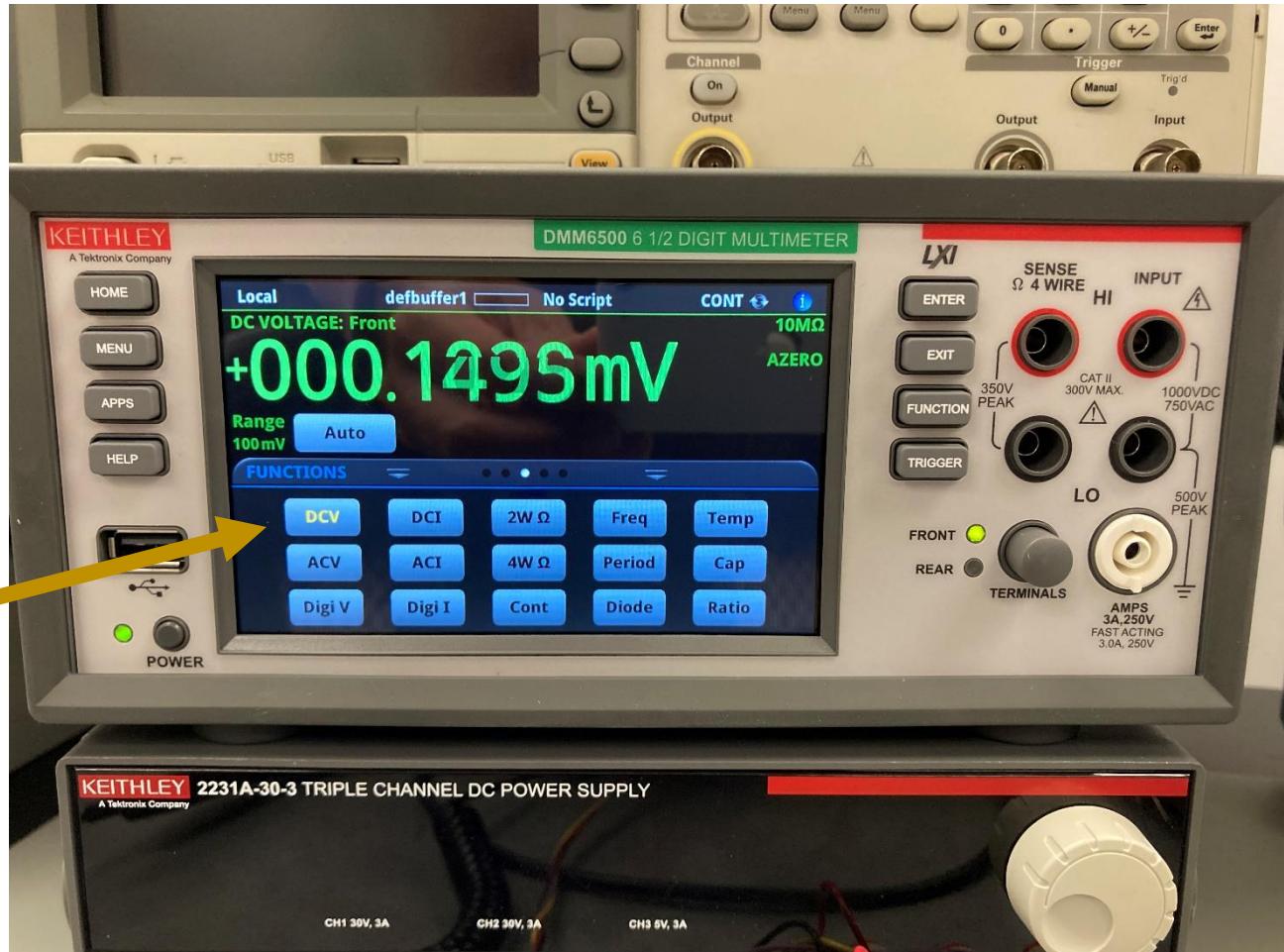- You might need to use the voltmeter to see what is going on inside your circuit.
- Your meter will probably look like this.
- Turn it on, and push the DCV button for measuring DC Voltage.




Voltmeter

- Connect your voltmeter to your breadboard using the banana-plug/coax/minigrabber cable.
- There is a small tab on one side of the banana-plug – this goes in the black ground hole on the voltmeter.
- The meter should read +5 volts.




Logic Probe

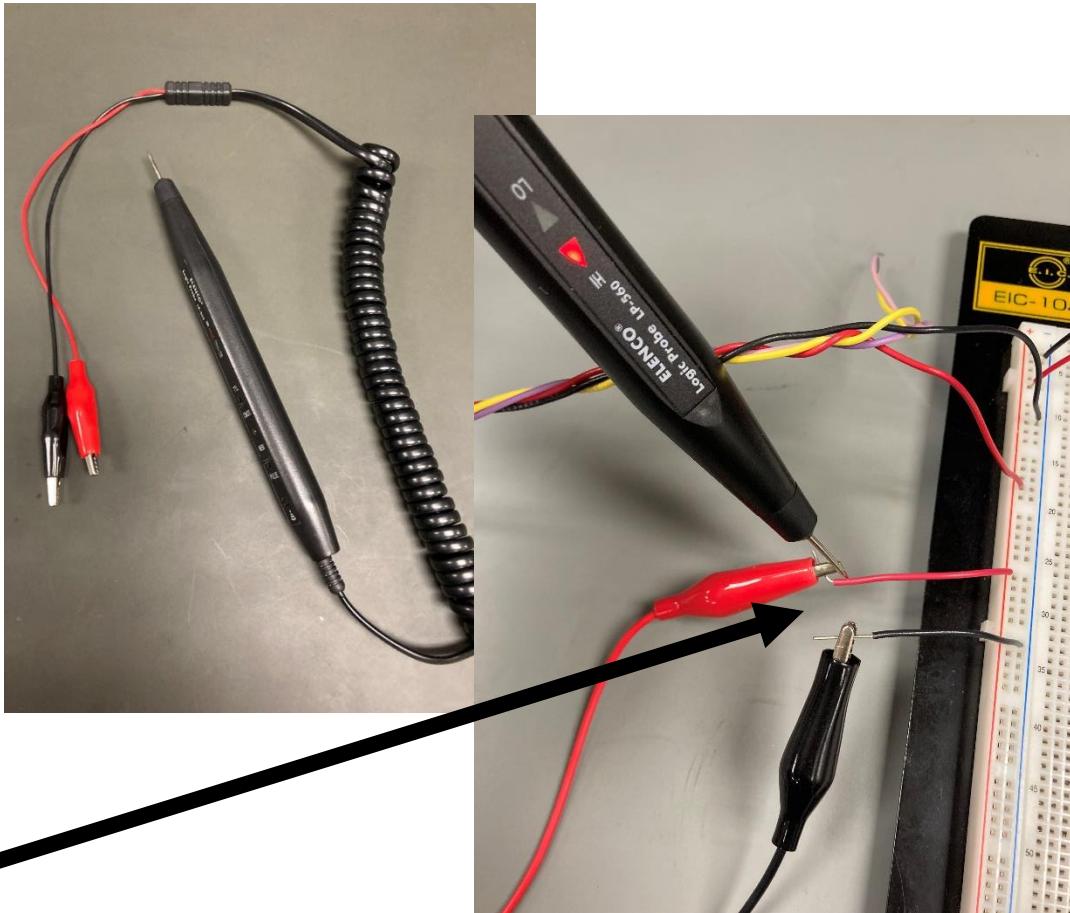- You can also use the logic probe to check the logic state of a signal.
- The green LED will light if the signal is a logic low, and the red LED will light if the signal is a logic high.
- There is also a low tone for logic low, and high tone for logic high.
- Put the probe on the +5 V and see. Then put probe on Ground.



First Logic Circuit

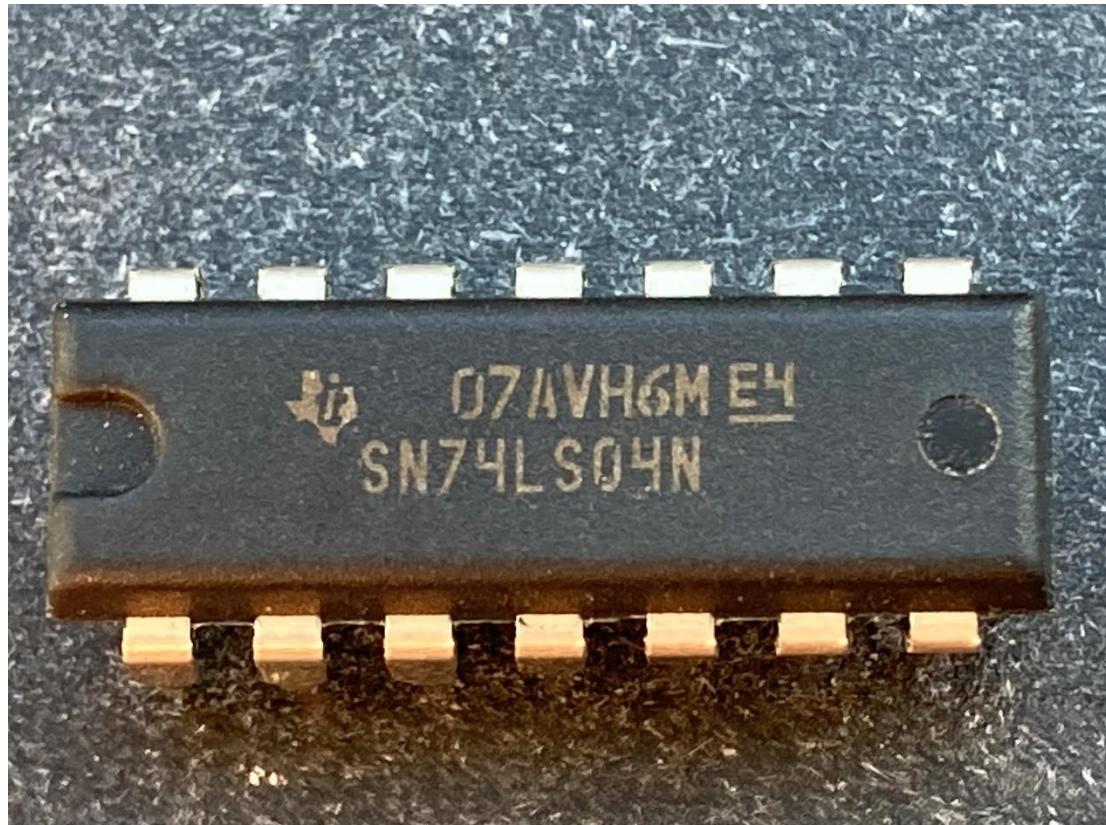- The logic chips we use are in a DIP package. DIP is short for “Dual In-Line Package”. The distance between pins is 0.10 inches. The package is 0.30 inches wide.
- We will be using 7400 series LS TTL logic chips. TTL is short for “Transistor-transistor logic”, and LS is short for “Low-power Shottkey”.




First Logic Circuit

- The 7400 series was one of the early logic families from the 1970's.
- Several variants of the series have been created since, including S (Shottkey), LS (Low-Power Shottkey) which is the type we use, and HC (high-speed CMOS).
- Other logic series have also been created, such as 4000 series CMOS.
- The difference is in what type of transistors are used to make them.
- For this lab, the first two digits will always be 74, then LS, and the next digits identify the function of the chip
 - 74LS04 – Inverter
 - 74LS08 – AND
 - 74LS32 – OR


First Logic Circuit

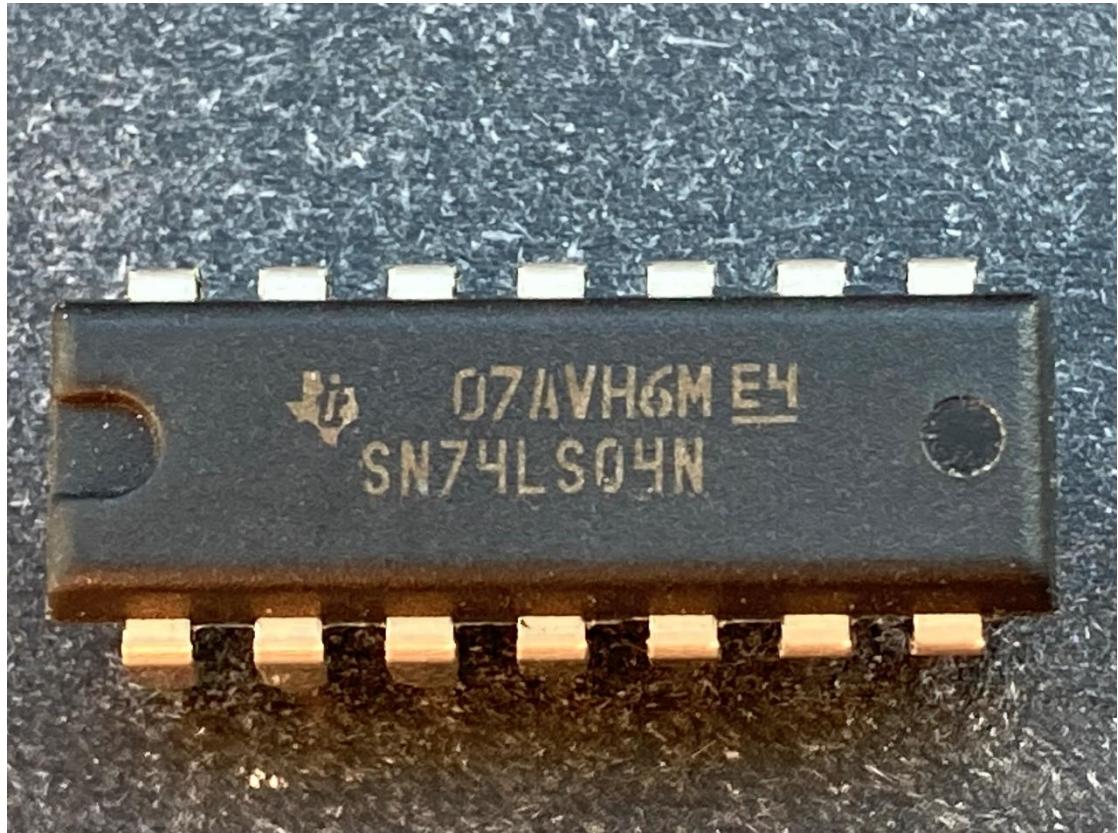- The part number is printed on the top of the chip. It can be a bit cryptic, and there are often extra letters and lines:
- The full part number is SN74LS04N
- The letters before the 74 usually identify the manufacturer. There is no real standard – manufacturers just picked some letters that no one else used. SN means “Texas Instruments”.




First Logic Circuit

- The extra letters at the end usually identify the temperature grade, and the package style.
- The N identifies the package type, which is PDIP, which just means plastic DIP package.
- Originally there was just DIP packages, but now there are several variations.
- SOIC (Small Outline IC), SOP (Small outline package), SO (Small outline), SSOP, QSOP, TSOP, LCC (Leadless chip carrier), BGA (Ball-grid array), and more...

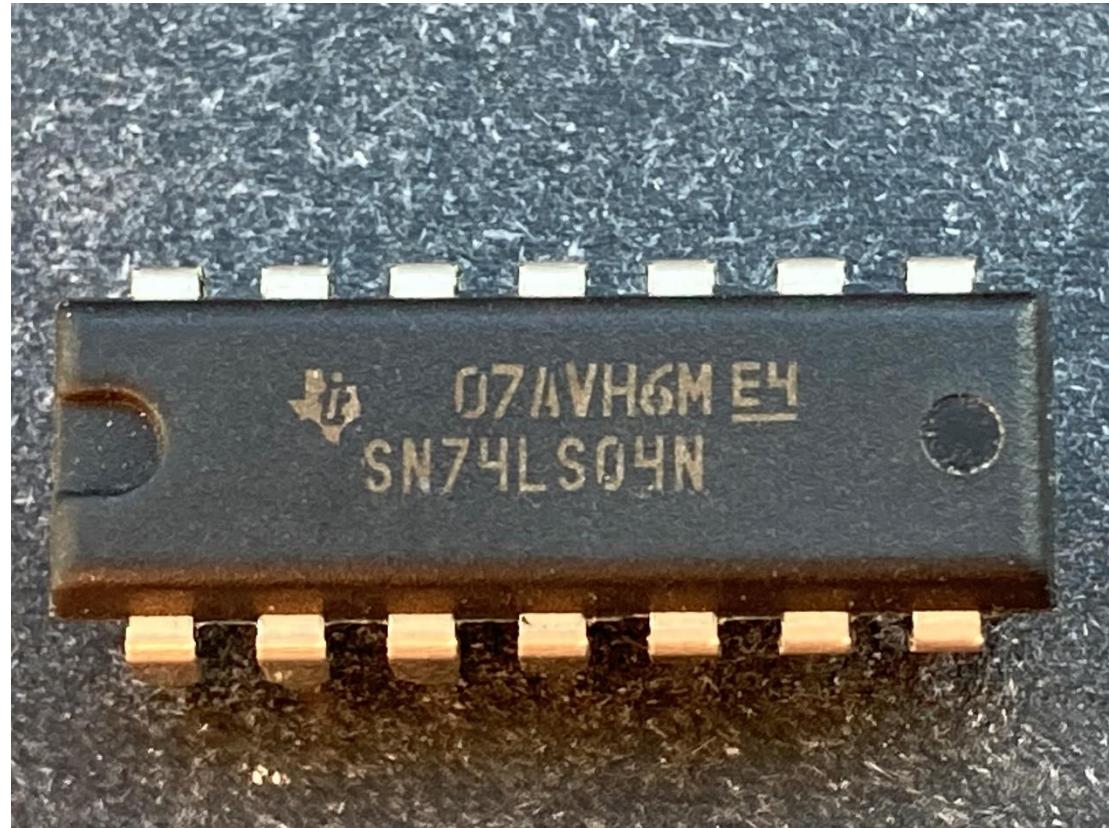


First Logic Circuit

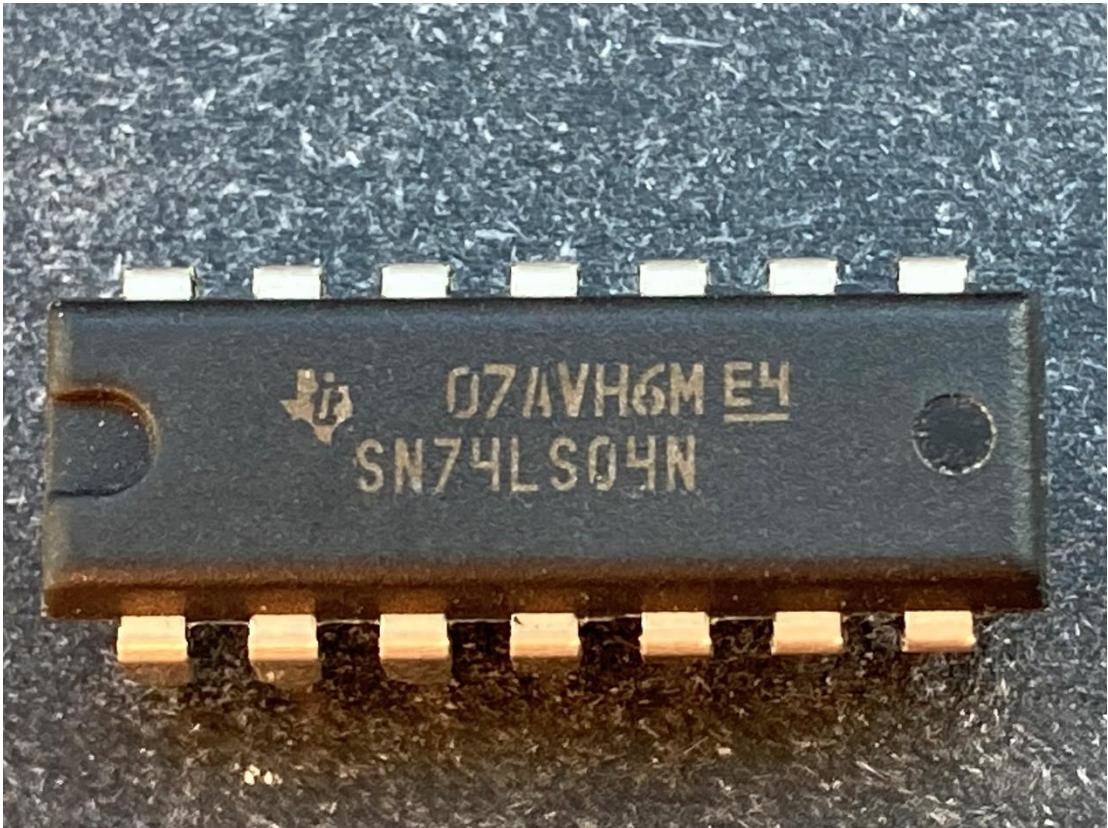- Often there is another letter which encodes the temperature grade of the chip. If there is no code, it usually means the chip is commercial temperature grade, which means the operating specification are guaranteed over a temperature range of 0°C to 70°C.
- The performance of semiconductors varies over temperature, which is why it has to be specified.




First Logic Circuit

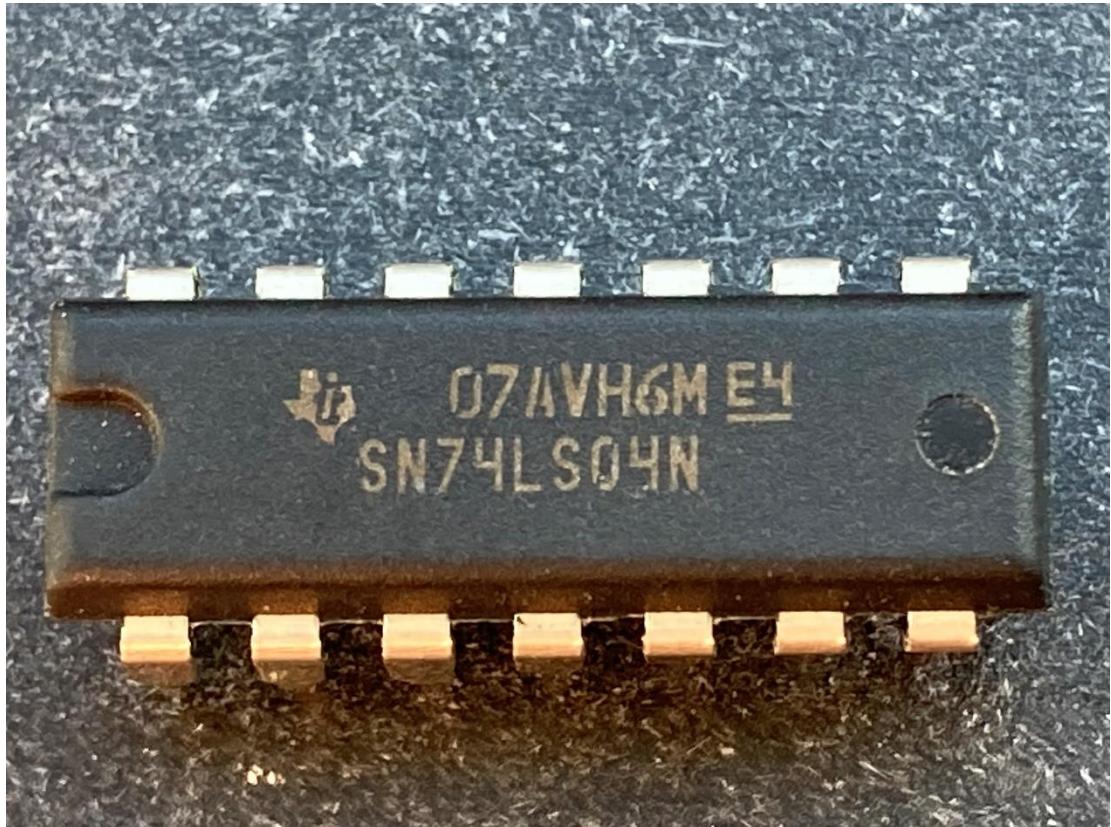- Note that the first line is NOT the part number in this example. It is some manufacturer specific codes, usually identifying where the chip was made and when.
- Typically the manufacture date is encoded as 4 digits. First 2 digits are the week of the year, and second two are year. 2420 would be 24th week of 2020. This chip uses a non-standard coding.





First Logic Circuit

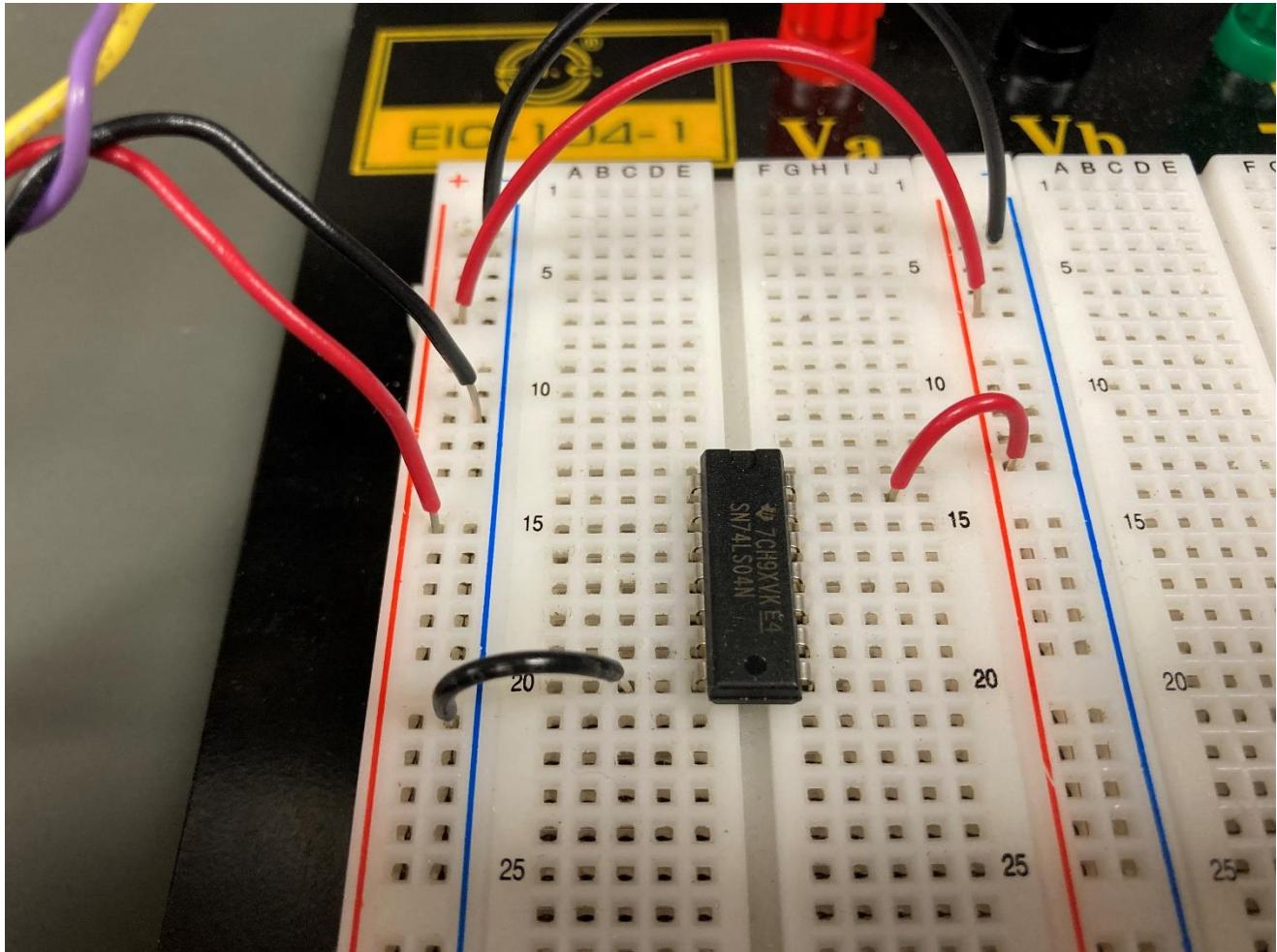- Find a “74LS04” hex inverter from the parts bins. The “hex” just means there are 6 identical inverters in the same package.
- Plug the inverter into your breadboard as shown. You can plug it anywhere as long as it straddles the center channel on the breadboard.



First Logic Circuit

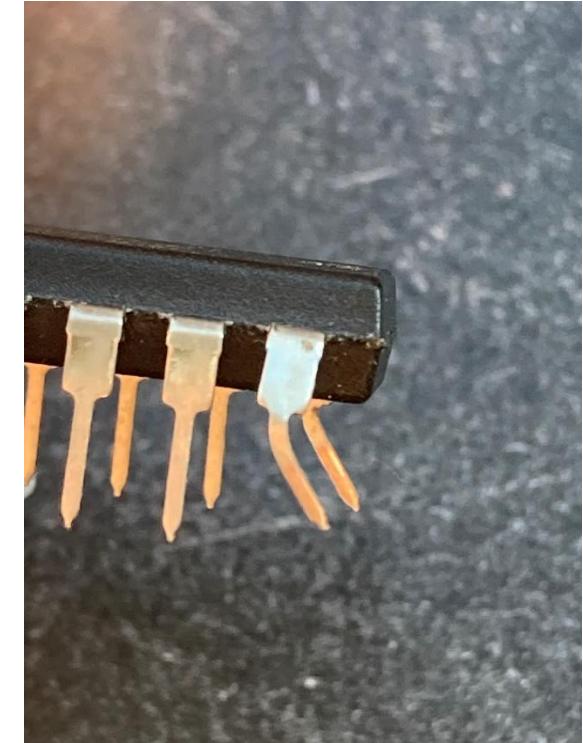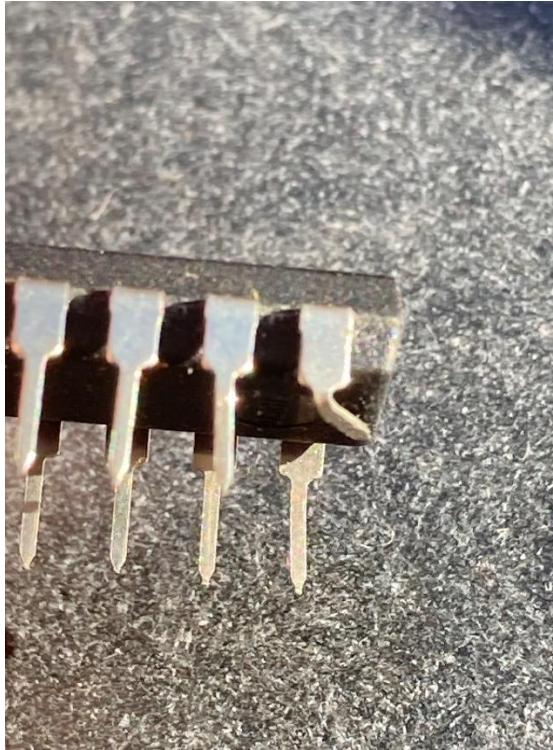
- Check the pins to make sure they are not bent or folded under.
- Folded under pins can be difficult to find, because once the chip is plugged into the breadboard, it looks fine – **BUT IT ISN'T!!**
- You can gently bend pins back with the pliers, but sometimes they will break.



When removing chips from breadboard, pull them straight out to avoid this problem.


Wiring

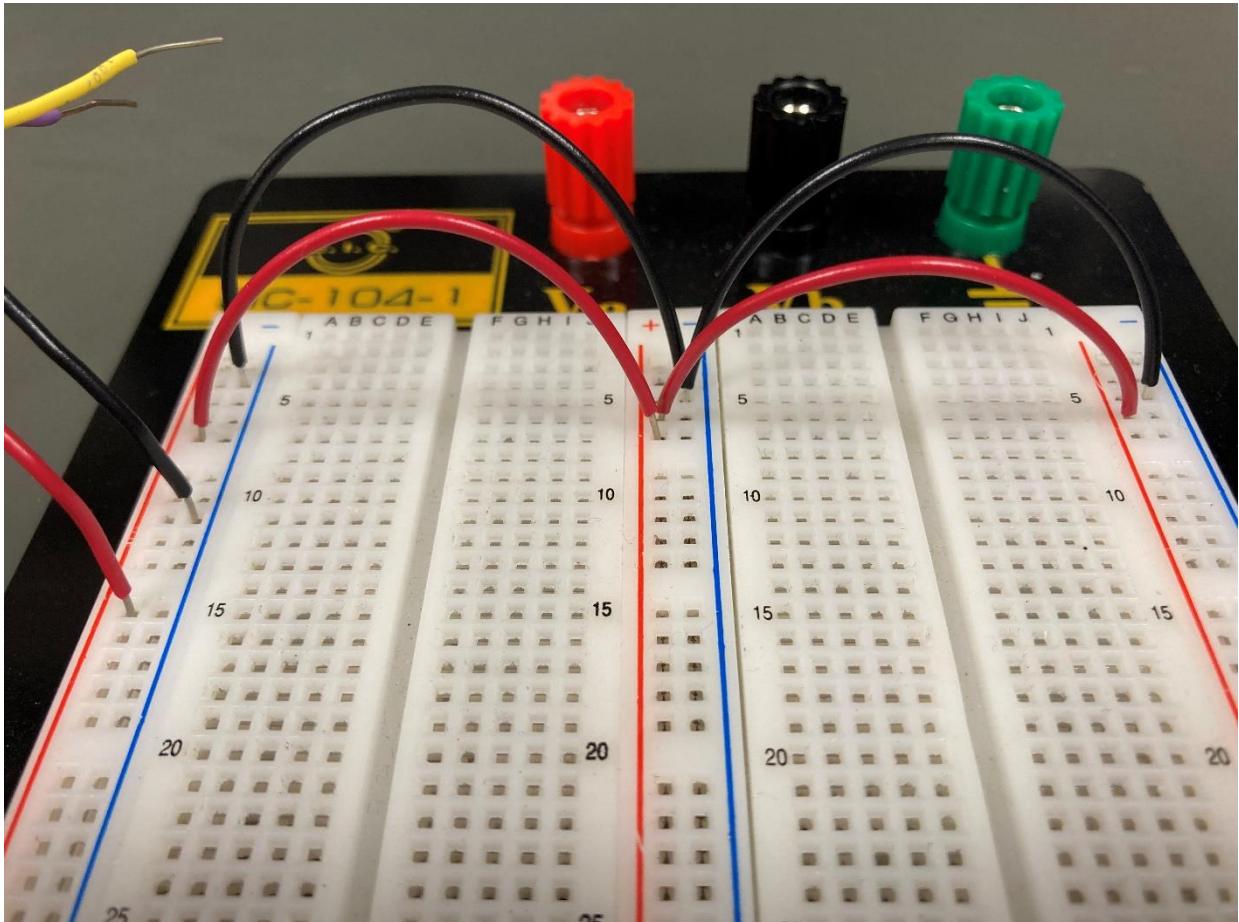- The power/ground busses are all separate, so you have to jumper to connect them.




First Logic Circuit

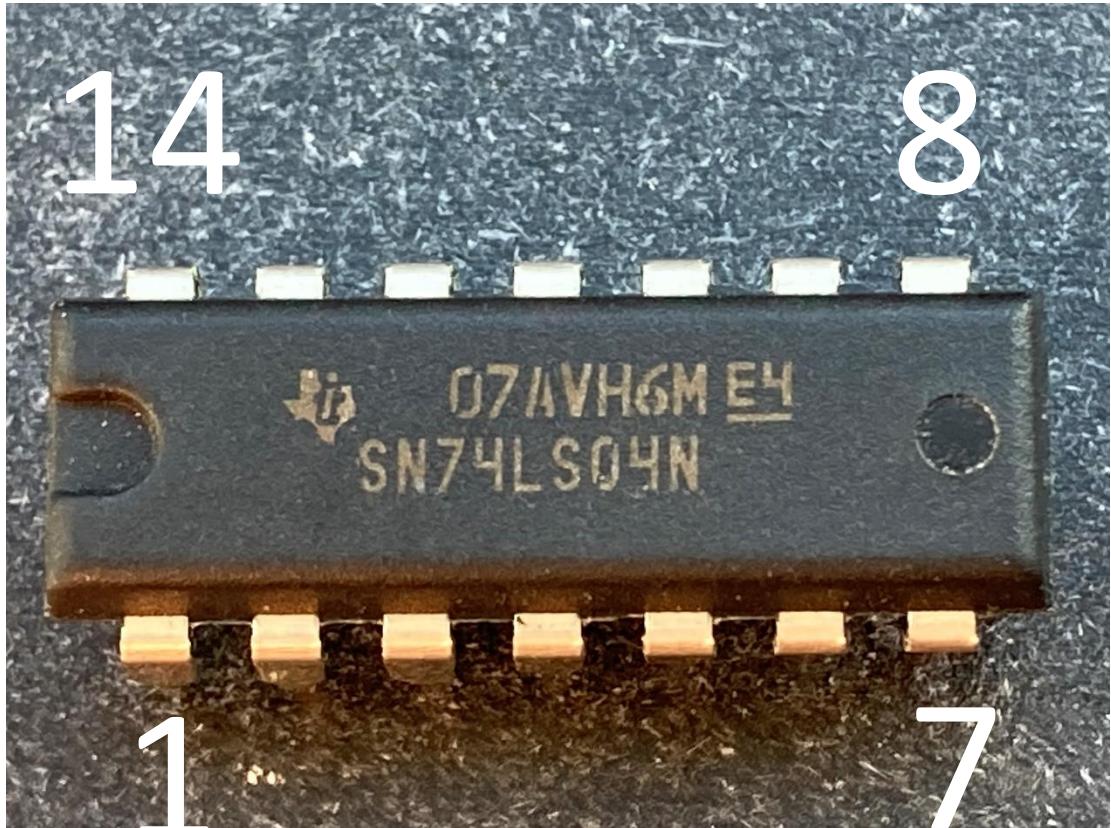- All the logic chips will require +5V in order to work. For the 74LS04, power goes to pin 14, and ground goes to pin 7.
- There is a dot or a notch on one end of the chip. Orient the chip with the dot or notch to the left. Pin 1 is on the bottom left corner. From there the pins are numbered in a counter-clockwise direction. Pin 14 is in the upper left corner.



First Logic Circuit

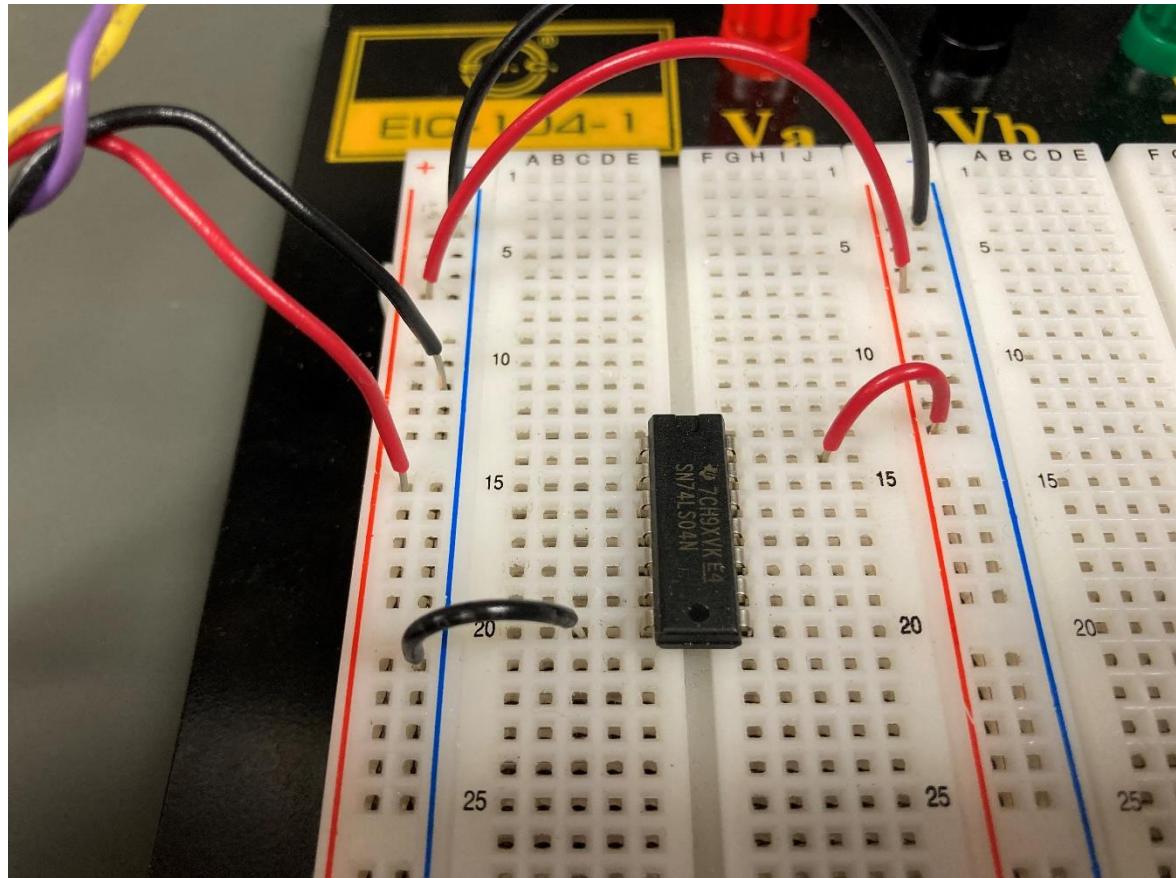- Using a red wire jumper, connect from the +5V bus to pin 14 of the inverter.
- Using a black wire jumper, connect from the ground bus to pin 7 of the inverter.




First Logic Circuit

- The function of the pins, called the pinout, is described in the manufacturer's data sheet for the part.
- It is not always obvious – the inverter input is A, and its output is Y. They are numbered 1 to 6.
- Pin 1 is the input to inverter 1 (1A), pin 2 is the output of inverter 1 (1Y)
- The pinout for different package types is often provided, like here for the SN5404, which is the military grade version.


**SN5404, SN54LS04, SN54S04,
 SN7404, SN74LS04, SN74S04
 HEX INVERTERS**

SDLS029C – DECEMBER 1983 – REVISED JANUARY 2004

SN5404 . . . J PACKAGE
 SN54LS04, SN54S04 . . . J OR W PACKAGE
 SN7404, SN74S04 . . . B, N, OR NS PACKAGE
 SN74LS04 . . . D, DB, N, OR NS PACKAGE
 (TOP VIEW)

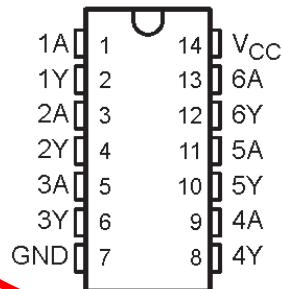


SN5404 . . . W PACKAGE
 (TOP VIEW)

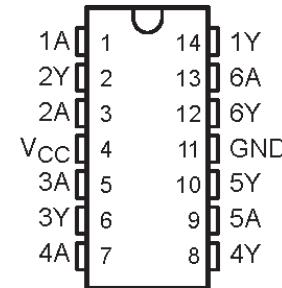


Wiring

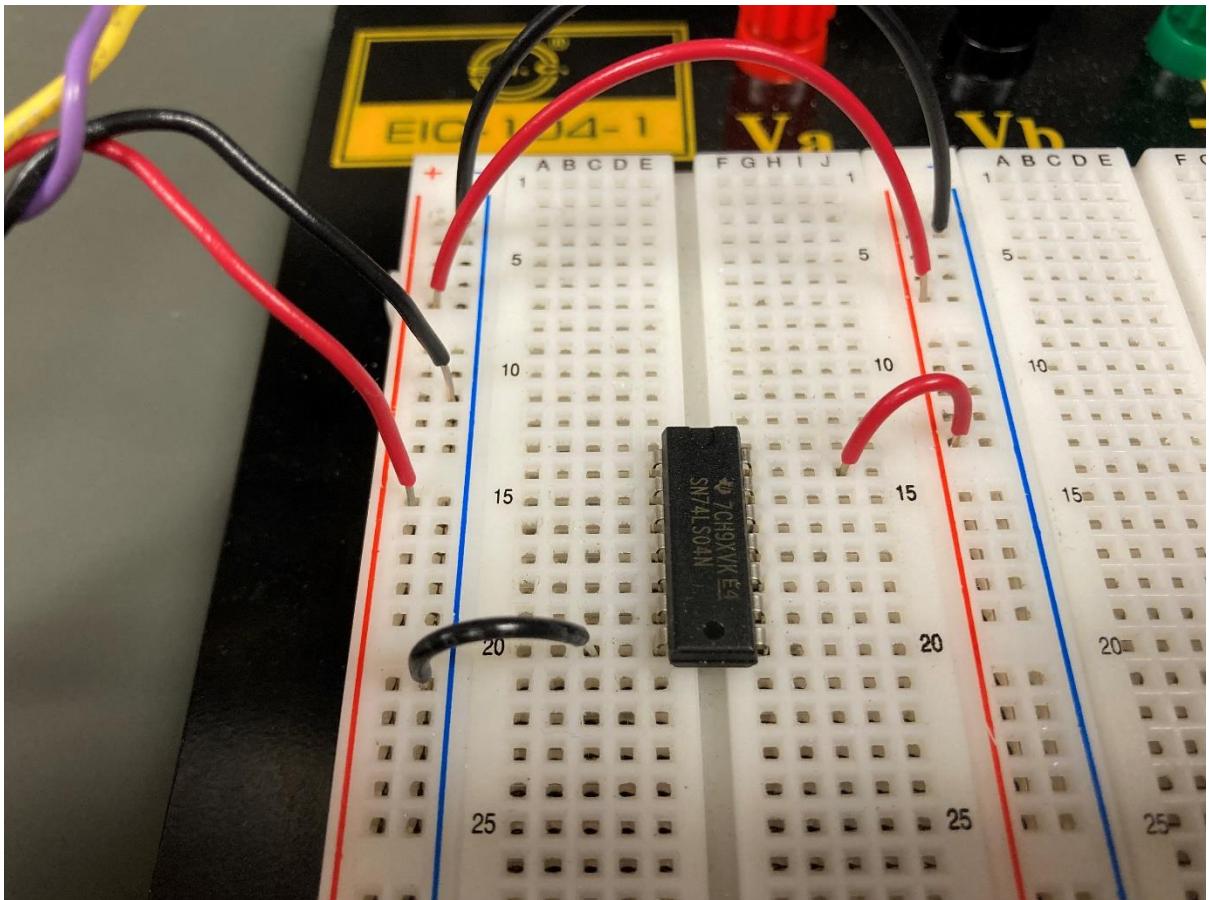- Please color code your power and ground wires. That makes it easier to identify wiring errors, and easier for your TA to help you if your circuit is not working.
- Don't use red and black for the signal wires – there are plenty of other wire colors in the lab.





Wiring

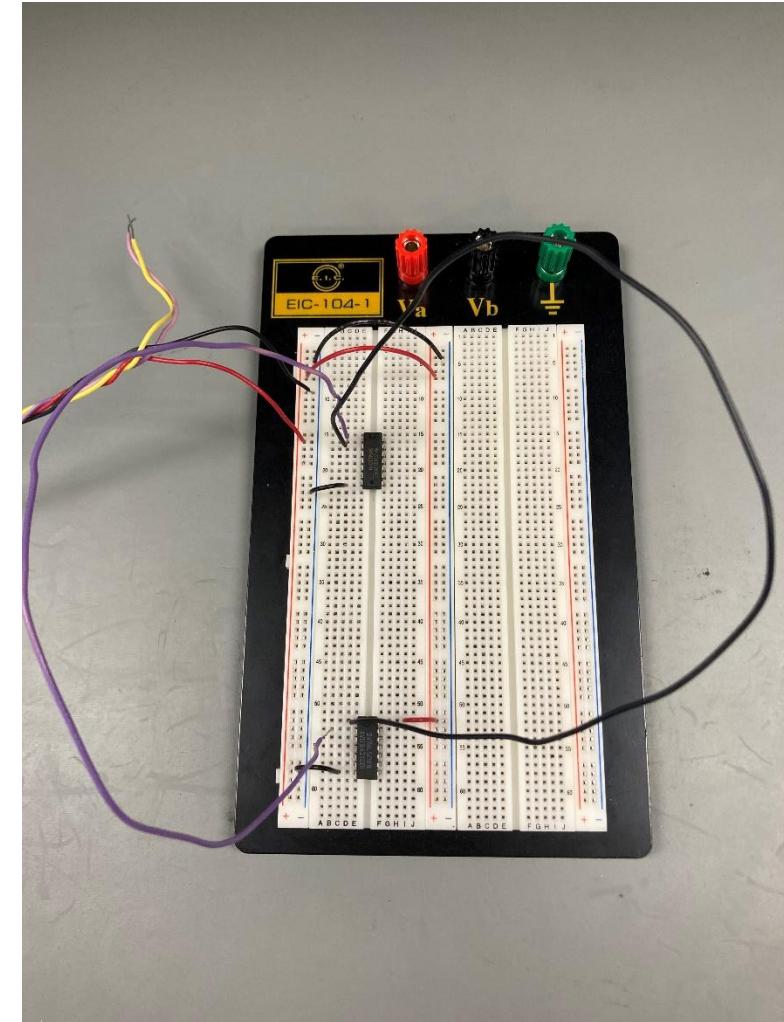- Try to position chips near each other that have a lot of wiring connections between them.
- These chips could be closer together.
- Avoid excessively long wires.




Wiring

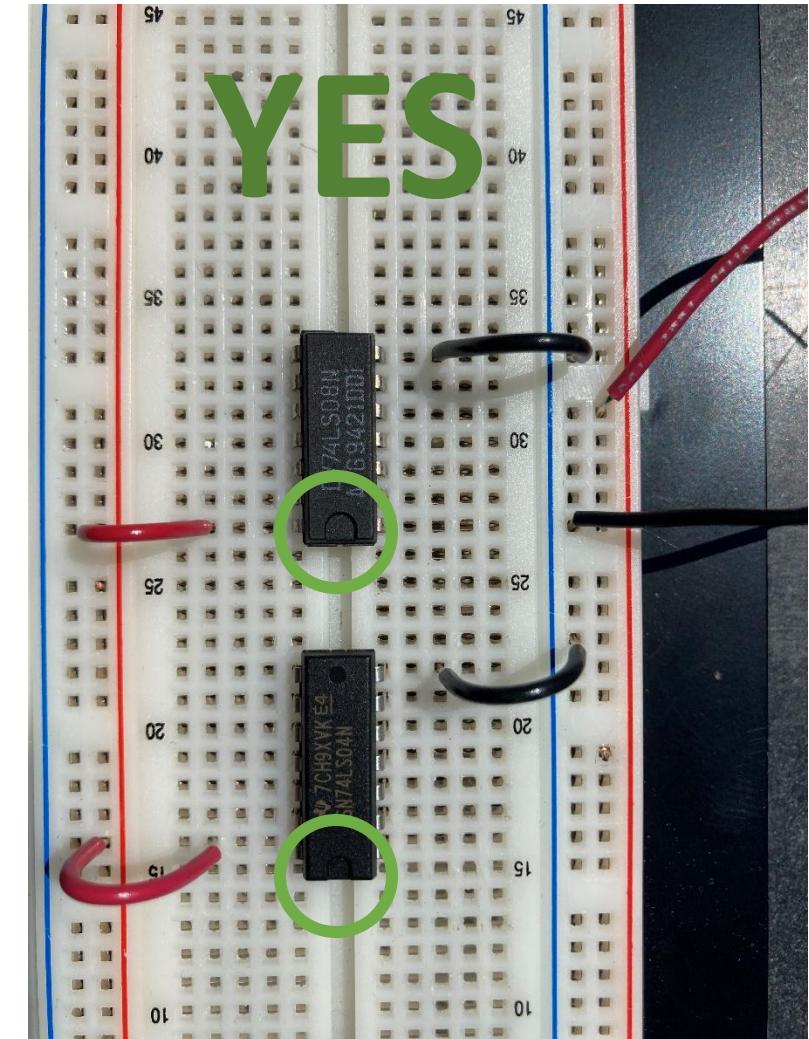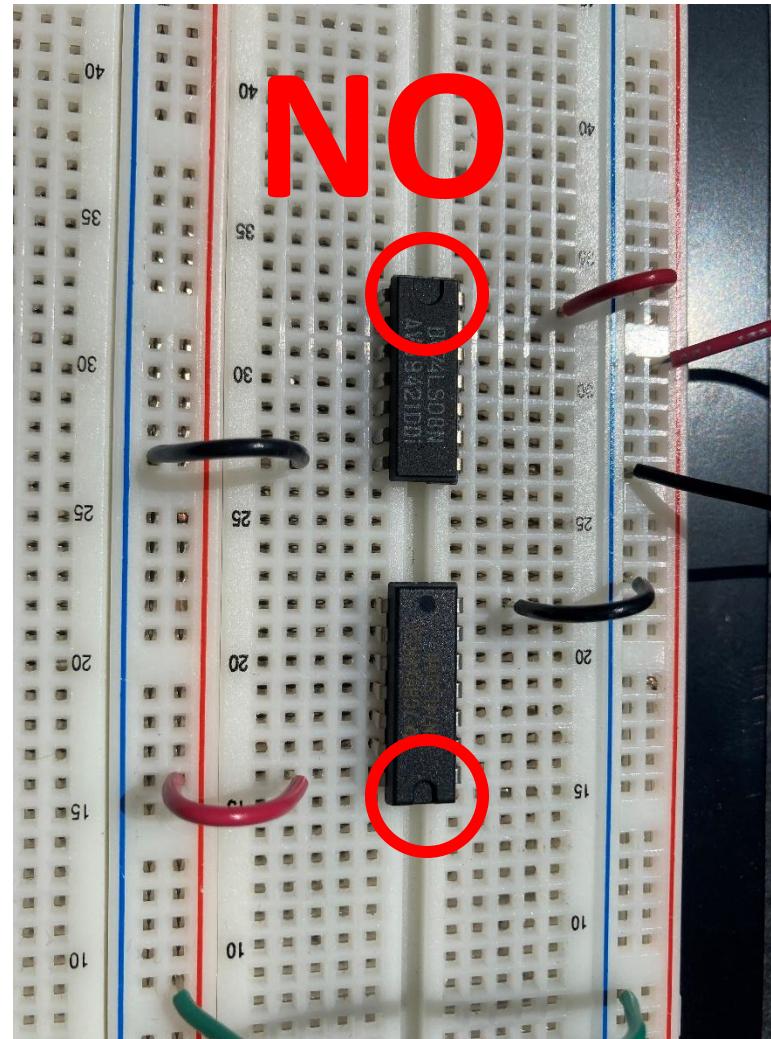- Put all the chips with the notch the same way!
- Keeping them all pointed the same way is one less thing to worry about.



Wiring

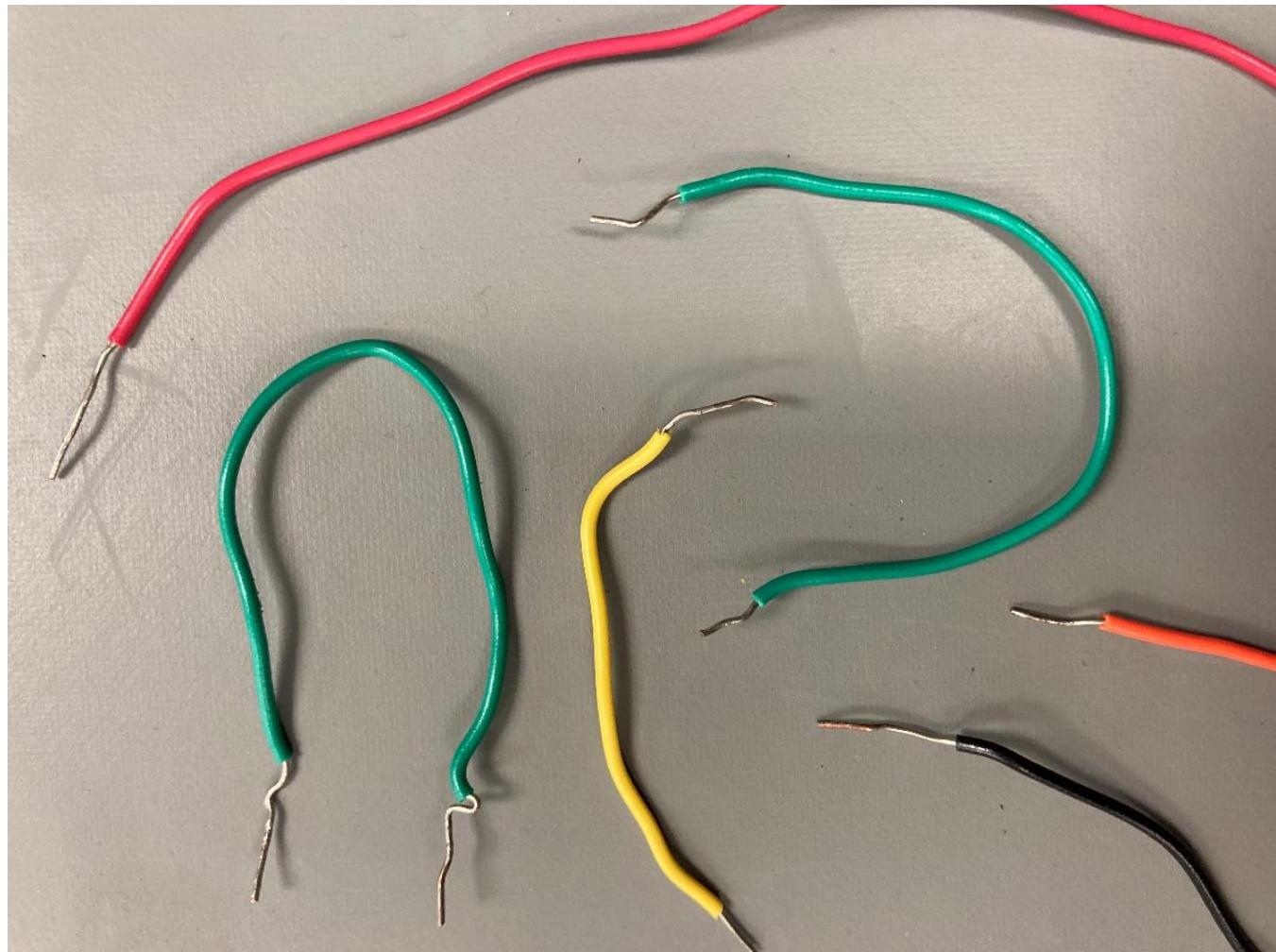- Cut off and re-strip the ends of wires if they are mangled. It will be difficult to insert mangled wires into the breadboard.





Wiring

- Use the second notch down from the end for stripping the wires.
- The notch will be labeled 24, which is for stripping 24 AWG wire.
- AWG is short for “American Wire Gauge” which is a wire diameter standard.





Wiring

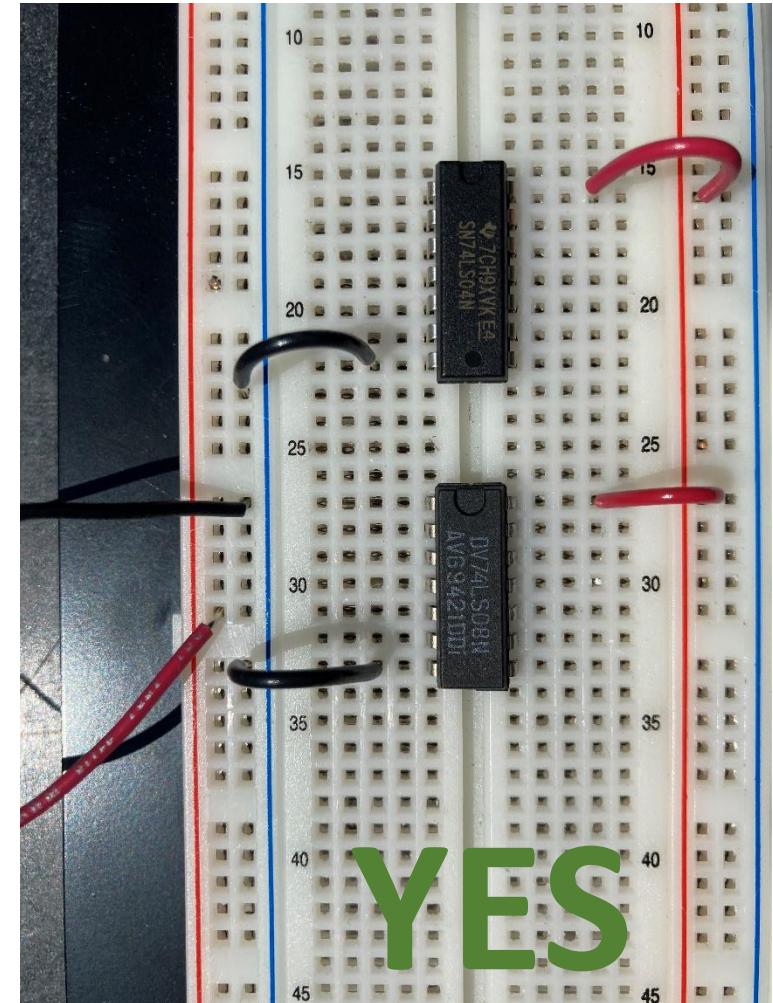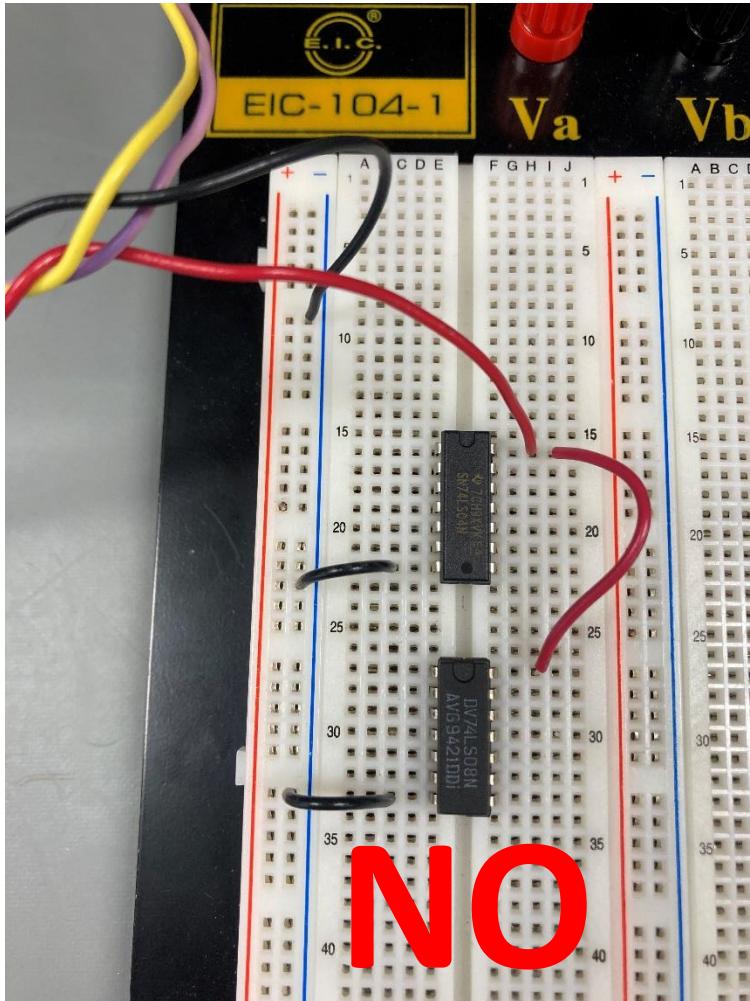- Don't "daisy-chain" the power connections to the chip. Jumper from the power/ground bus to the chips.




Wiring

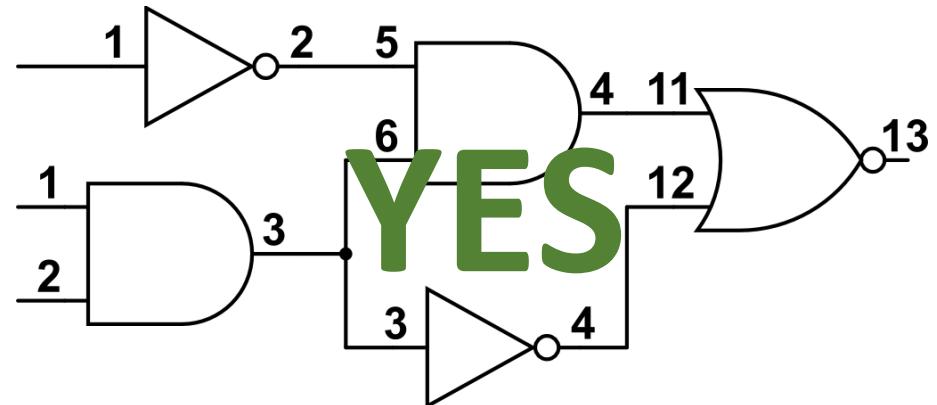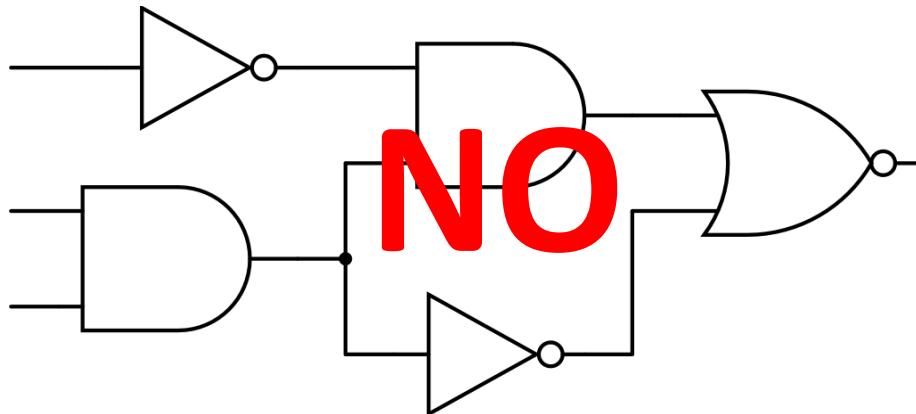- Draw a schematic, and label all the pin numbers.
- Many logic chips have more than one gate in them. It is very difficult to remember which gate you used where.
- Which circuit would you rather wire? And troubleshoot!?




First Logic Circuit

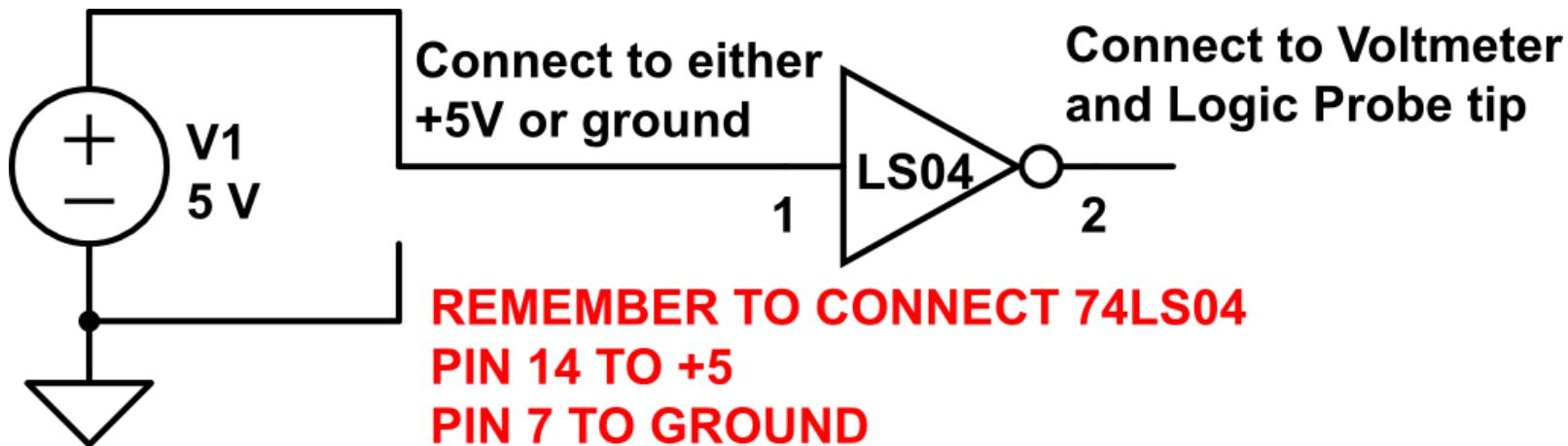- Put a jumper from pin 1 of the 74LS04 to +5V. Pin 1 is the input of the first inverter in the chip.
- Connect your voltmeter and logic probe to pin 2.





First Logic Circuit

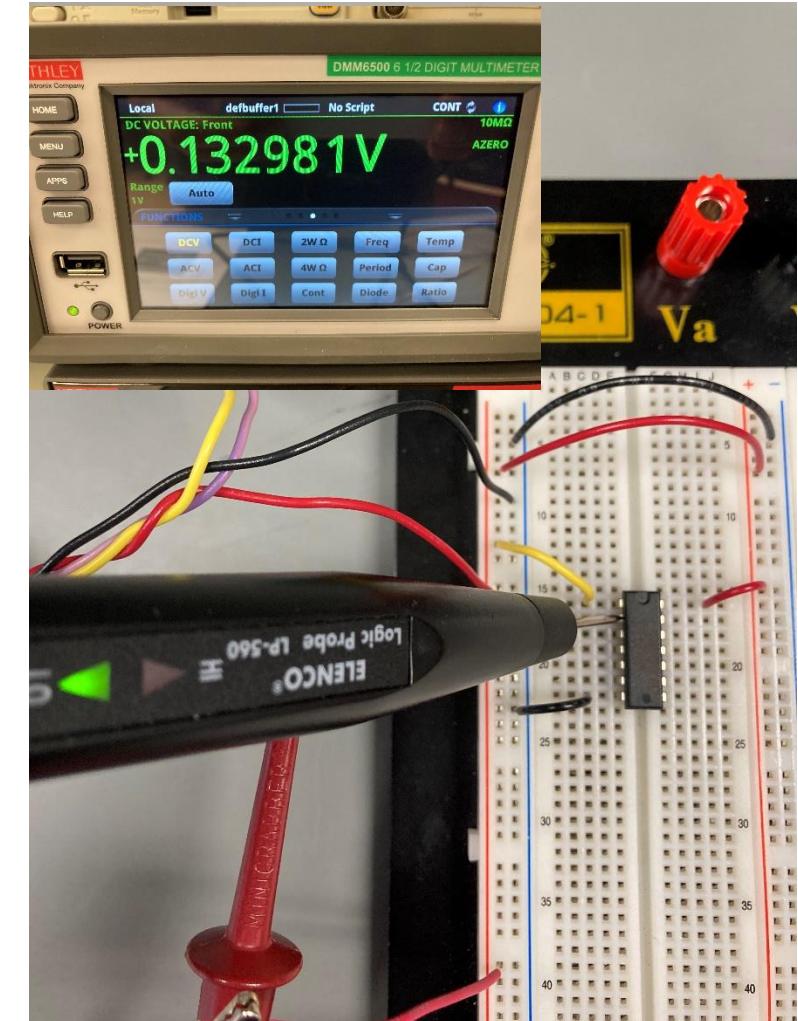- What do you see?
- With a logic 1 (+5V) going in, a logic 0 (0V) should be coming out.
- Note the voltmeter shows close to 0V, but not exactly.
- Move the pin 1 jumper to +5v.
- Check the logic level on pin 2 again. What do you see now?



Using Switches for Inputs

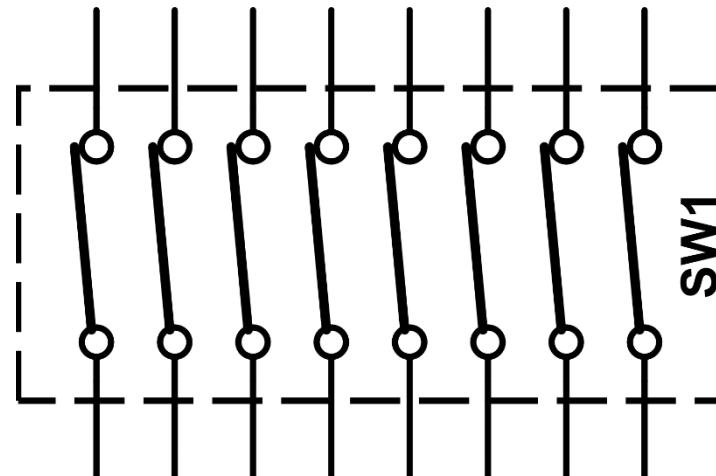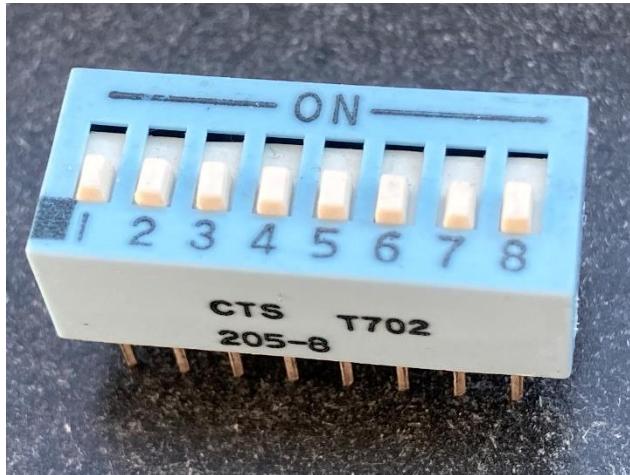- Using wires to create a logic input is annoying – it's better to use some switches.
- Get an 8 position DIP-Switch from the parts bins.
- There are 8 individual “SPST” switches in a single package, wired as follows.





Switches Types

- SPST means “Single-pole, Single-throw”.
- A switches pole are the number of individual switches that operate with the same handle.
- A two pole switch would be two switches that are connected to a single handle, and thus switch at the same time.


SPST
Single Pole
Single Throw



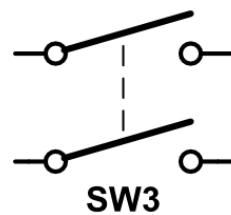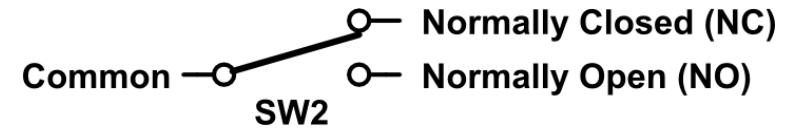SPDT
Single Pole
Double Throw
Common terminal can be connected to one of two other terminals.



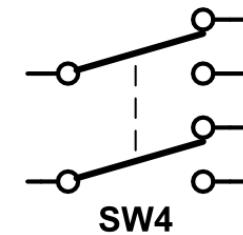
DPST
Double Pole
Single Throw
Two switches connected to the same handle.



DPDT
Double Pole
Double Throw


Switches Types

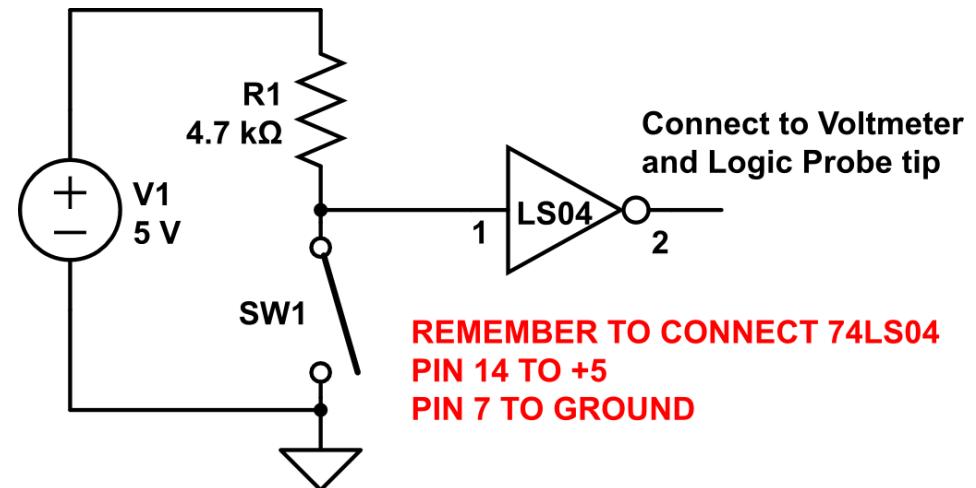- We need to wire a switch to pin 1, but there is a complication.
- Logic gate inputs do not like to be left “floating”, or not connected to anything. They should always be at either a high (5V) or low (ground).
- One way to solve the problem is by adding a “pull-up” resistor. As long as the value is not too big, this will hold the input high. Then connect the switch from the input to ground.



Switches Types

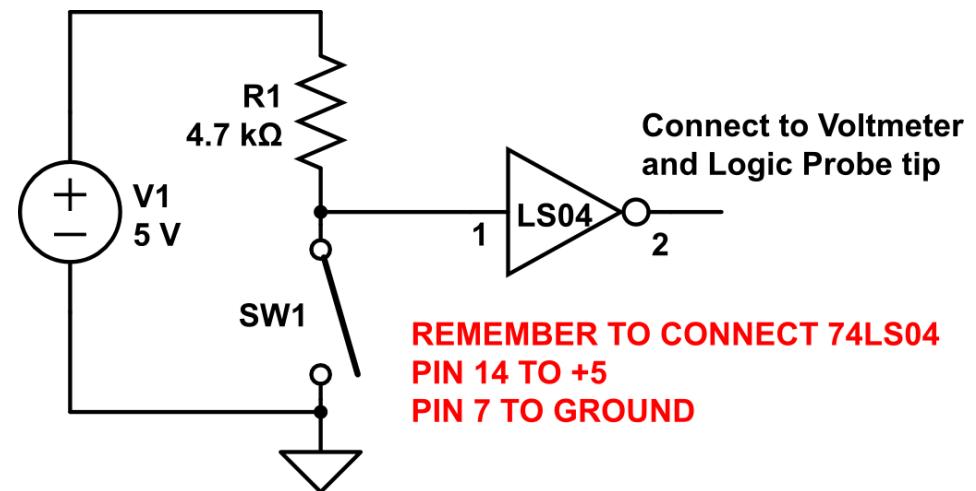- Wire up one of the switches in the DIP switch and a 4.7k pull-up resistor to pin 1.
- Watch what happens to the output on pin 2 as you open and close the switch.
- Switch closed is logic low input, which will be inverted and be a high on the output.




Output LEDs

- There will be times you need to see multiple logic levels at the same time.
- You can drive an LED with a logic gate output, but there are complications.
- TTL Logic gate outputs cannot supply much current. They are much better at sinking current – current flowing into the output pin.


Output LEDs

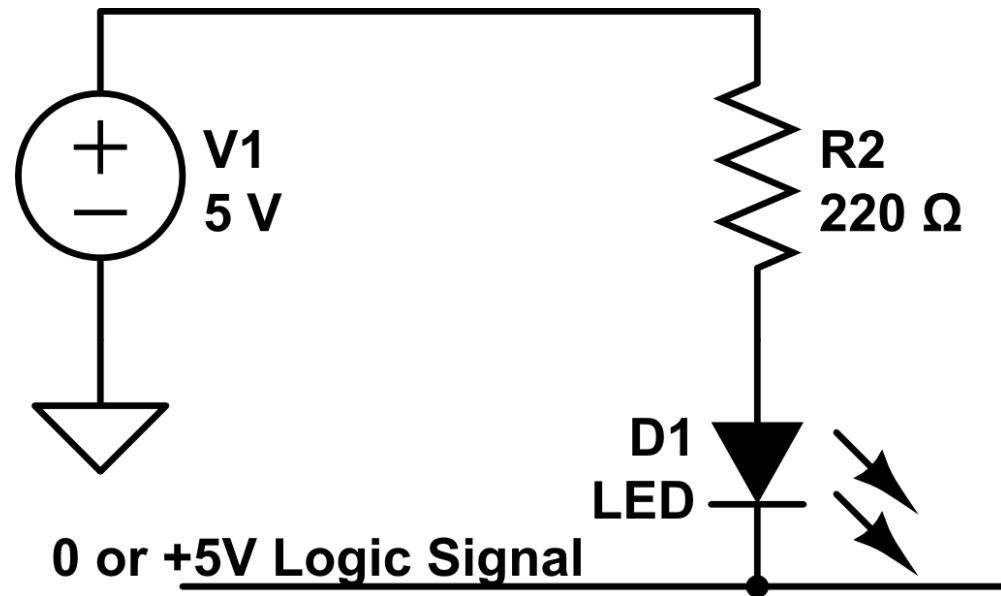- We can wire up an LED to a logic signal like this, so that when the logic level is low (0V), the LED will be ON.
- When the logic level is high (+5V), the LED will be OFF.
- But now the LED represents the opposite of the actual logic state.
How to fix??



Output LEDs

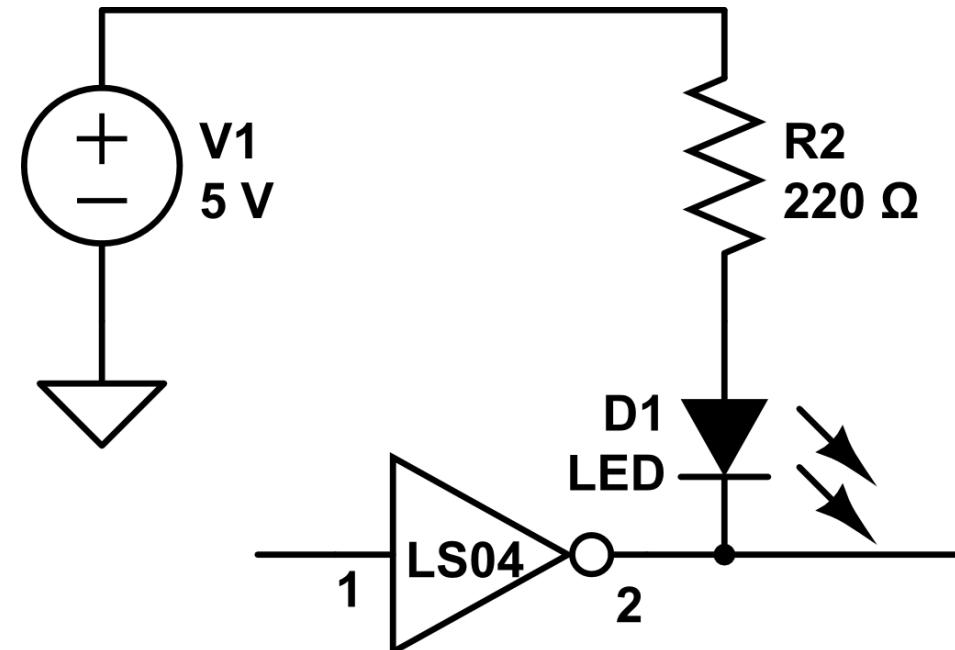- We can fix the inversion problem by driving the LED with an inverter.
- Now, if the input is LOW, the inverter output will be HIGH, and the LED will be OFF.
- If the input is HIGH the inverter output will be LOW, and the LED will be ON.





Output LEDs

- The resistor in series with the LED does two things.
- It limits the current through the LED so it won't be damaged.
- It prevents the logic output from rising too far above ground. When sinking a large current, the output voltage could increase above 2 volts.
- This will cause problems for other inputs connected to this output.

AND Gate

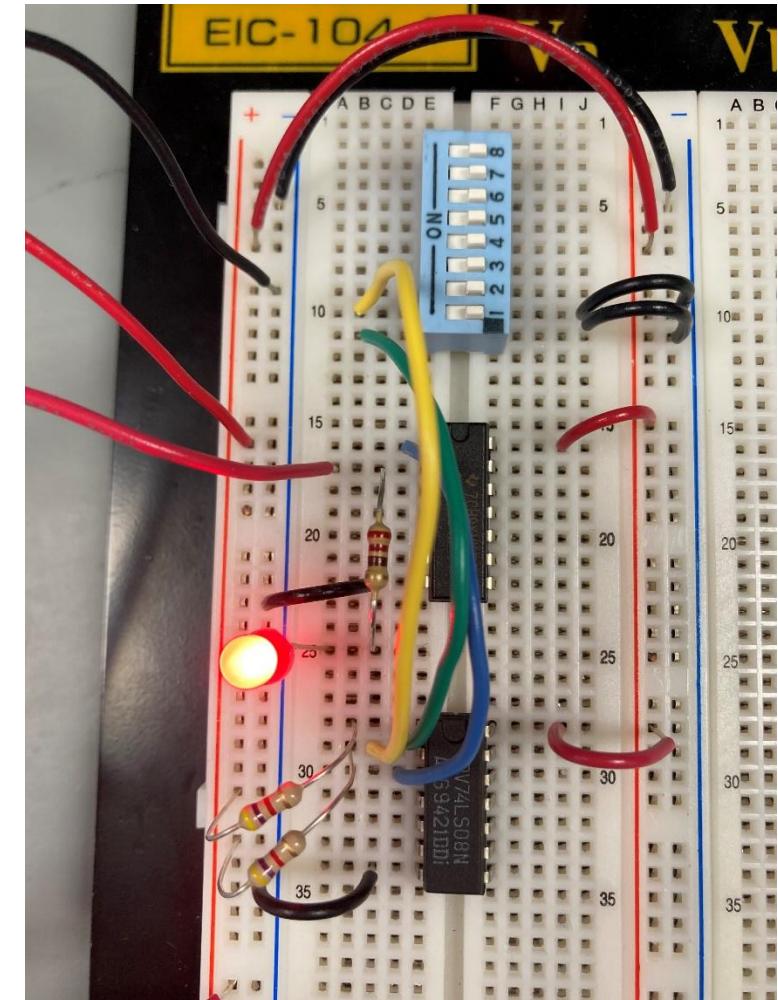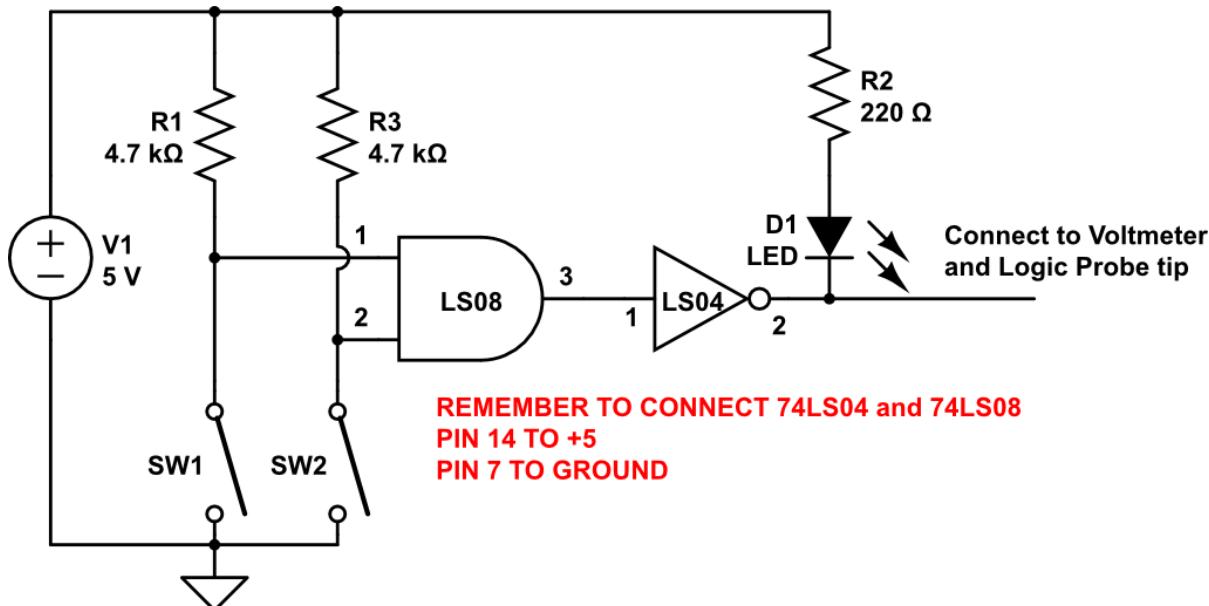- Add a 74LS08 to your breadboard, and connect power and ground.
- Connect the output of the first AND gate, pin 3, to the input of the inverter, pin 1.
- Wire a switch/resistor to both pin 1 and 2 of the AND gate.



AND Gate

- Change the switches and confirm the logical AND function.
- Both switches ON will be both AND inputs LOW, so output will be LOW, and LED will be OFF.
- Both switches OFF will be both AND inputs HIGH, so output will be HIGH, and LED will be ON.

