
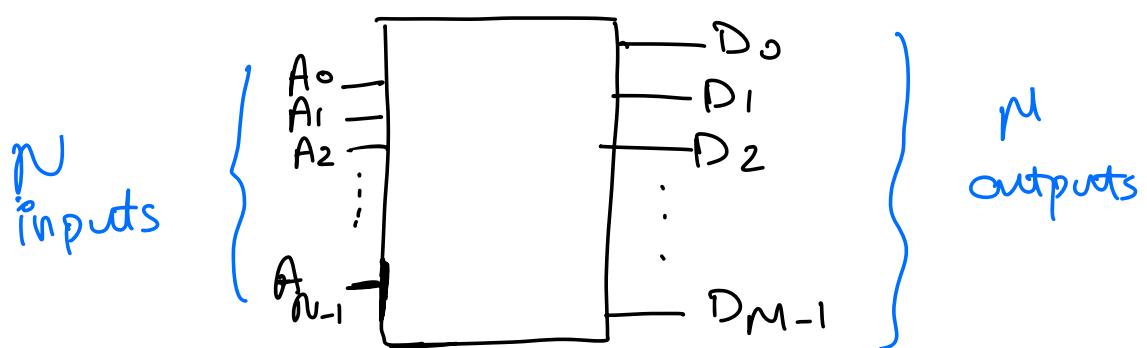


Transistors \rightarrow gates \rightarrow Specialized building blocks
 (AND
 OR
 NAND
 :
 :)
 (Decoders , encoders
 multiplexers, . . .)

N-to-M Binary Decoder:

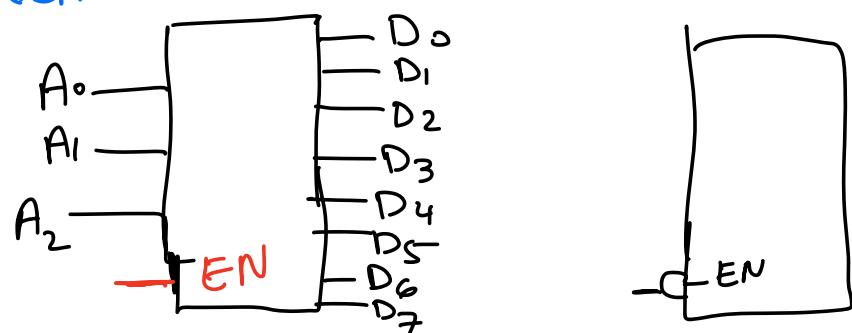

3-to-8 Decoder:




The value of the input makes the corresponding output to be true:

$$\left\{ \begin{array}{l} A_0 = 0 \\ A_1 = 0 \\ A_2 = 0 \end{array} \right. \rightarrow \left\{ \begin{array}{l} D_0 = 1 \\ D_1, \dots, D_7 = 0 \end{array} \right.$$

$$\left\{ \begin{array}{l} A_0 = 1 \\ A_1 = 0 \\ A_2 = 0 \end{array} \right. \rightarrow \left\{ \begin{array}{l} D_0 = 0, D_1 = 1, D_2, \dots, D_7 = 0 \end{array} \right.$$

A_2	A_1	A_0	EN	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
X	X	X	0	0	0	0	0	0	0	0	0
-	-	-	-	-	-	-	-	-	-	-	-
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	0	1	0
0	1	1	1	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	1	0	0	0	0	0
1	1	0	1	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

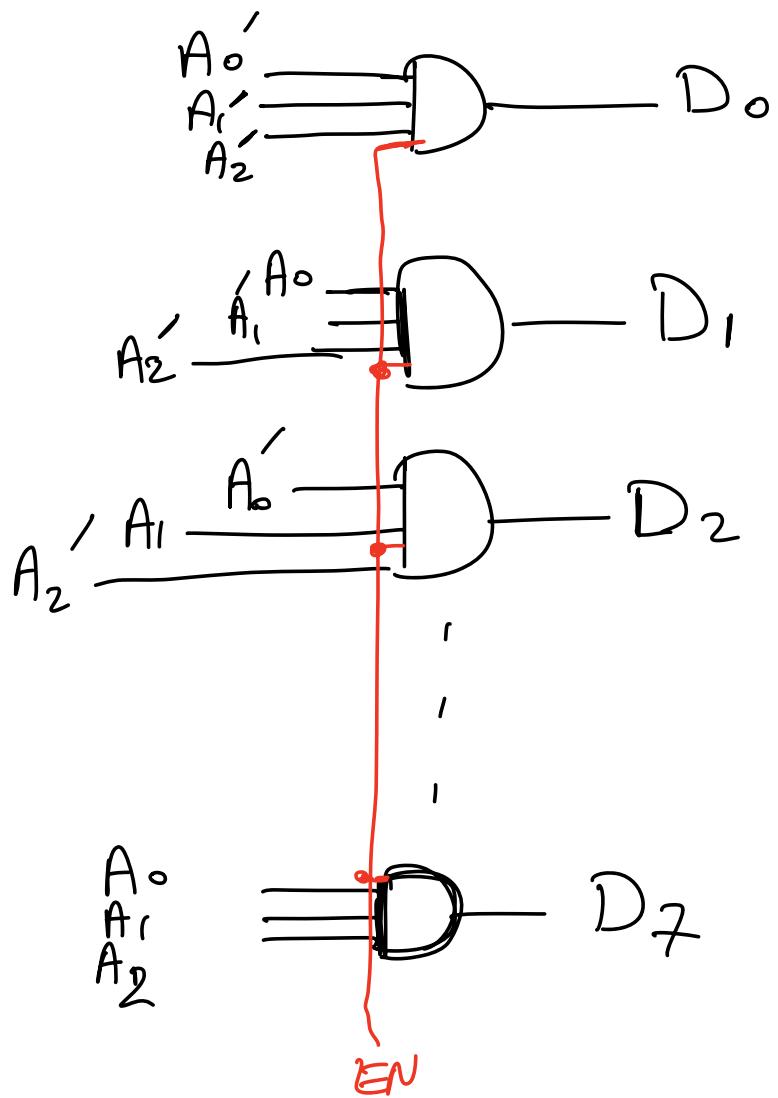

Any Boolean function can be implemented using a decoder and "OR" gates.


Example: implement F_1 and F_2

using a 3×8


A_2	A_1	A_0	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

decoder and
two OR gates.

Similar to Sum of
minterms

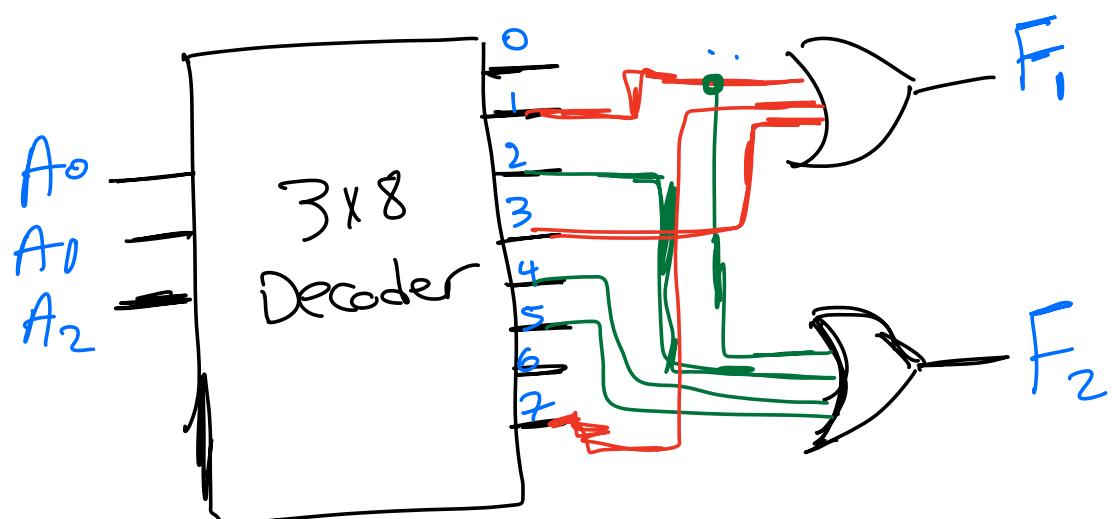


BCD - to 7-Segment decoder

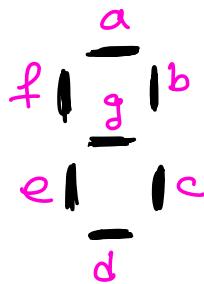


$A_3\ A_2\ A_1\ A_0$	a	b	c	d	e	f	g
0 0 0 0							0
0 0 0 1	0			0	0	0	0
0 0 1 0			0			0	
0 0 1 1						0	0
0 1 0 0	0				0		
0 1 0 1		0			0		
0 1 1 0		0			0		
0 1 1 1				0	0	0	0
1 0 0 0							
1 0 0 1				0	0		

Circuit to Control LED @:

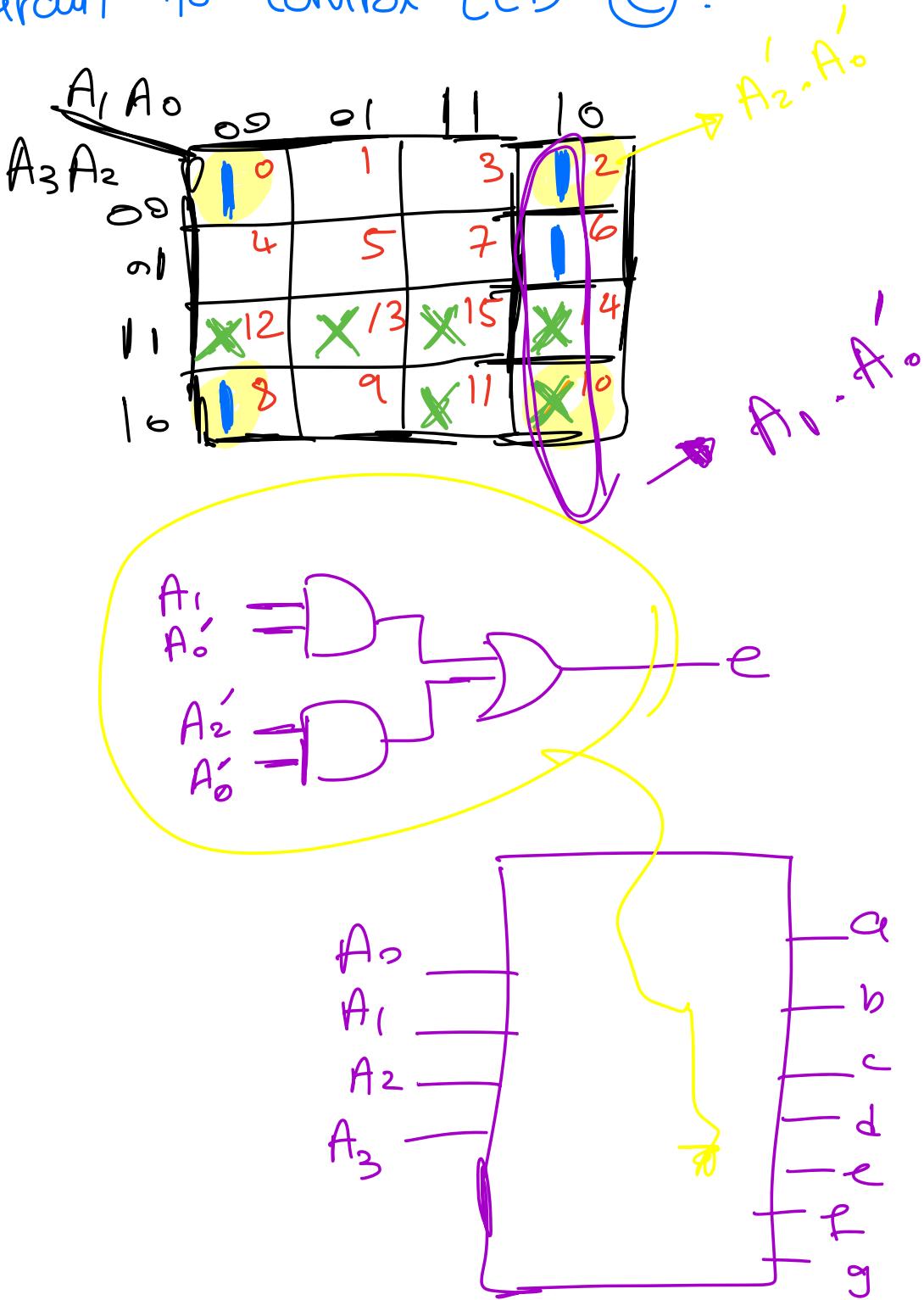

Cascading Decoders:

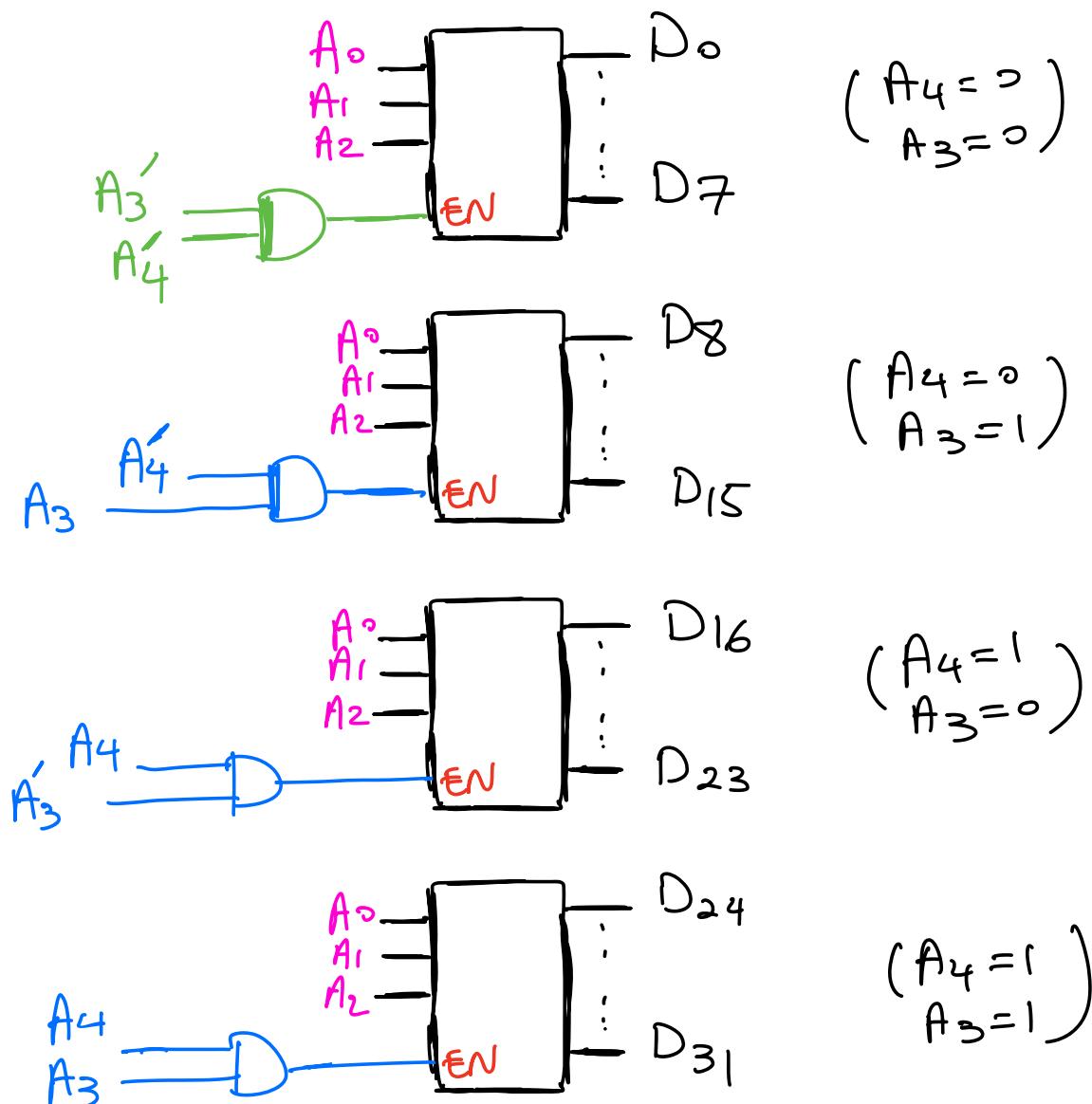
Example: Design a 5-to-32 Decoder using 3-to-8 Decoders, which have "EN" input.




$A_4 \ A_3 \ A_2 \ A_1 \ A_0$

Use the Decoder 74X138 to realize:

$$f(x, y, z) = \prod (4, 5, 7)$$

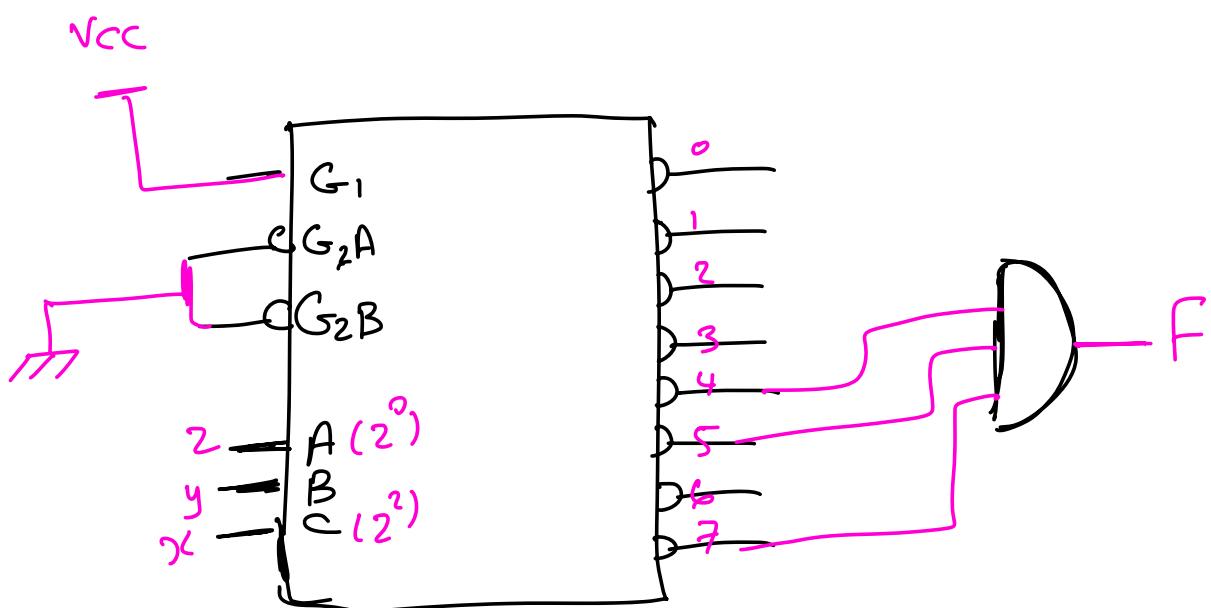


Encoders :



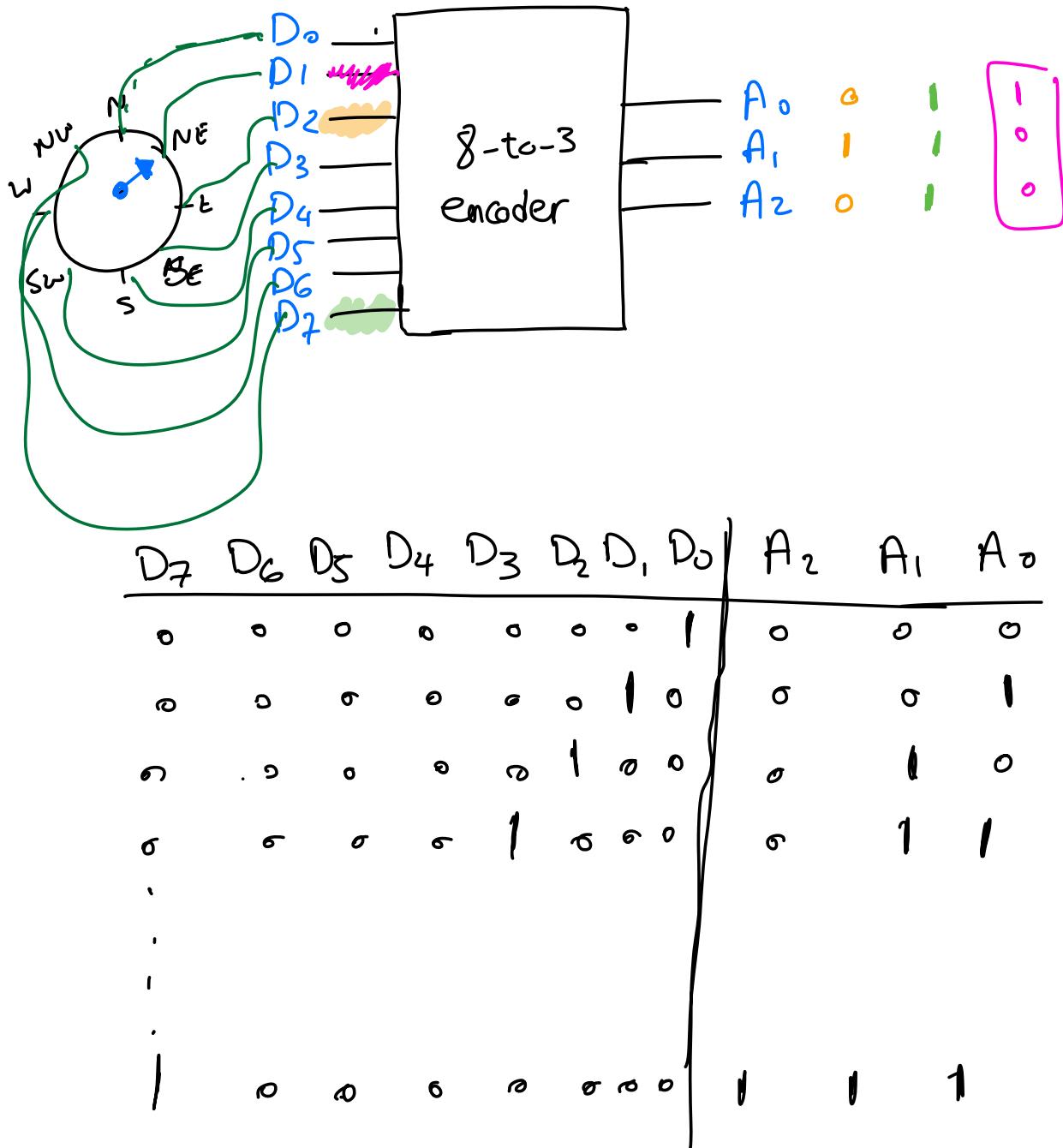


If more than one input is "1", then the encoder does not work properly.

"Priority Encoders"

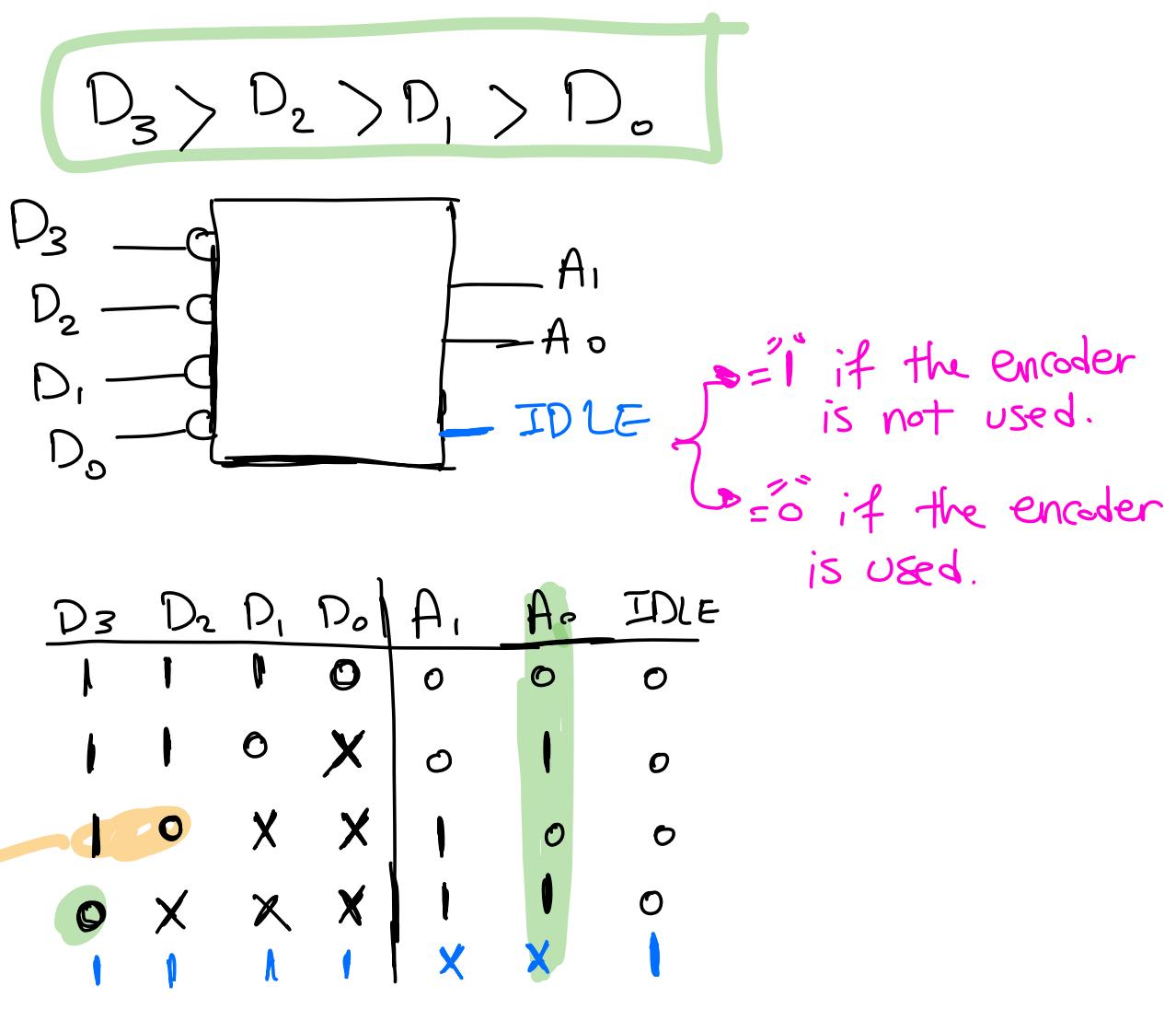Example: Design a 4-to-2 priority encoder that gives "priority" to the most significant input position:




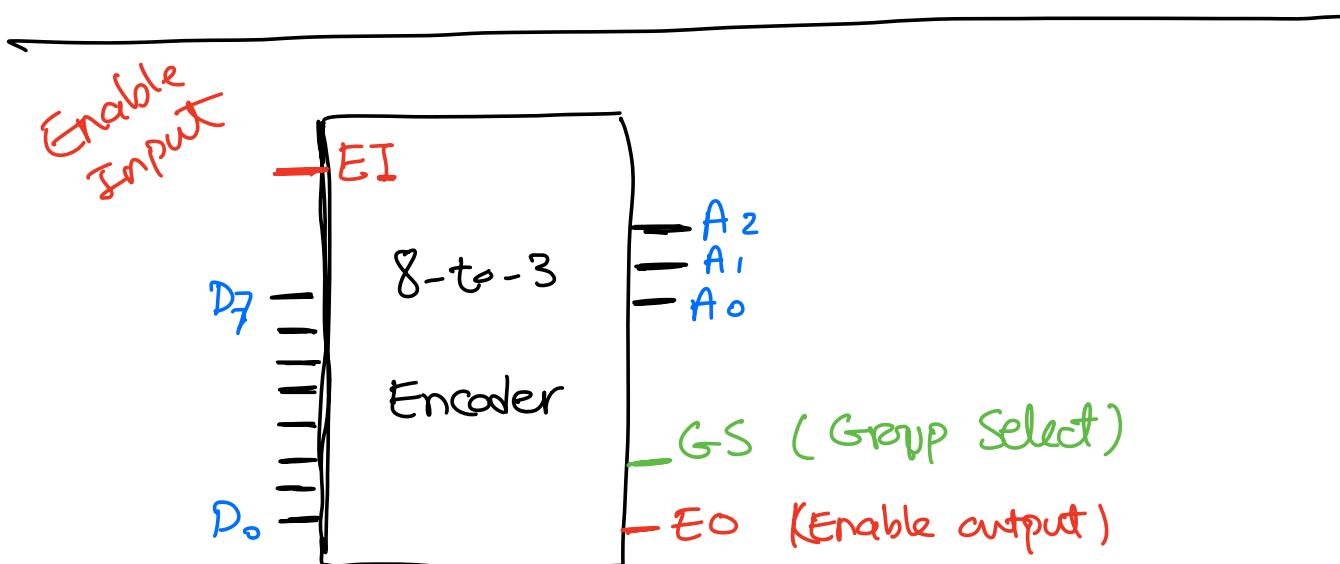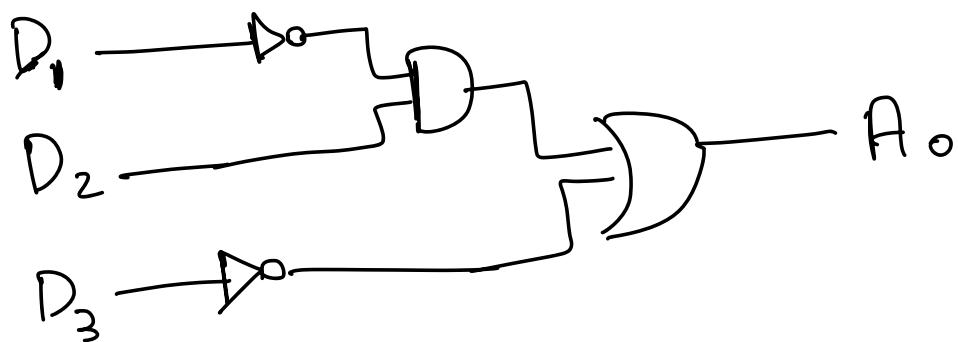
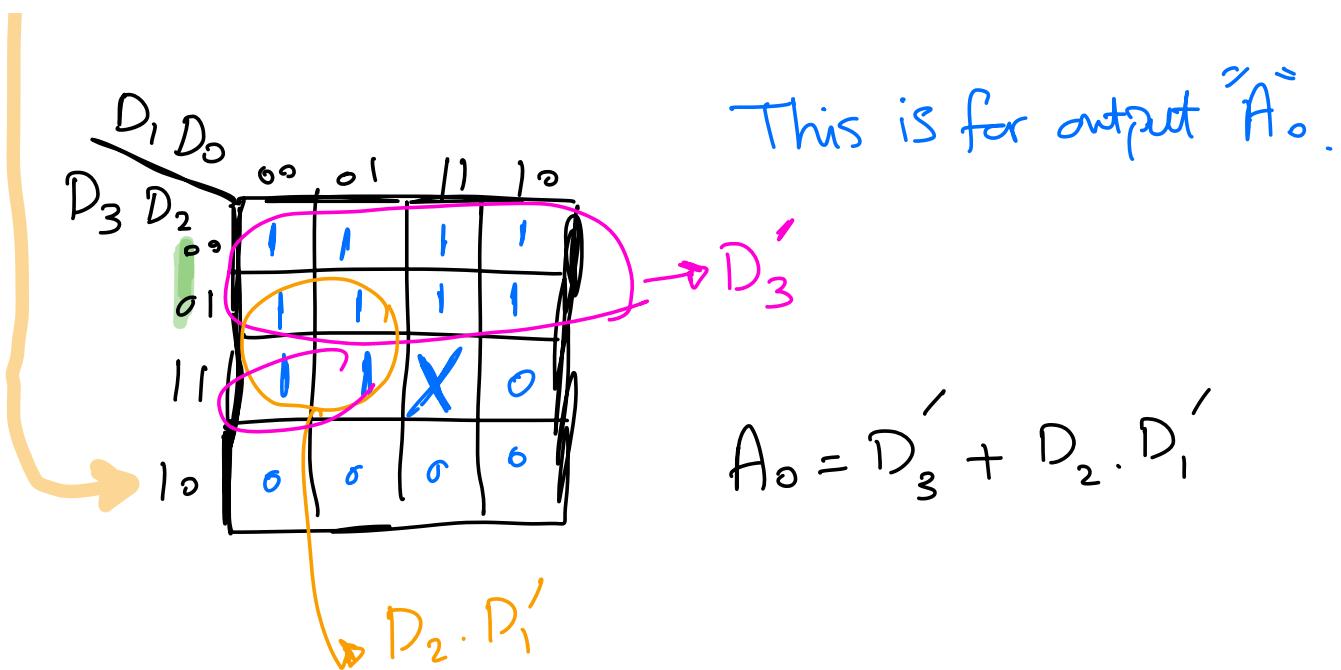


GS: } $EI = 1$
 AND
 one or more inputs are asserted. } $\Rightarrow GS = 1$


$E0 = 1$ if $EI = 1$ but there is nothing at the input

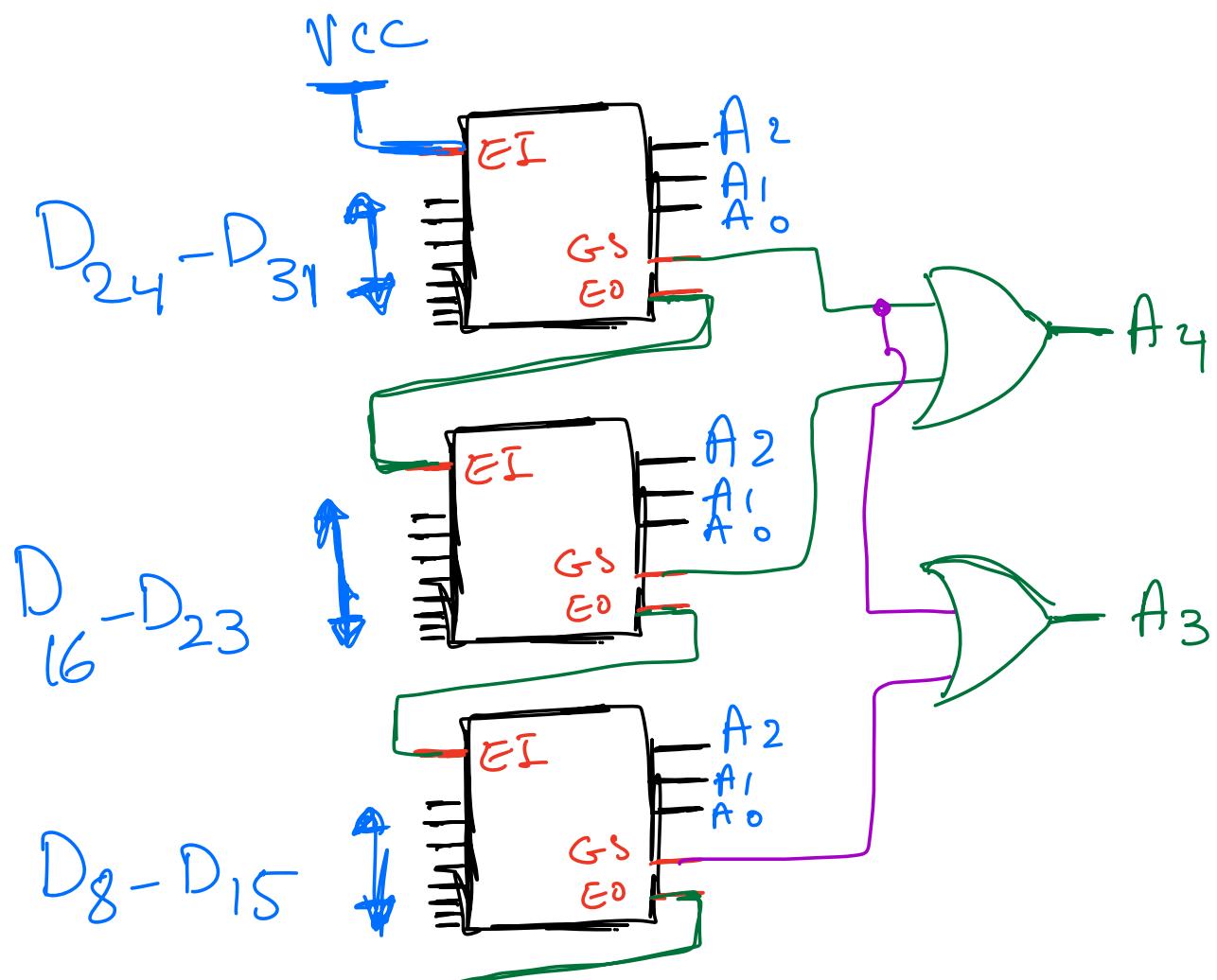build a 32-to-5 encoder using 8-to-3 encoders with EI , $E0$, and GS input/outputs.



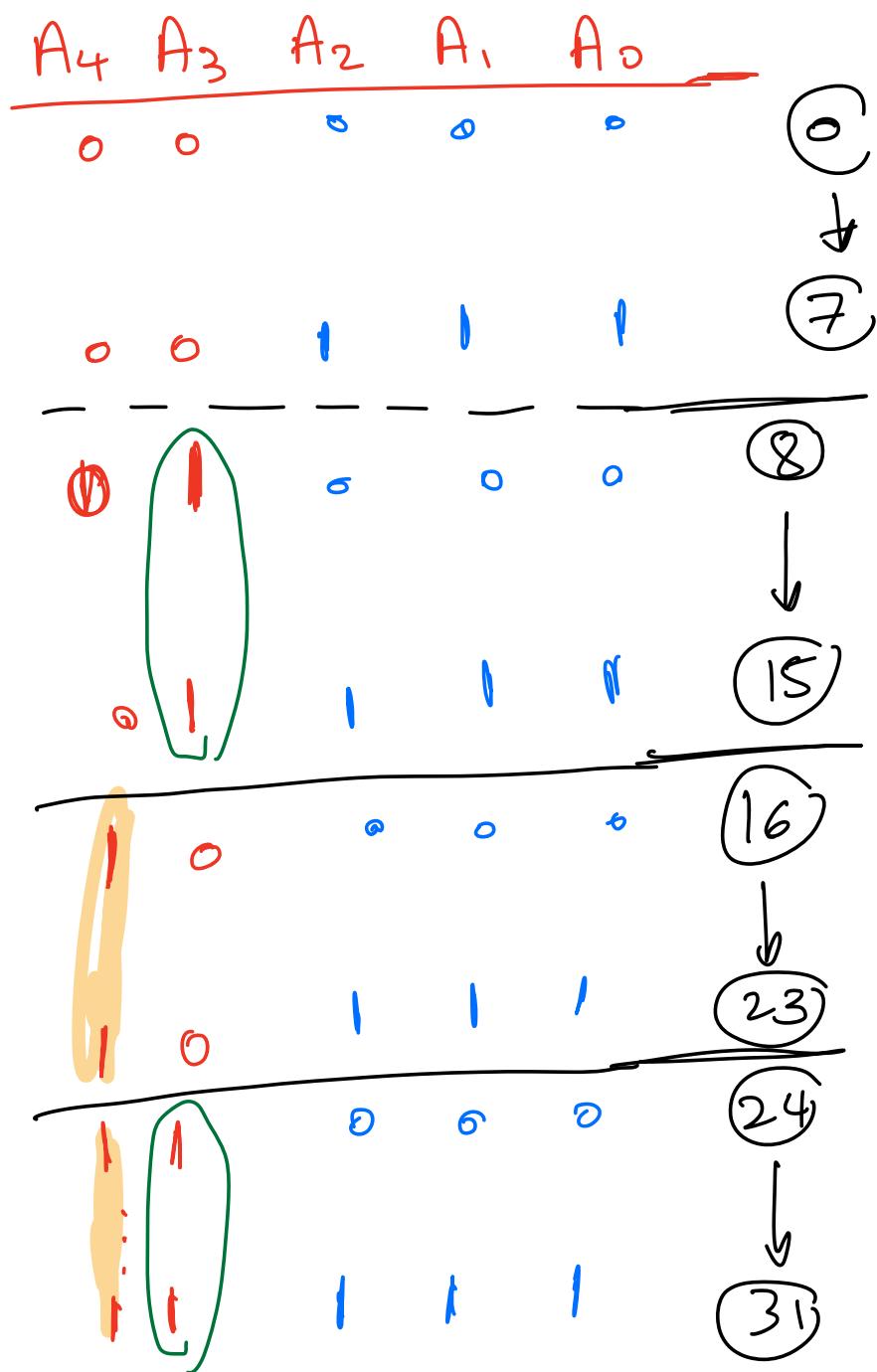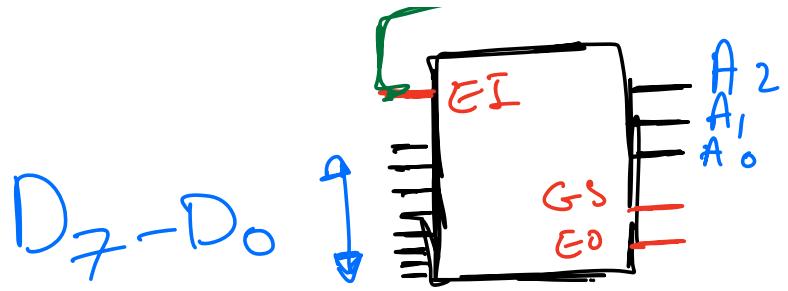


Multiplexers : (Digital Switch)

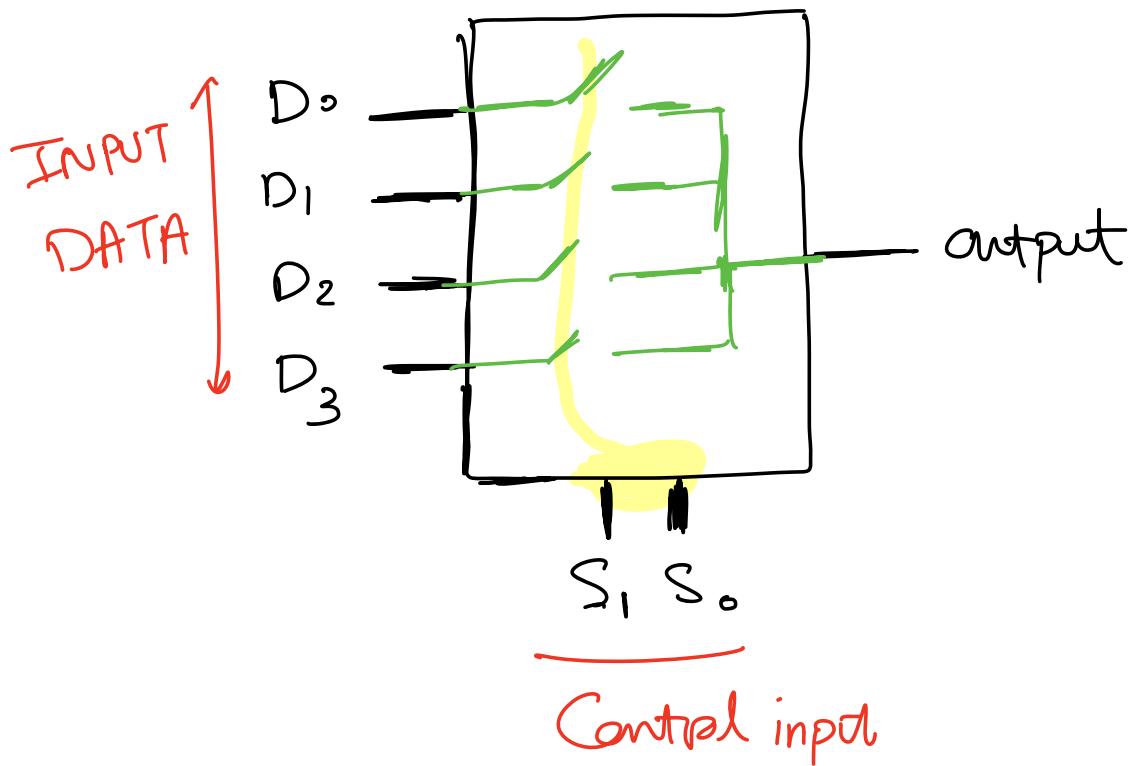


$$S_1 = 0, S_0 = 0 \Rightarrow \text{output} = D_0$$

$$S_1 = 0, S_0 = 1 \Rightarrow \text{output} = D_1$$

S ₁ , S ₀	output
0 0	D ₀
0 1	D ₁
1 0	D ₂
1 1	D ₃

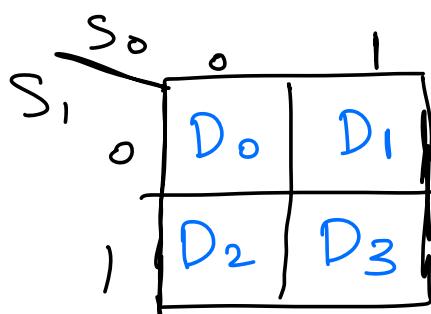


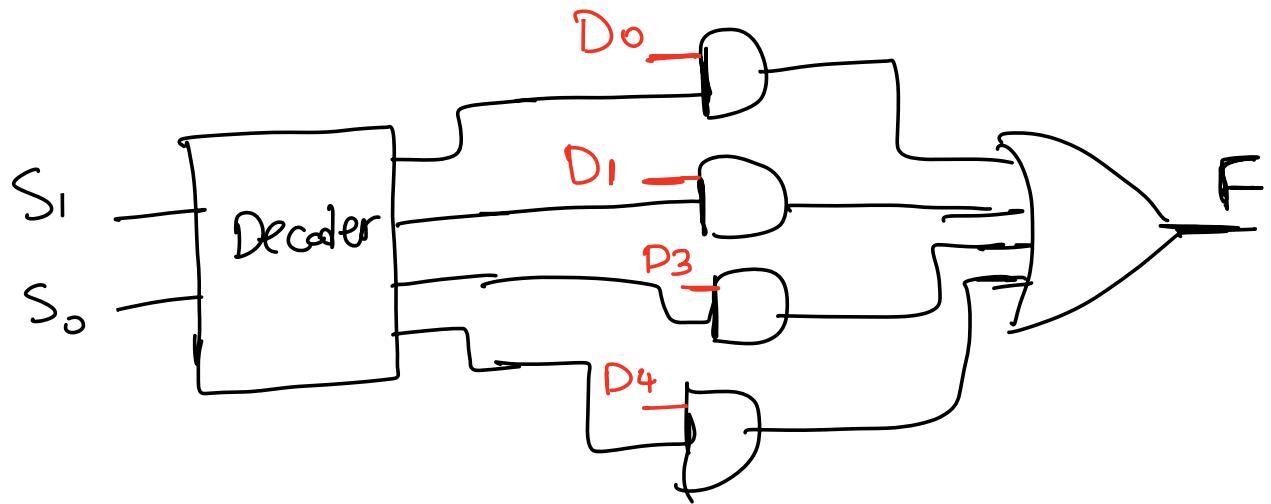


Building functions with Multiplexers:

$$f(x,y,z) = \sum(3,4,6,7)$$

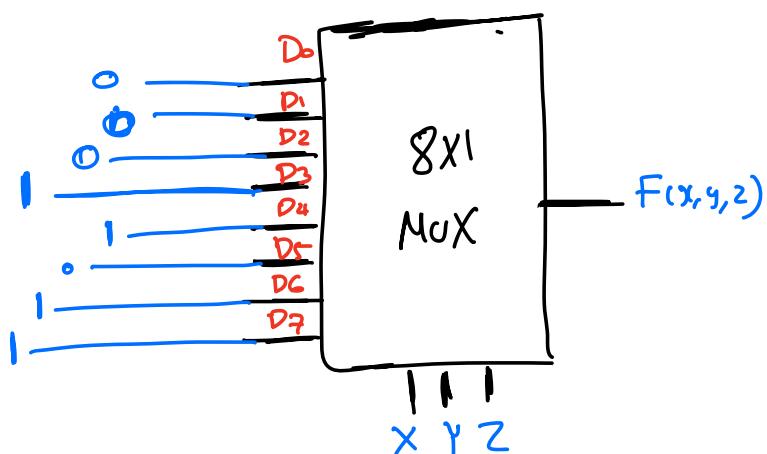Build $f(x,y,z)$ with an 8×1 multiplexer:



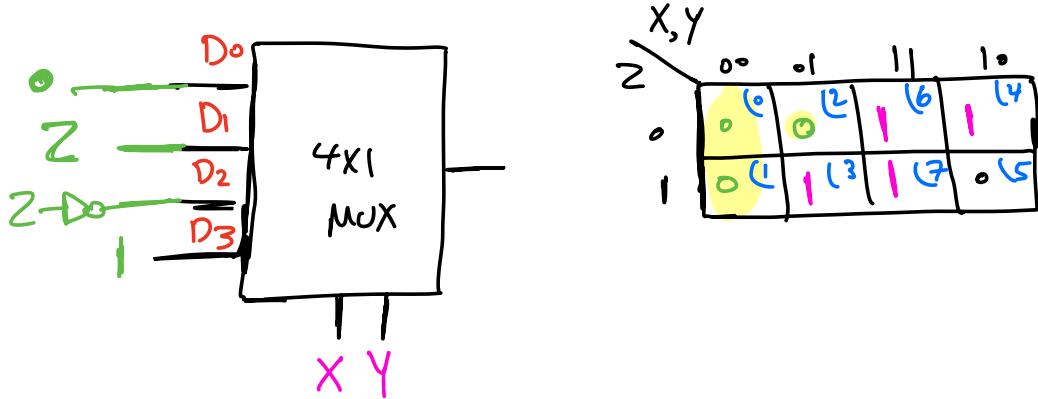
Build $F(x_1, y, z)$ using a 4×1 multiplexer:




$$\text{Example: } f(x_1, x_2, x_3, x_4) = \sum(4, 5, 6, 7, 8, 13, 14, 15)$$


a) build with an 8×1 MUX

b) build with a 4×1 MUX

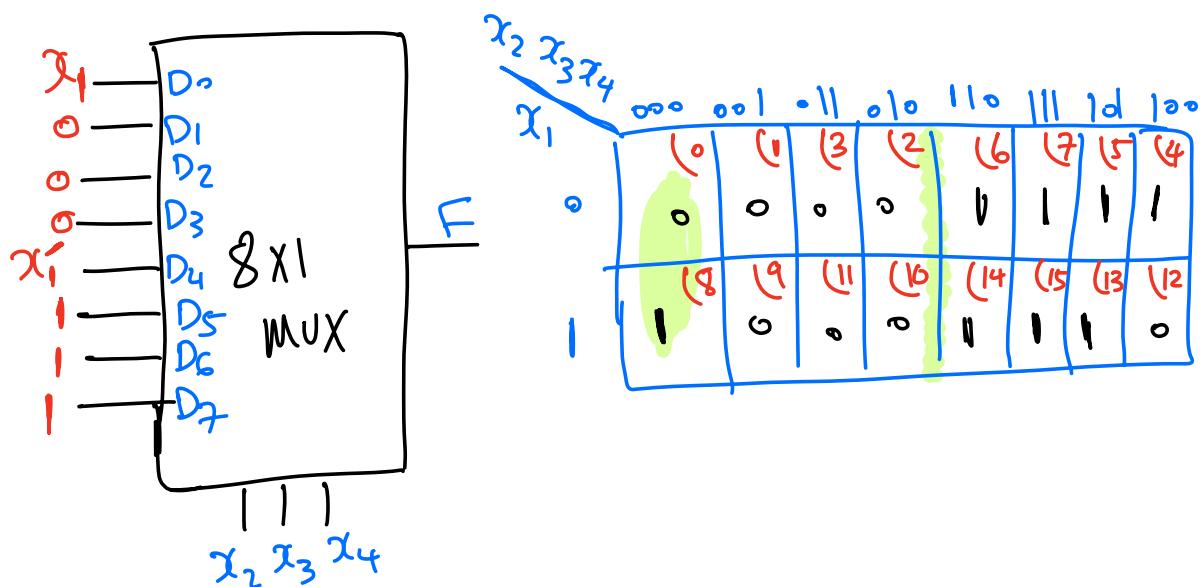

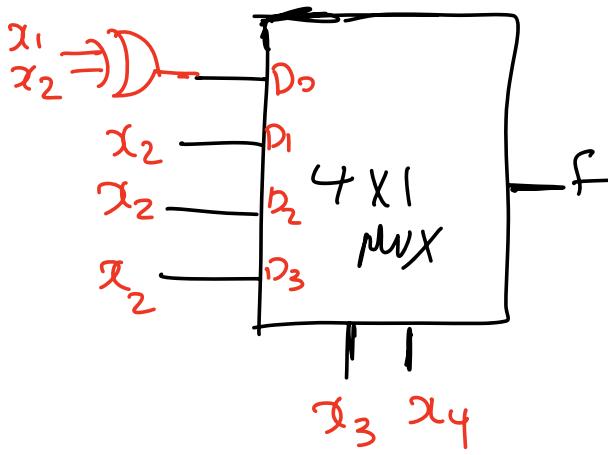


$x_3 \oplus x_4$	00	01	11	10
$x_1 \oplus x_2$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	1	1	1
10	1	0	0	0

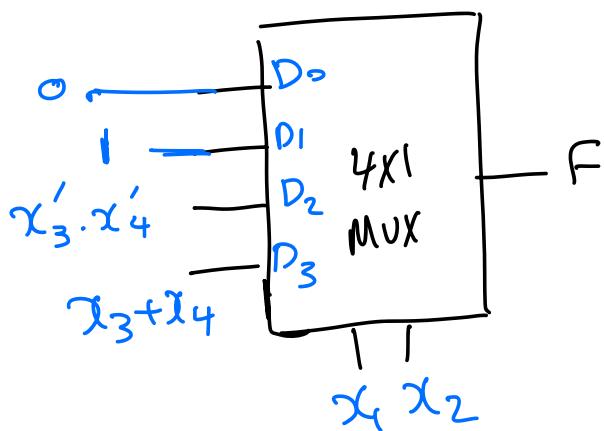

$x_3 \oplus x_4$	00	01	11	10
$x_1 \oplus x_2$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	1	1	1
10	1	0	0	0

$$(x_3 + x_4)' = \overline{x_3} \cdot \overline{x_4}$$

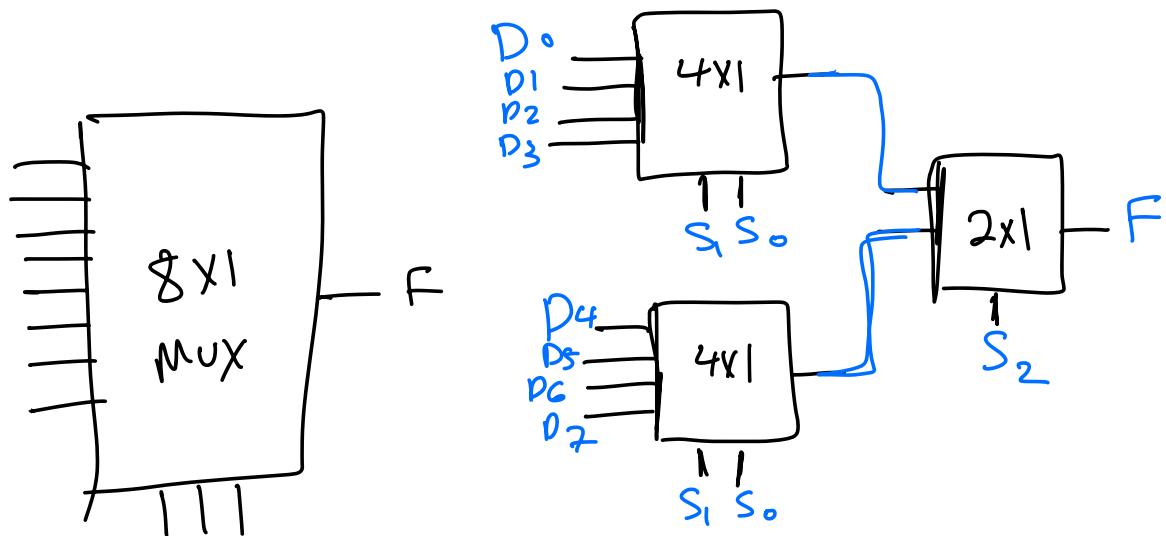
Build an 8×1 MUX using two 4×1 MUX and a 2×1 MUX



S_2	S_1	S_0
0	0	0
0	0	1
0	1	0
1	1	1


Build an 8×1 MUX using four 2×1 MUX and one 4×1 MUX.

DeMultiplexers :

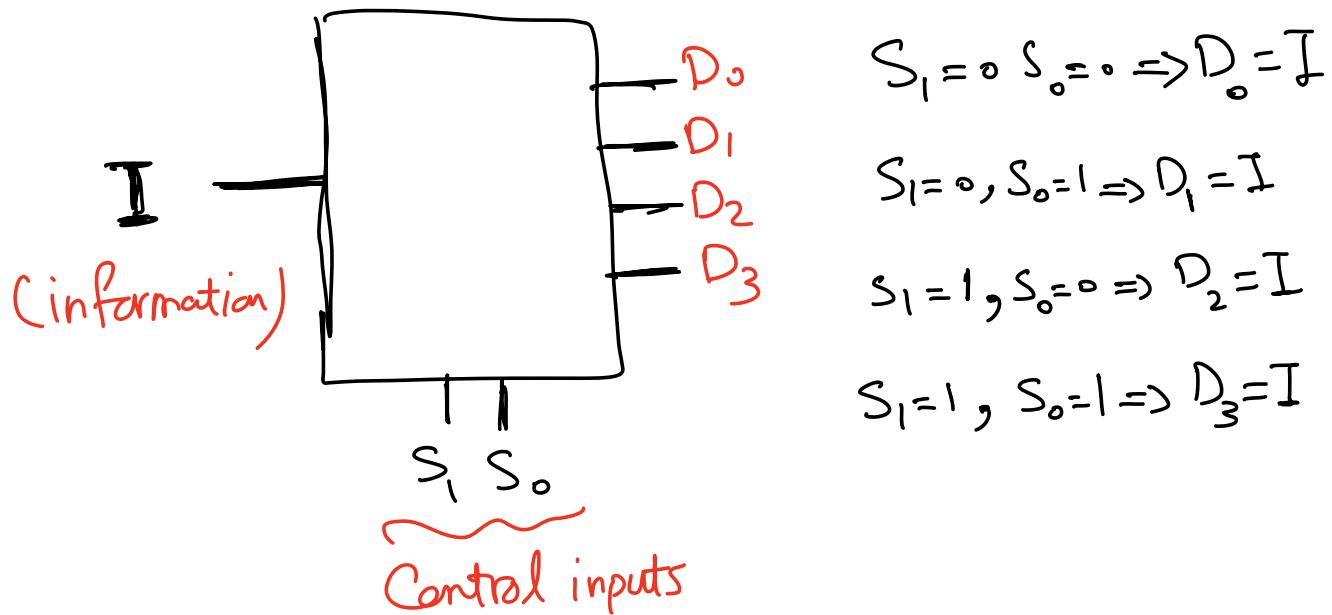


Build functions with Demultiplexers

$$f(A, B, C) = \sum(2, 4, 7)$$

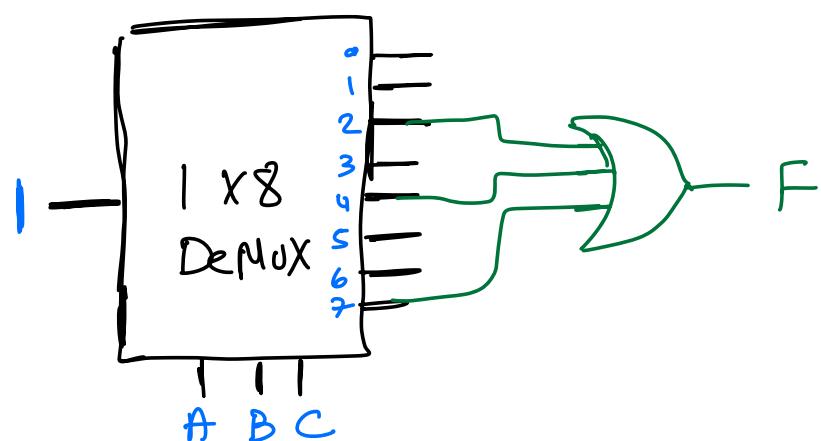

Convert a decoder to demultiplexer :

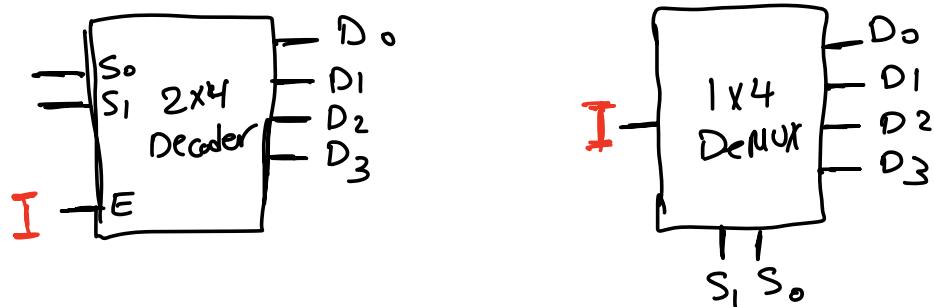


Comparators :

Equality Comparators : Compares two binary #'s, and indicates if they are equal.

Magnitude Comparators : Compares two binary #'s, and produces relational conditions: A < B, A = B, A > B



How to build equality Comparators :

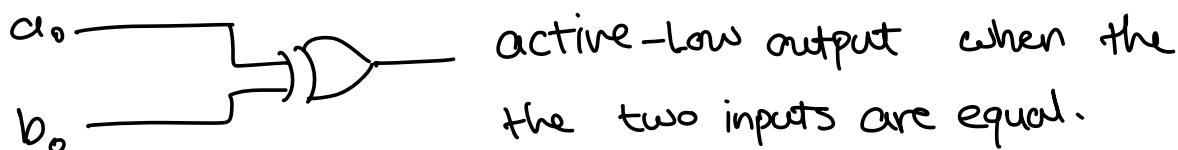


4-bit equality Comparator:

A: $a_3 \ a_2 \ a_1 \ a_0$

B: $b_3 \ b_2 \ b_1 \ b_0$

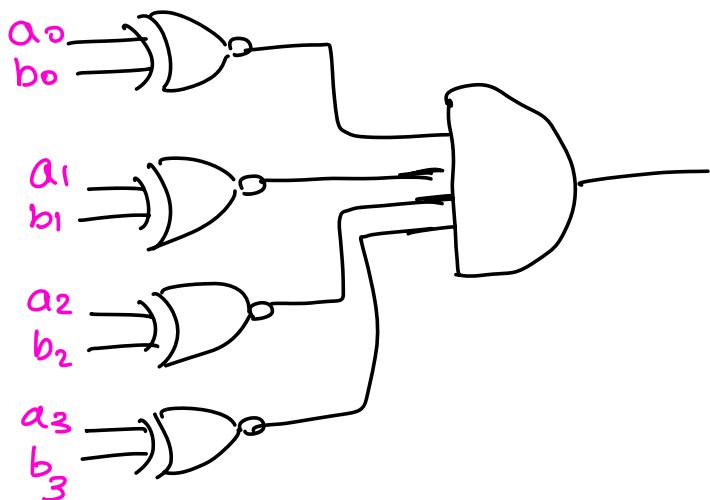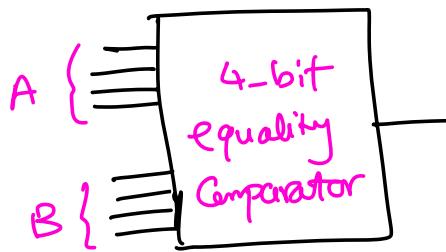

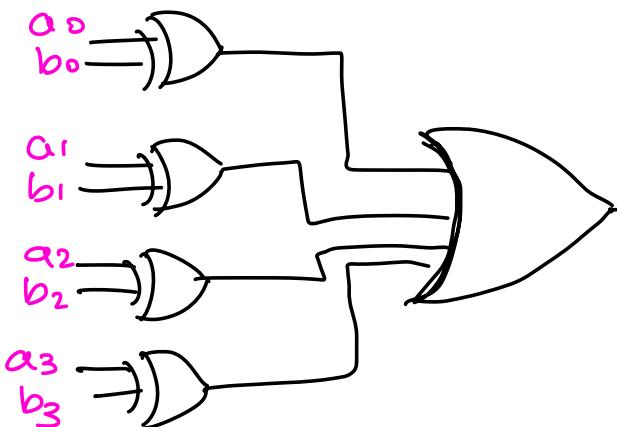active-high
output when
A and B are equal.



active-low
output when
A and B are equal.

Magnitude Comparator : $\begin{cases} A < B \\ A = B \\ A > B \end{cases}$

$$\begin{array}{l} A = (93)_{10} \\ B = (78)_{10} \end{array} \quad) \quad 9 > 7 \Rightarrow A > B$$

Algorithm:

- Start with the most Significant digit and do Comparison
- Keep Comparing digits to the right
- Once any digit of "A" is greater or less than the corresponding digit in "B", then we can make a decision.
- If all digits are equal, then both A and B are equal.

$A: a_3 \ a_2 \ a_1 \ a_0 \rightarrow B: b_3 \ b_2 \ b_1 \ b_0$

a_3, b_3	a_2, b_2	a_1, b_1	a_0, b_0
$a_3 > b_3$	X	X	X
$a_3 < b_3$	X	X	X
$a_3 = b_3$	$a_2 > b_2$	X	X
$a_3 = b_3$	$a_2 < b_2$	X	X
$a_3 = b_3$	$a_2 = b_2$	$a_1 > b_1$	X
$a_3 = b_3$	$a_2 = b_2$	$a_1 < b_1$	X
$a_3 = b_3$	$a_2 = b_2$	$a_1 = b_1$	$a_0 > b_0$
$a_3 = b_3$	$a_2 = b_2$	$a_1 = b_1$	$a_0 < b_0$
$a_3 = b_3$	$a_2 = b_2$	$a_1 = b_1$	$a_0 = b_0$

$A > B$	$A < B$	$A = B$
1	0	0
0	1	0
1	0	0
0	1	0
1	0	0
0	1	0
1	0	0
0	1	0
0	0	1

for $a_3 > b_3$ to be true : $\begin{cases} a_3 = 1 \\ b_3 = 0 \end{cases}$

$$a_3 \cdot b'_3$$

for $a_3 = b_3$ AND $a_2 > b_2$ to be true


$$(a_3 \oplus b_3) \cdot (a_2 \cdot b'_2)$$



XNOR

$$\boxed{A > B} : a_3 \cdot b'_3 + [(a_3 \oplus b_3) \cdot (a_2 \cdot b'_2)]$$

$$+ [(a_3 \oplus b_3) \cdot (a_2 \oplus b_2) \cdot (a_1 \cdot b'_1)]$$
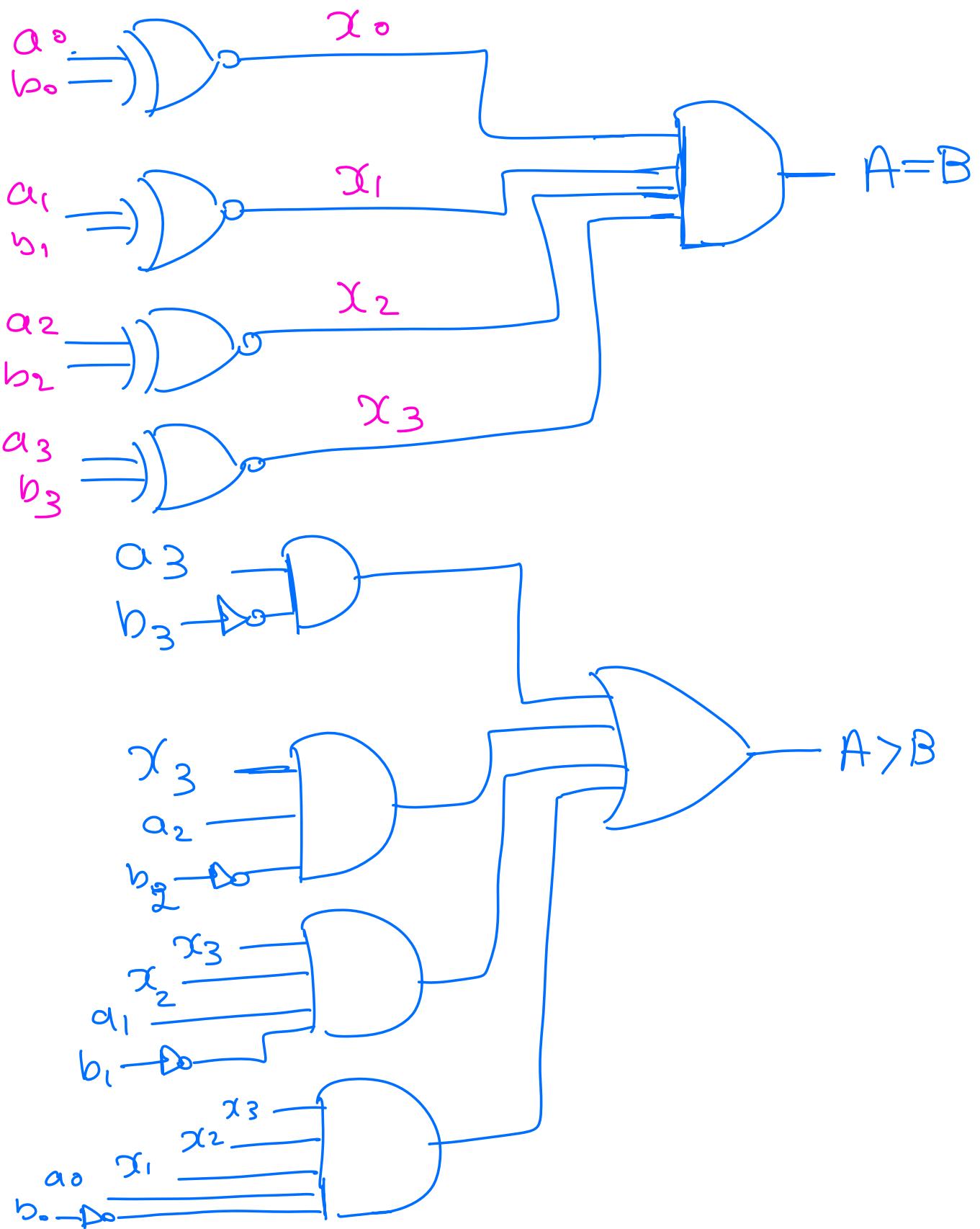
$$+ [(a_3 \oplus b_3) \cdot (a_2 \oplus b_2) \cdot (a_1 \odot b_1) \cdot (a_0 \cdot b'_0)]$$




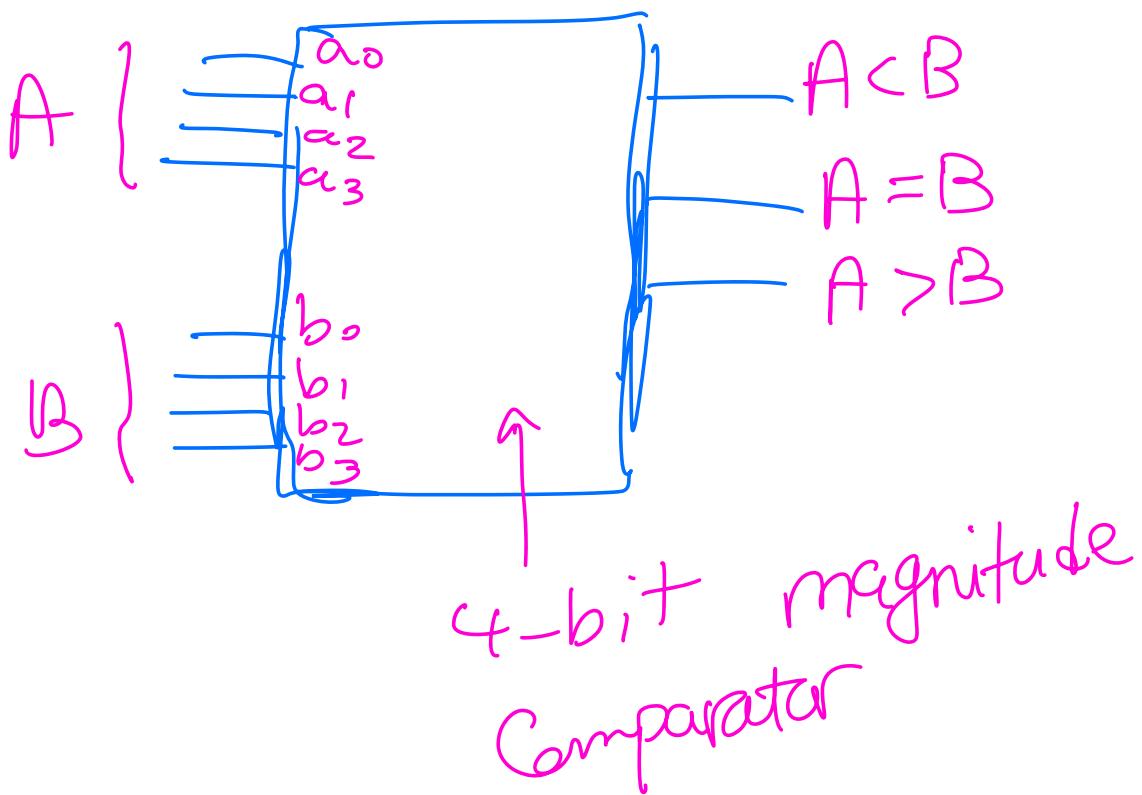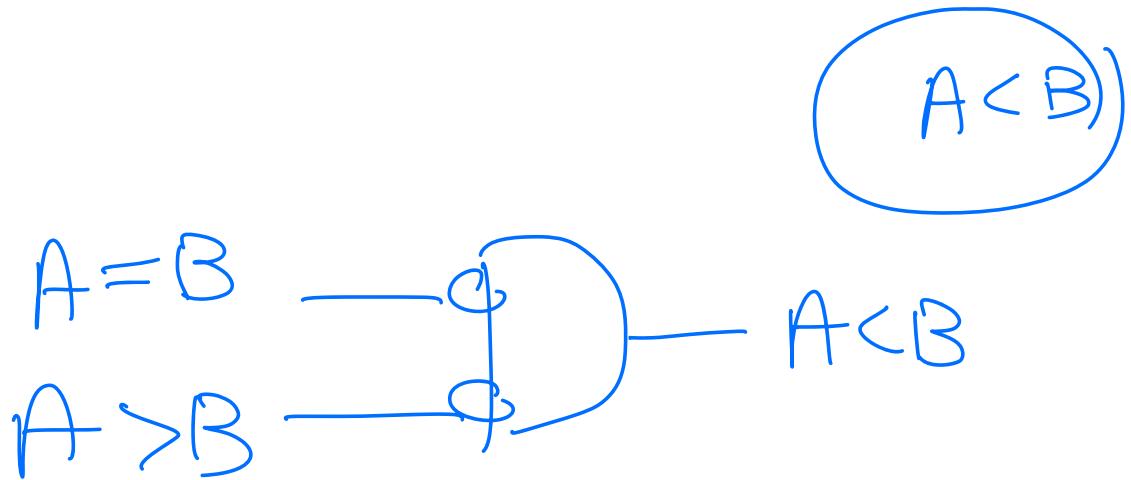


Build an 8-bit magnitude comparator
using two 4-bit Comparators

A: $a_7 \ a_8 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0$

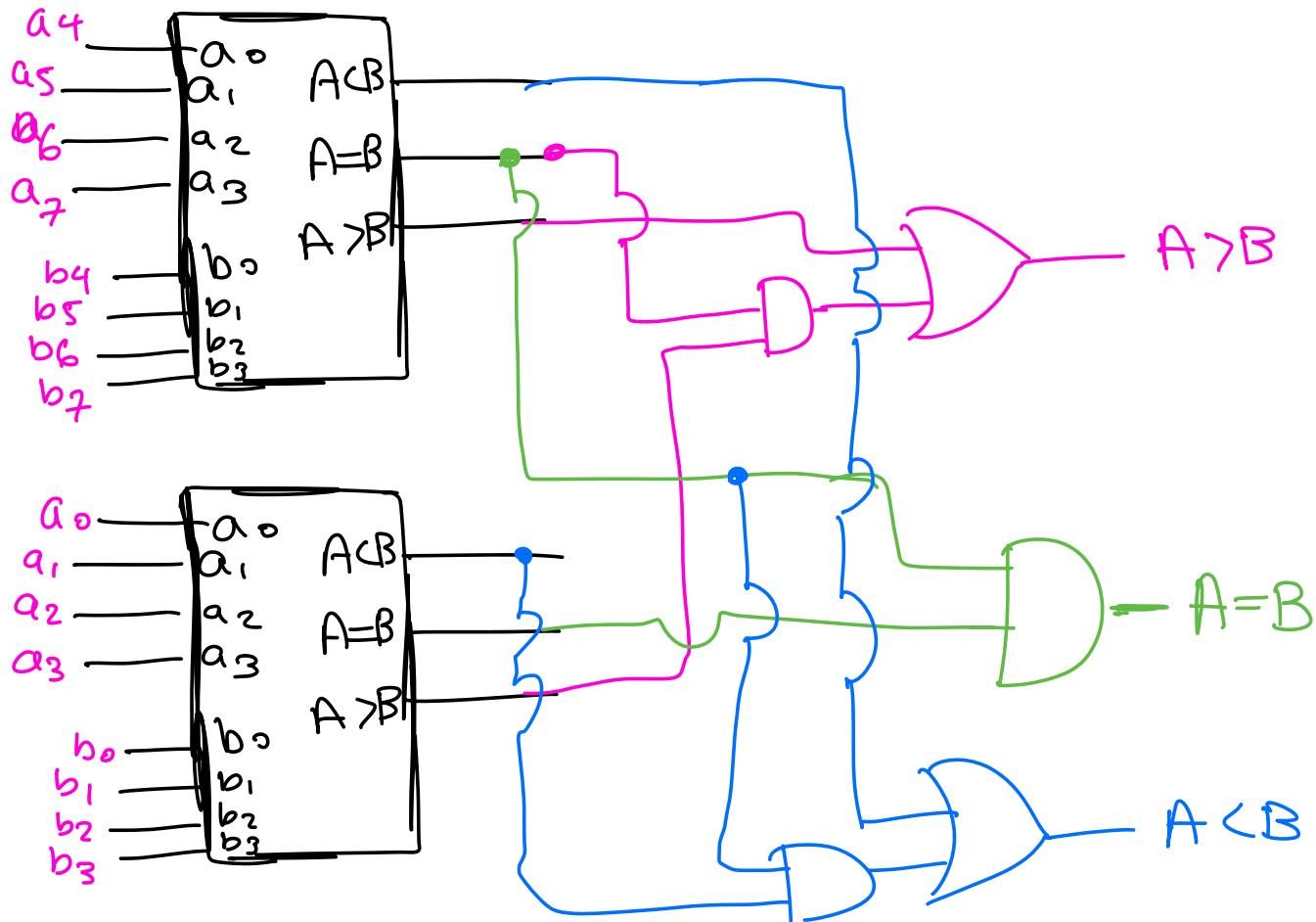B: $b_7 \ b_6 \ b_5 \ b_4 \ b_3 \ b_2 \ b_1 \ b_0$




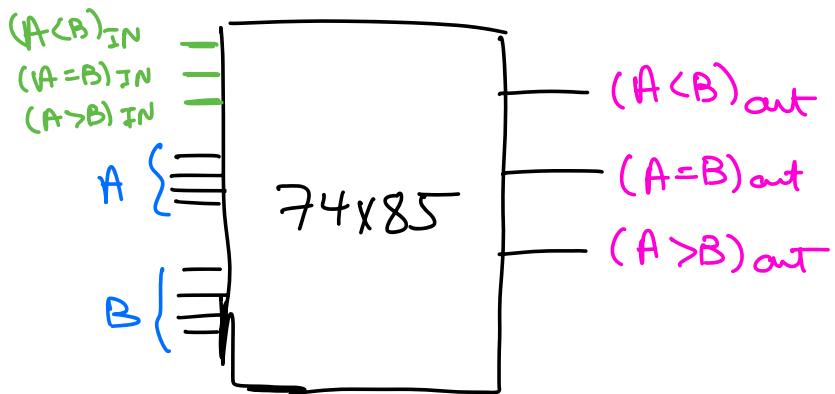

$$(A = B)_{out} = (A = B) \cdot (A = B)_{IN}$$

$$(A > B)_{out} = (A > B) + (A = B) \cdot (A > B)_{IN}$$
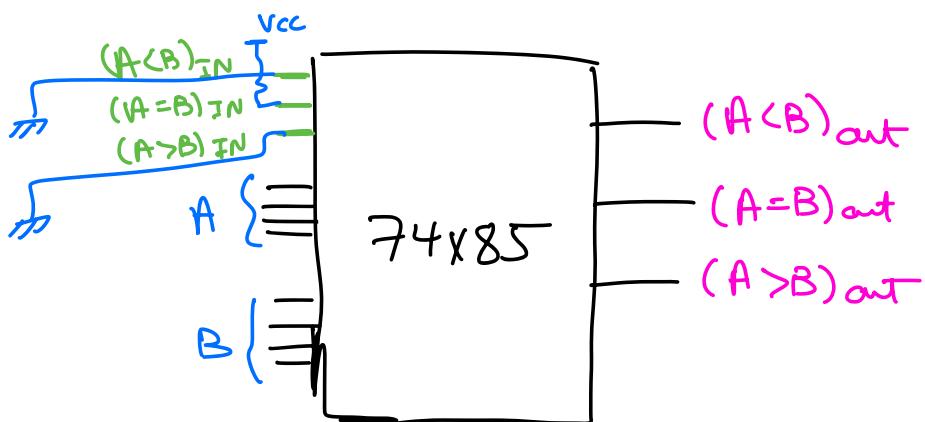
$$(A < B)_{out} = (A < B) + (A = B) \cdot (A < B)_{IN}$$




↑ How to use 74x85 as a 4-bit Comparator

Practice: Use 74x85 to build a 12-bit Comparator.

A: $a_3 \ a_2 \ a_1 \ a_0$

B: $b_3 \ b_2 \ b_1 \ b_0$

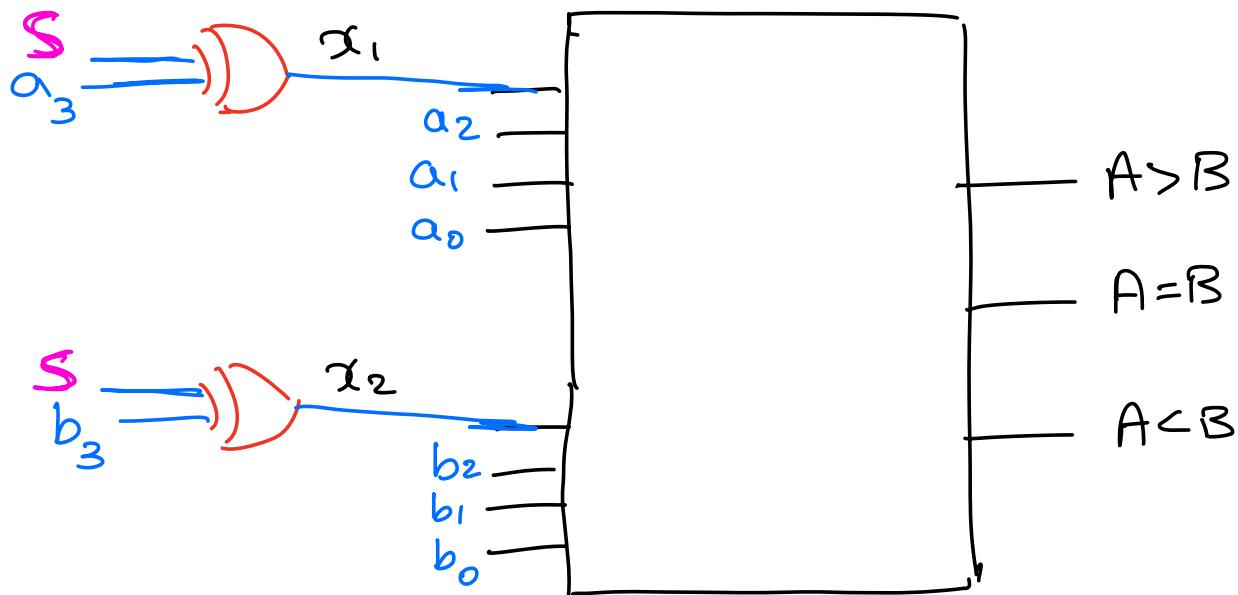

when $S=0$: unsigned numbers Comparator

when $S=1$: 2's-Complement numbers Comparator

S : Control Signal

- $S=0$ unsigned numbers
- $S=1$ 2's-Complement numbers

$$\text{when } S=0 \quad \left\{ \begin{array}{l} x_1 = a_3 \\ x_2 = b_3 \end{array} \right. \quad \begin{aligned} x_1 &= S \cdot a'_3 + S' \cdot a_3 \\ x_2 &= S \cdot b'_3 + S' \cdot b_3 \end{aligned}$$

Typical operation of magnitude Comparators
for unsigned numbers.

when $S=1$:
$$\begin{cases} x_1 = a_3' \\ x_2 = b_3'' \end{cases}$$

a_3	b_3		x_1	x_2
0	0	$A > 0, B > 0$	1	1
1	1	$A < 0, B < 0$	0	0
0	1	$A > 0, B < 0$	1	0

Example: $\begin{cases} A = 0111 \quad (+7) \\ B = 0110 \quad (+6) \end{cases} \xrightarrow{S=1} \begin{array}{|c|c|c|c|} \hline & 1 & 1 & 1 \\ \hline & 1 & 1 & 0 \\ \hline \end{array} \quad A > B$

$$(-1)x_2^3 + 1x_2^2 + 1x_2 + 1x_2^0 = -1$$

Example: $\begin{cases} A = 1111 \quad (-1) \\ B = 1110 \quad (-2) \end{cases} \xrightarrow{S=1} \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 1 \\ \hline 0 & 1 & 1 & 0 \\ \hline \end{array} \quad A > B$

Example: $\begin{cases} A = 0111 \quad (+7) \\ B = 1110 \quad (-2) \end{cases} \xrightarrow{S=1} \begin{array}{|c|c|c|c|} \hline 1 & 1 & 1 & 1 \\ \hline 0 & 1 & 1 & 0 \\ \hline \end{array} \quad A > B$