

# Basic Circuits

Dov Kruger

Department of Electrical and Computer Engineering  
Rutgers University

September 3, 2024

R

R

# Basic Electricity

- Electricity is energy moving through the medium of electrons
- Analogies
  - Ocean Wave moving
  - Hydraulic Analogy

Electricity	Units	Abbrev	Hydraulic Analogy
Circuit			Water in a closed loop of pipe
Voltage	Volt	$V$	Water pressure
Current	Amps	$A$	flow
Power	Watt	$W$	Energy/time
Resistance	Ohms	$\Omega$	Resistance to flow (friction)

R

# Hydraulic Analogy

[https://en.wikipedia.org/wiki/Hydraulic\\_analogy](https://en.wikipedia.org/wiki/Hydraulic_analogy)

Electrical Component	Hydraulic Equivalent
Battery	Pump
Resistor	Friction in Pipe
Wire	Pipe

R

- Volt (V) Energy/electron
- Current (Amps, A) number of electrons/second
- Resistance (Ohms,  $\Omega$ , R)
- Power (Watts, W)
- Energy (Joules, J)

R

# SI Prefixes

Name	Abbreviation	Value
Pico	p	$10^{-12}$
Nano	n	$10^{-9}$
Micro	$\mu$	$10^{-6}$
Milli	m	$10^{-3}$
Kilo	k	$10^3$
Mega	M	$10^6$
Giga	G	$10^9$

R

# Units with Prefixes

- $10^3 \text{ ohms} = 1 \text{ kilo-ohm}$
- $10^6 \text{ Watts} = 1 \text{ Megawatt (MW)}$
- $10^9 \text{ Volts} = 1 \text{ Gigavolt (GV)}$
- $10^{-3} \text{ Amps} = 1 \text{ milliAmp (mA)}$
- $10^{-6} \text{ meters} = 1 \mu\text{m} = 1 \text{ micron}$
- $10^{-9} \text{ seconds} = 1 \text{ nanosecond} = 1 \text{ ns}$
- $10^{-12} \text{ seconds} = 1 \text{ picosecond} = 1 \text{ ps}$

R

# Basic DC Circuit Variables

- Voltage: Analogous to water pressure
  - The force that moves electrons around the circuit
  - Energy per electron
- current
  - The number of electrons flowing per unit time
- Resistance
  - The resistance to the flow of electricity
  - Analogous to friction
  - Converts some current to waste heat

Ohm's Law:  $V = I \cdot R$

R

# Analog Circuits

- Analog means a point in the circuit can have any voltage
- It takes time to change voltage because of capacitance

R

- Digital is a simplified abstraction of Circuits
- Fixed voltage levels (can be multiple levels)
- For this course we consider only 2 levels
- High ( $V_{cc}$ ) and low ( $0V$ )
- High (1) and Low (0)
- Any extraneous signal (noise) can be ignored
- Theoretically instantaneous

# Practical Digital Circuits


- Digital is a simplified abstraction of Circuits
- We consider only high ( $V_{cc}$ ) or low (0V)
- High (1) and Low (0)
- Any extraneous signal (noise) can be ignored
- Theoretically instantaneous

R
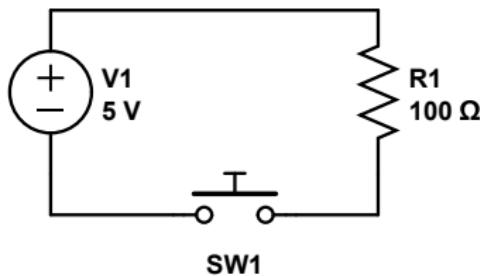
# Correct Terminology: Forget "on" and "off"

Turn a light "on"


- Closed switch (both sides same voltage)
- Open switch (both sides can be different)
- A switch creates a path for electricity



**R**
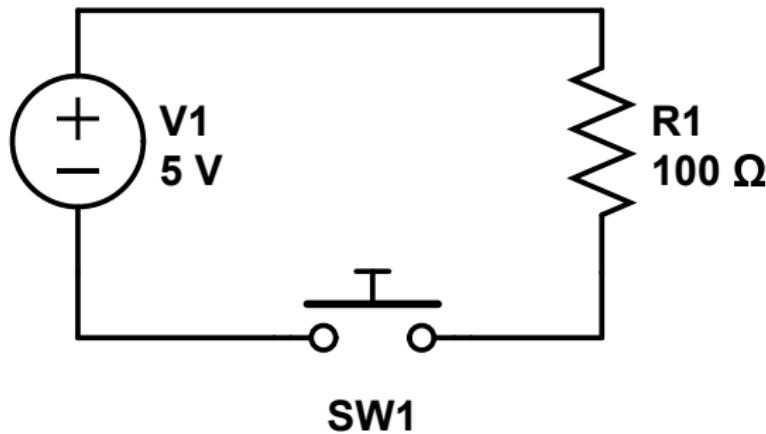
# Simple Circuit

- Every circuit needs three basic components:
  1. A voltage source
  2. A simple closed path
  3. A load
- The circuit must be closed for current to flow.



**R**

## Example: Broken Circuit


- If the path is not closed the circuit is broken
- Without a closed path, electricity cannot flow.



**R**
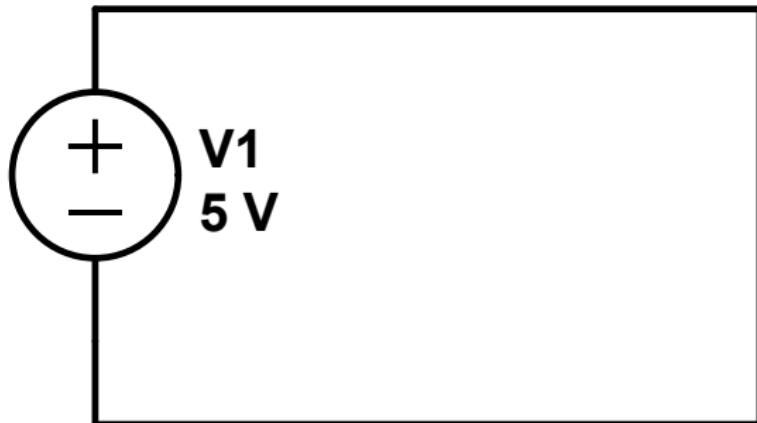
## Example: Short Circuit

- A short circuit happens when the load is bypassed.
- Without the load, too much electricity flows.
- This can cause overheating and damage to the circuit.



R

## Example: No Voltage Source


- Without a voltage source, there is no reason for electricity to flow.
- The circuit remains inactive without a power supply.



R
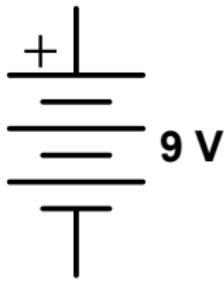
# Battery

- Converts chemical energy to electrical energy
- Provides a constant voltage source
- Essential for powering circuits



Actual Device

Schematic Symbol

R

# Resistor

- A resistor restricts current
- Analogous to a pipe with friction
- Ohm's law:  $V = IR$
- Power:  $P = VI = I^2R$
- If you exceed the power rating, resistor can overheat




Actual Device

Schematic Symbol


R
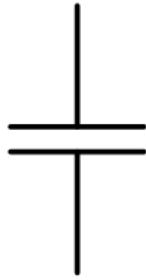
# Capacitor

- Stores electrical energy as an electric field
- Used to smooth out voltage in circuits
- Capacitance measured in Farads (F)
- Analogous to a tire, too much pressure can blow it up!
- $E = \frac{1}{2}CV^2$



Schematic Symbol

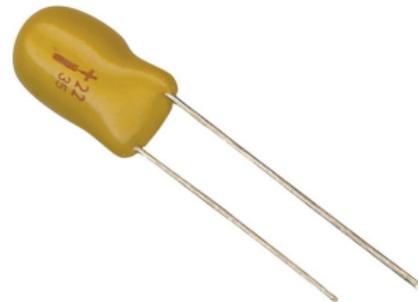


Actual Device

R
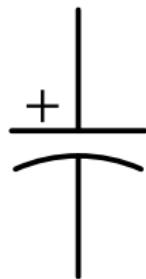
# Electrolytic Capacitor

- Polarized Capacitor
- Can blow up if voltage is applied in reverse
- Higher capacitance values than ceramic capacitors
- Commonly used in power supply filtering



Schematic Symbol



Actual Device

R


# Inductor

- Stores energy in a magnetic field
- Resists changes in current
- Commonly used in filters and power supplies
- Inductance measured in Henries (H)
- $E = \frac{1}{2}LI^2$




Schematic Symbol

**R**

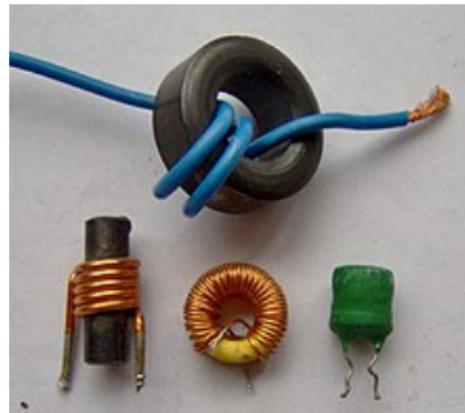

Actual Device

# Voltage Source

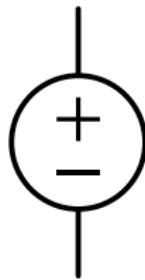

Schematic Symbol

Actual Device

R

# SPST Switch

- Single Pole Single Throw (SPST)
- Simple on-off switch
- Connects or disconnects a single path



Schematic Symbol



Actual Device

R

# SPDT Switch

- Single Pole Double Throw (SPDT)
- Directs current to one of two paths
- Used for selecting between two circuits



Schematic Symbol




Actual Device

R
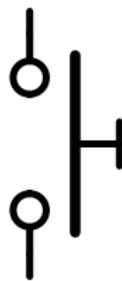
# Momentary On Pushbutton

- 4 pins
- When pressed, the wires are connected
- Each side is connected all the time
- The two sides are connected when the button is pressed



Schematic Symbol



Actual Device

R

# Momentary Off Pushbutton

Schematic Symbol

Actual Device

R

# Fuse

- A fuse is a safety device
- Protects electrical circuits from excessive current
- Thin wire or strip that melts when too much current flows through it
- The weakest link, breaking before the rest of the circuit



**R**


Schematic Symbol



Actual Device
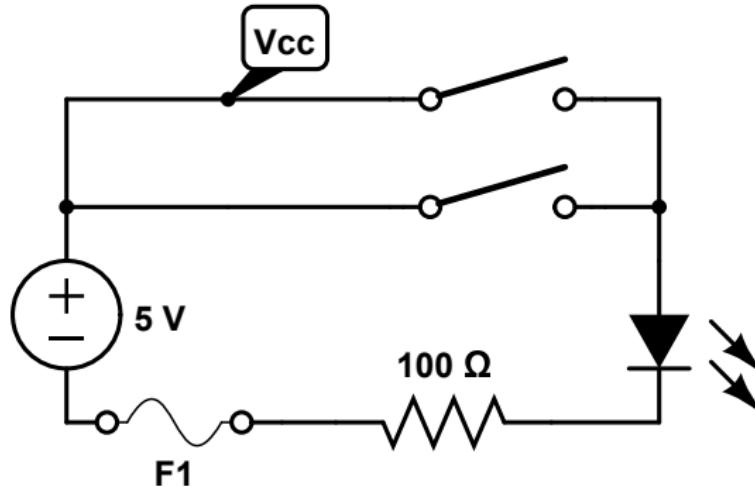
# Using a Fuse

- Fuses must be in Series
- Should burn out before the rest of the circuit




R

# Diode

- A diode allows current to flow in one direction
- Practically equivalent to a small resistor forward and large in reverse
- Has a low forward voltage drop and high reverse resistance
- Arrow is in the direction of positive current



Schematic Symbol

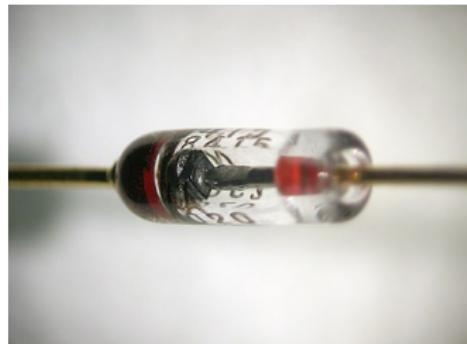


Actual Device


R
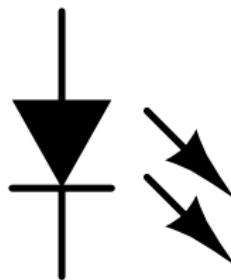
# LED

- An LED is a special kind of diode
- Atomically tuned to emit light of one specific color
- Like any diode, current must flow forward
- Extremely little waste heat, highly efficient



Schematic Symbol

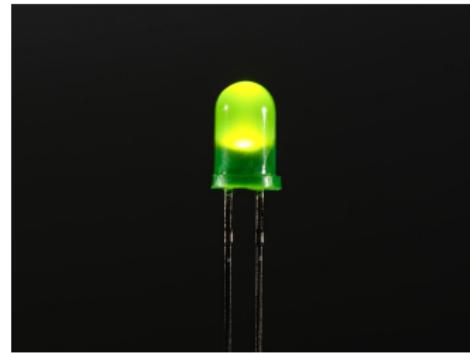

Actual Device

R


# Conductors, Insulators, and Semiconductors

- A conductor (metals) has low resistance
- Outer electrons easily raised into conduction Background
- Insulators have very high resistance
- Very difficult to break electrons out of their orbits
- Semiconductors have medium resistance
- Extremely pure materials, doped with tiny amounts of other materials
- Silicon: 1 part per trillion (ppt) pure
- Doped with Boron and Phosphor (parts per billion (ppb))

R

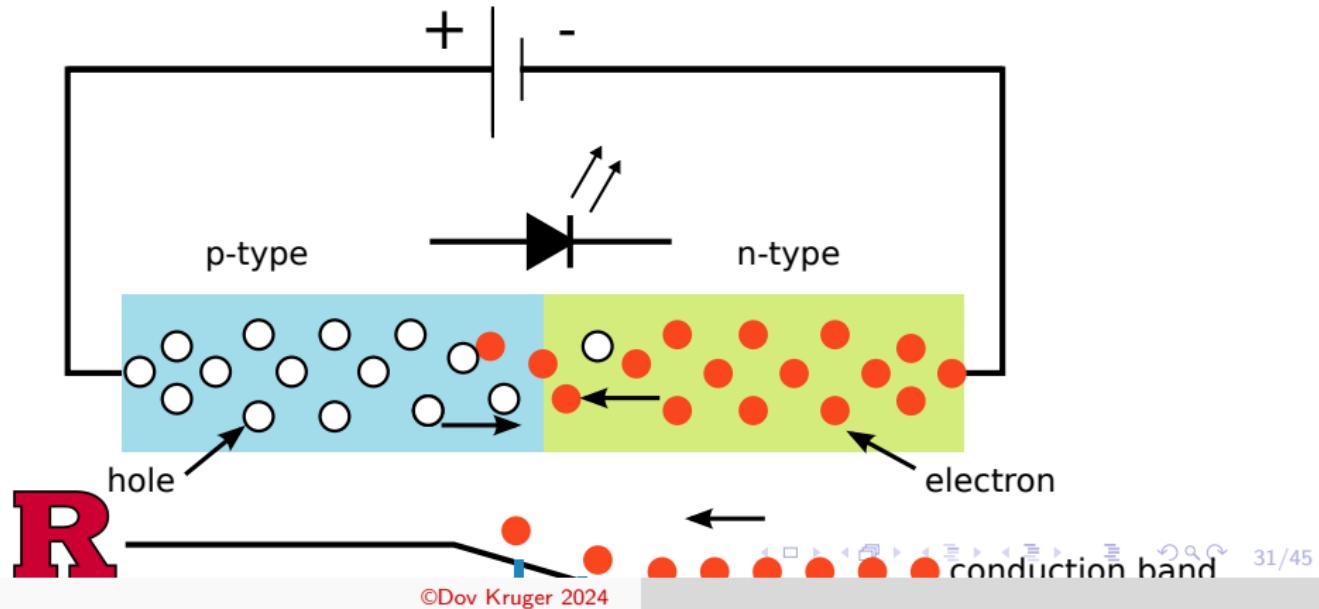
# How does an LED Work?

- LEDs are doped with specific chemicals
- Each electron crossing the gap loses a precise amount of energy
- The color is determined by the energy gap between the two layers
- see <https://www.youtube.com/watch?v=JBtEckh3L9Q>



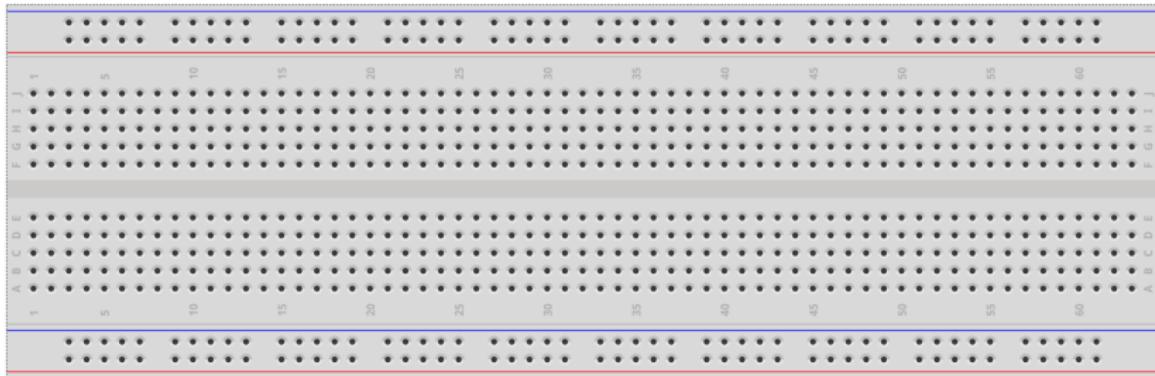
# Breadboard Connections

- Power busses: vertical columns on edges
- Rows: horizontal lines for component connections
- Power distribution: busses connected along entire length
- Row connectivity: each row is electrically connected




R

# Find the Bug

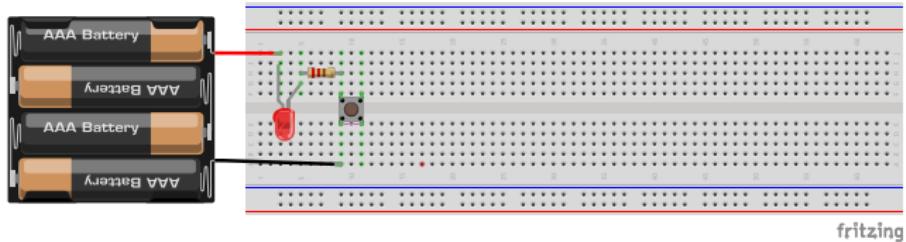


R

# Find the Bug

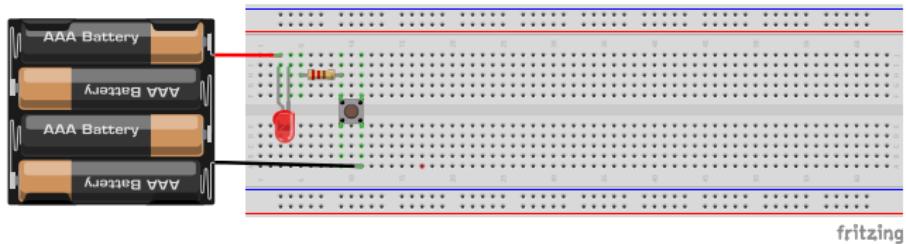


R

# Find the Bug

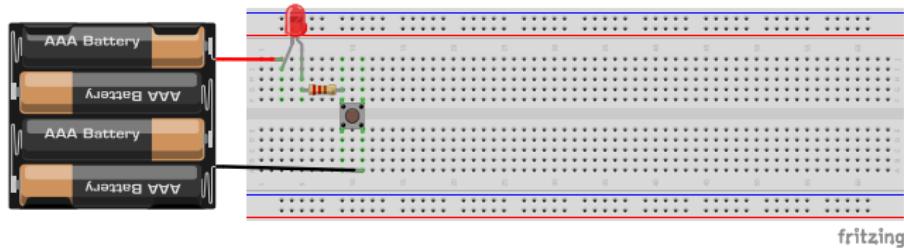


R

# Find the Bug

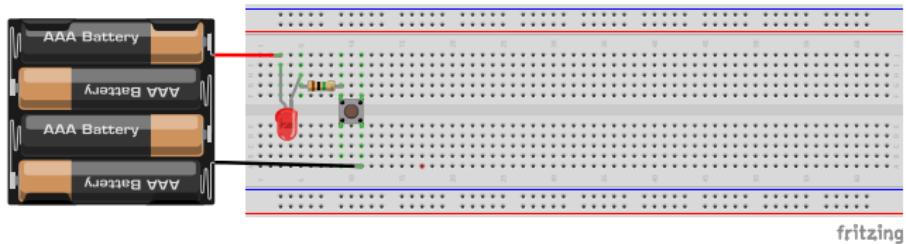


R

# Find the Bug

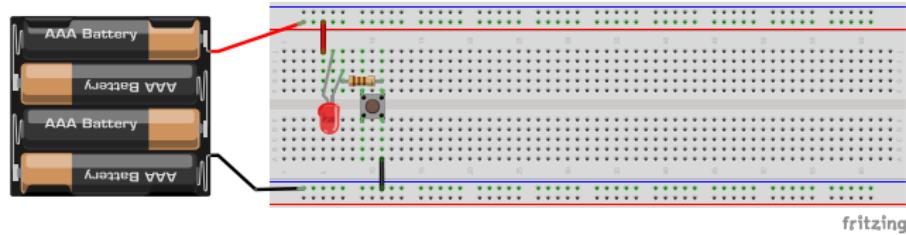


R

# Find the Bug

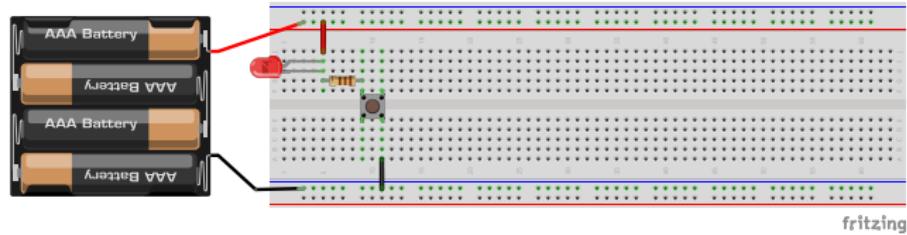


R

# Find the Bug

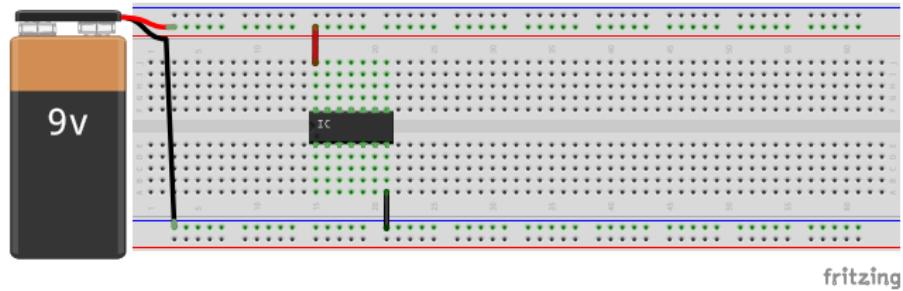


R

# Find the Bug

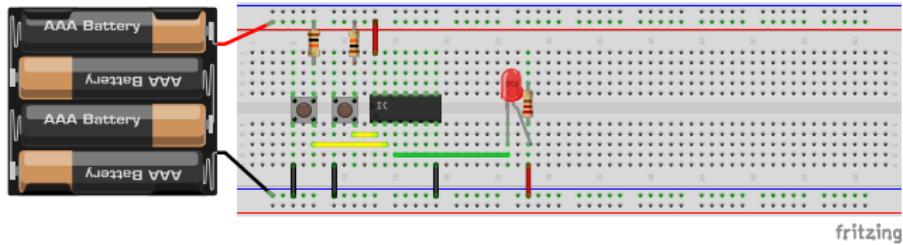

R


# Find the Bug

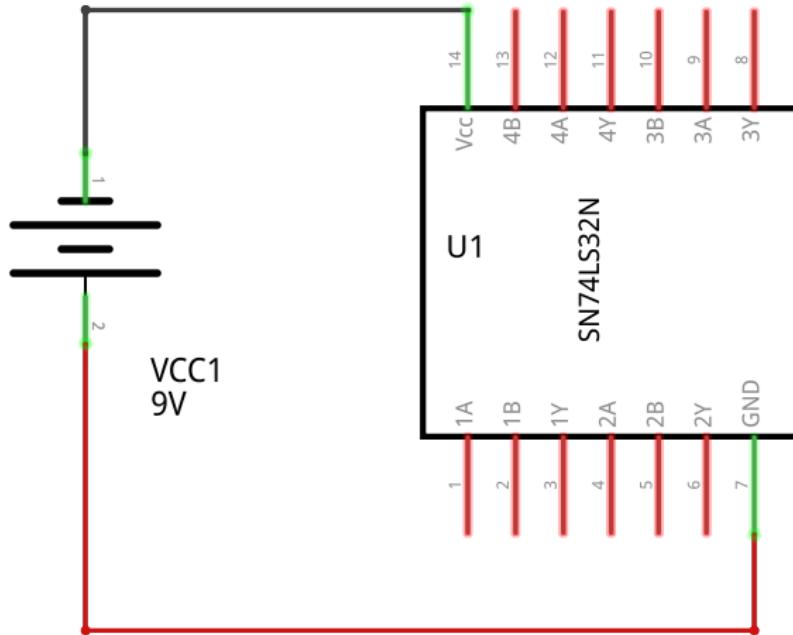

fritzing

R

# Find the Bug

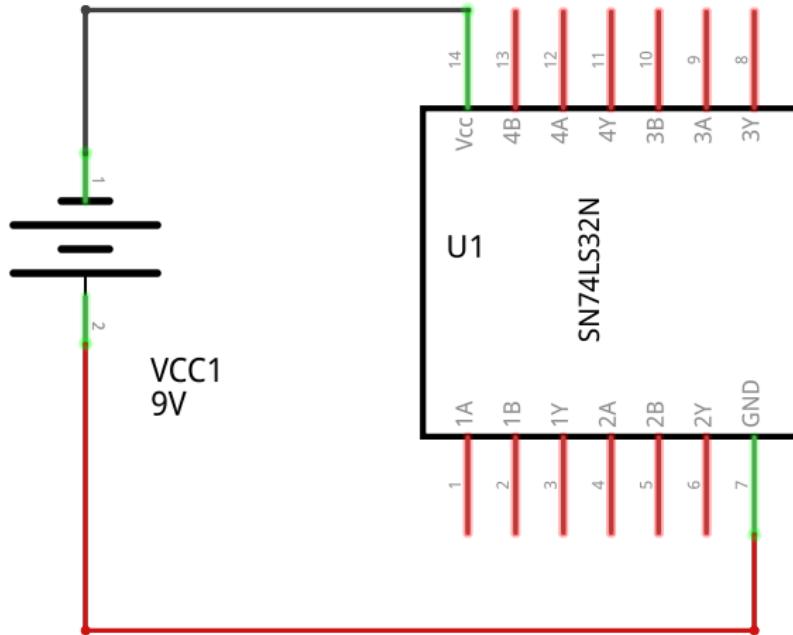

fritzing

R

# Introducing the DMM



R


## Measuring Voltage



E
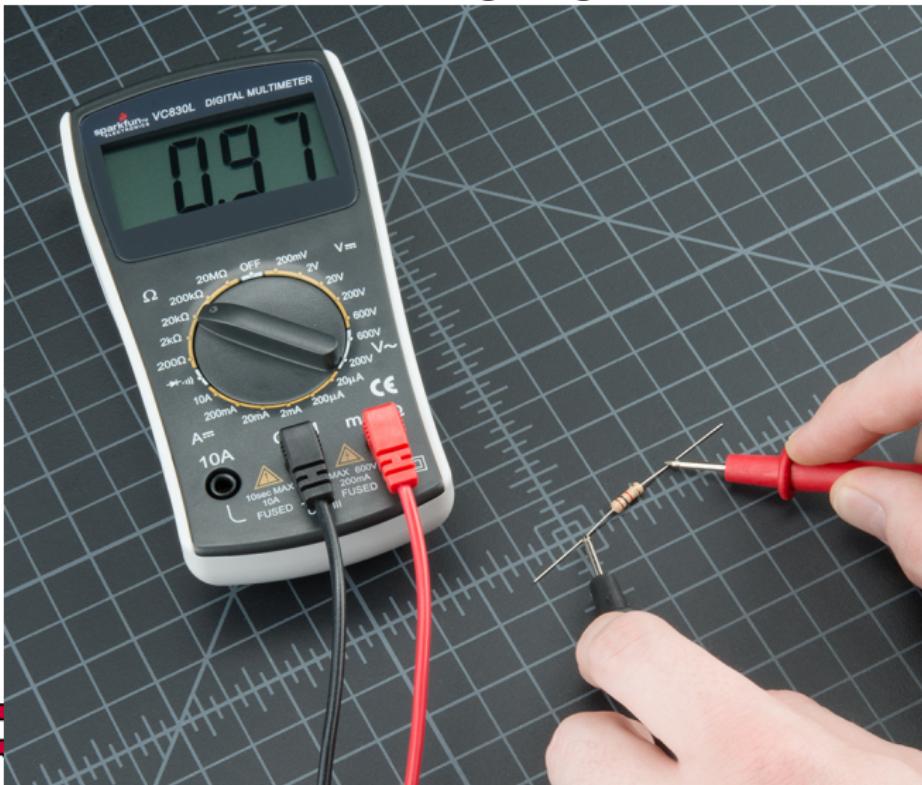
# Measuring Resistance

- Manual range DMM
- Set to the smallest range larger than the resistor



F

# How not to Measure Resistance

- What is



R