

# Arithmetic and Memory

Dov Kruger

Department of Electrical and Computer Engineering  
Rutgers University

October 27, 2025



# How do Computers do Arithmetic?

- This module describes how computers crunch numbers
- By the end you will be able to
  - Build a ripple carry adder
  - Calculate gate delays to know how long circuit takes
  - Design a faster carry look-ahead adder
  - Understand how multiplication works on a computer
  - Identify optimizations for multiplication and division (shift)
  - Learn what a flip-flop is and how it stores bits
  - Learn how to address memory




- ALU: Arithmetic Logic Unit
- LSB: Least Significant Bit
- MSB: Most Significant Bit
- Overflow: When the result of an operation is too large to be represented in the available bits


 
# Half Adder

- Half Adder: Adds two bits and outputs the sum and carry
- Inputs: A, B
- Outputs: Sum, Carry




# Full Adder

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



 
# Full Adder

- Full Adder: Adds two bits and outputs the sum and carry
- Inputs: A, B, Carry
- Outputs: Sum, Carry
- Count the gate delays
- 74LS gate delays typically 10ns
- modern gates in a CPU 5-20ps?



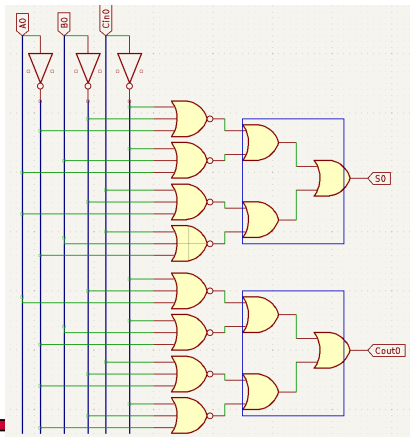
# More Realistic Full Adder

- XOR doesn't really exist
- Do as much as possible in parallel (not entirely, my CAD skills are not good)


 
# Ripple Carry Adder


- Ripple Carry Adder: Adds two numbers using full adders
- Inputs:  $A[3:0]$ ,  $B[3:0]$
- Outputs:  $\text{Sum}[3:0]$ , Carry
- Count the gate delays: 4




 
# Carry Look-Ahead Adder

- Carry Look-Ahead Adder: Adds 4 bits and calculates the carry
- Inputs:  $A[3:0]$ ,  $B[3:0]$ , Carry
- Outputs:  $\text{Sum}[3:0]$ , Carry
- Count the gate delays: 2



# When does Addition Overflow?

When the result is too large to be represented in the available bits  
Unsigned

- 
- Example:  $1111 + 0001 = 0000$  (overflow)
- Example:  $0111 + 0001 = 1000$  (no overflow)

Signed

- 
- Example:  $0111 + 0001 = 1000$  (-8, overflow)
- Example:  $0011 + 0011 = 0110$  (6, no overflow)



# Multiplication

- Multiplication is repeated addition and shifting
- Long Multiplication example

$$\begin{array}{r} 64 \\ 986 \\ * 157 \\ \hline 6902 \\ 49300 \\ 986000 \\ \hline \end{array}$$

- Then add the results



# Multiplication in Binary

Notice: multiplying two  $n$ -bit numbers produces a  $2n$ -bit number!



```
      01000001  (65)
x     00110001  (49)
```

```
      01000001  (This is 65 shifted by 0)
     010000010000  (This is 65 shifted by 4)
    0100000100000  (This is 65 shifted by 5)
  000011001110001
```


  
# Multiplication Implemented as a loop



- Using a clock, early computers would repeatedly add and shift
- for n-bit multiplication, takes n clock cycles
- For CPUs without a multiply, it's a program
- Doing it in hardware in a single operation requires  $n^2$  additions
- Faster than doing it in a loop, but still much slower than addition



- Since multiplication is much slower than addition, can we go faster?
- For a single multiplication, not this way
- But if we have many numbers, we can make the multiplier even slower, but pipeline the circuit
- Example: AMD 7700X CPU can
  - latency: It takes 4 clock cycles to get the answer
  - multiply 1 number every clock
  - Two multiplier units, so it can do 2 multiplies every clock



# Pipelining Multiplication

  


# 4-bit Example ALU Operations

- All operations shown are typical of computer ALUs
- Each operation completes in a single clock cycle
- 4-bit examples generalize to 8, 16, 32, 64+ bits
- Operations include: logic, shifts, rotates, bit masking






# ALU: Bitwise AND

 

Example: 1010 AND 1100 = 1000




# ALU: Bitwise OR

 

Example: 1010 OR 1100 = 1110




# ALU: Bitwise XOR

 

Example: 1010 XOR 1100 = 0110



# ALU: Bitwise NOT




 


Example: NOT 1010 = 0101



 
 
 
 
# ALU: Logical Shift Left

Shifting left by  $n$  bits is equivalent to multiplying by  $2^n$



 
 
 
 
# ALU: Logical Shift Right

Shifting right by  $n$  bits is equivalent to dividing by  $2^n$



 
 
 
 
# ALU: Arithmetic Shift Left

Shifting left by  $n$  bits is equivalent to multiplying by  $2^n$


    
# ALU: Arithmetic Shift Right


Shifting right by  $n$  bits is equivalent to dividing by  $2^n$   
Sign bit is preserved (sign extension).



**R**



# ALU: Rotate Left

 


bits lost.

MSB wraps around to LSB. No



# ALU: Rotate Right

 

bits lost.

LSB wraps around to MSB. No



# Rotate in C++ and in Verilog

- In the C family of languages there is no rotate operation.

- However, we can construct one

```
rotr(x, n, size) = (x << n) | (x >> (size - n))
```

```
rotr(x, n, size) = (x >> n) | (x << (size - n))
```

- In Verilog we can construct it using:

```
rotr(x, n, size) = {x[n-1:0], x[size-1:n]}
```

```
rotr(x, n, size) = {x[size-n-1:0], x[size-1:size-n]}
```

Verilog example to rotate an a left by 2, and b right by 3

```
logic [7:0] a, b;
```

```
assign a_rotr = {a[5:0], a[7:6]};
```

```
assign b_rotr = {b[2:0], b[7:3]};
```



# Bit Masking: Set Bits with OR

Set specific bits to 1 using OR with a mask.

Data:	×	1	×	0
Mask:	1	0	1	0
OR				
Result:	1	1	1	0

Mask 1 bits force to 1; 0 bits pass through unchanged.



# Bit Masking: Clear Bits with AND

Clear specific bits to 0 using AND with inverted mask.

Data:	×	1	0	×
Mask:	0	1	1	0
AND				
Result:	0	1	0	0

Mask 0 bits force output to 0; 1 bits pass through.



# Bit Masking: Toggle Bits with XOR

Toggle specific bits using XOR with mask.

Data:	0	1	0	1
Mask:	0	1	1	0
XOR				
Result:	0	0	1	1

Mask 1 bits flip the corresponding data bit; 0 bits leave unchanged.



# Bit Masking: Testing bits

To test if a bit is set, AND with 1 in that position



# Bit Masking: Testing multiple Bits

To test if one of n bits are set, AND with 1 in those positions

Example: Test if any of the bits marked x are set

```
10001xxxx010100010
```

```
000001111000000000
```

First AND. All the rest of the bits turn to 0

if the number is not zero, then at least one of the bits is set

Example:

$Data = F32D, Mask = 0F00, Data \text{ AND } Mask = 0300$

Not zero, so at least one of the bits where the mask is 1 are set





# Bit Masking: Testing multiple Bits

To test if EVERY one of  $n$  bits are set, AND with 1 in those positions

Example: Test if ALL of the bits marked  $x$  are set

```
10001xx010x1000x10
000001100010000100
```

First AND. All the rest of the bits turn to 0  
if the result ( $A \text{ AND } MASK$ ) =  $MASK$  then ALL the bits are set

```
100011001011000110 AND
000001100010000100
000001000010000100 = DATA AND MASK
```

Example:  $DATA \text{ AND } MASK \neq MASK$ , so not all the bits are set



# ALU Status Flags

- **Z (Zero):** Set if result = 0
  - Example:  $0101 \text{ XOR } 0101 = 0000 \Rightarrow Z=1$
- **N (Negative):** Set if MSB = 1 (signed interpretation)
  - Example:  $1010 \Rightarrow N=1$  (= -6 in 4-bit signed)
- **V (Overflow):** Set if signed operation overflows
  - Example:  $0111 + 0001 = 1000 \Rightarrow V=1$  (7+1=-8 wrong!)
- **C (Carry):** Set if unsigned operation carries out
  - Example:  $1111 + 0001 = 0000$  with carry  $\Rightarrow C=1$



# How Does the ALU Work?

- Each circuit is a simple function of the inputs
- Combining them is a multiplexer
- We have to ignore all functions that aren't selected
- Two ways to do this
  - AND output with an enable signal for each function
  - Use a tri-state buffer to disable every function except the selected one



# Simple Example: ALU Combining Two functions

Very simple ALU:

- $OP = 0$ , A AND B
- $OP = 1$ , A OR B



# Simple ALU Using Tri-State Buffers




# Latches, Flipflops and Registers

- Latches are level-triggered memory elements
- Flipflops are edge-triggered memory elements
- A D-type flipflop is the fundamental building block of memory
- Registers are collections of flipflops
- Registers are used to store data
- Registers are used to store instructions
- Registers are used to store addresses


 
# D Type Flipflop


- D Type Flipflop: Stores a bit
- Inputs: D, Clock
- Outputs: Q
- Every time the clock ticks, data is stored


 
# D Type Flipflop Implementation

\* Select Simulate "Run Time Domain Simulation" to verify.


\*\* REMARK: Do not destroy and paste anything from outside the box (especially the node labels) unless you "nest" to these inputs together on all your flip flops.





 
# Building a Register

- Fastest computer memory is an array of flipflops
- Here is an 8-bit register


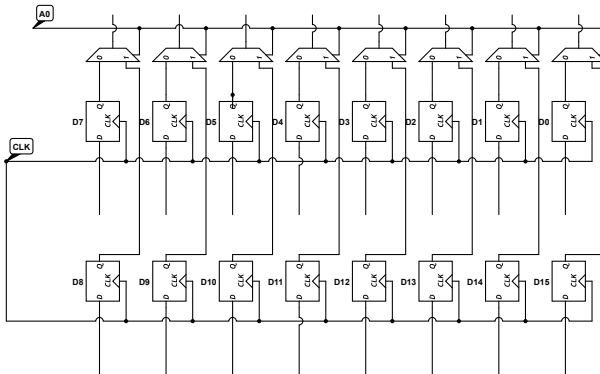
# Simplified Addressing Read Example: 1 bit



**R**



# Simulating Registers in Verilog

- First approach is a case statement
- However, this will get unwieldy many registers

```
module register(  
    input  [1:0] addr ,  
    input  [7:0] data ,  
    input  write ,  
    output [7:0] out  
);
```



# Simulating Registers in Verilog

```
reg [7:0] a, b, c, d
always @(posedge clk) begin
    if (write) begin
        case (addr)
            2'b00: a <= data;
            2'b01: b <= data;
            2'b10: c <= data;
            2'b11: d <= data;
        endcase
    end
    case (address)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
        2'b11: out = d;
    endcase
end
```



end

- Arrays are ordered lists of variables

```
integer x; // one 32-bit integer  
integer y[10]; // 10 integers, from y[0] to y[9]  
integer z[3:0]; // 4 integers, from z[0] to z[3]  
reg [7:0] r[3:0]; // 4 8-bit registers, r[0] to
```



## Register File using Arrays

```
module register_file(  
    input  [1:0]  addr,  
    input  [7:0]  data,  
    input  write ,  
    input  clk ,  
    output [7:0]  out  
);  
  
    reg [7:0] registers [3:0];  
    always @(posedge clk) begin  
        if (write) begin  
            registers[addr] <= data;  
        end  
        out <= registers[addr];  
    end  
endmodule
```

